

Loads in MOS Amplifiers

- (i) Resistive load — Actual Resistor as Load
- (ii) Active load — Device as Resistor




CDEEP
IIT Bombay


EE 618 L 10 / Slide 1

Active Loads: —

(A) Diode Connected Loads:

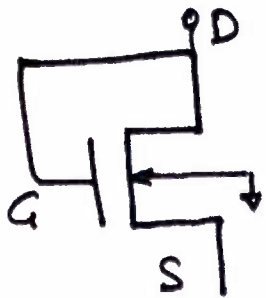

n-MOS

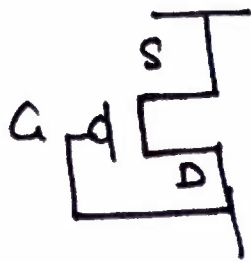

PMOS

In this case $V_{GD} = 0$

We have $V_{DS} = V_{GS} + V_{GD}$ for Normal Case.


\therefore Here $V_{DS} = V_{GS}$

$\text{or } V_{GS} - V_T < V_{DS}$ Device is


Always in Saturation. Then

$$I_{DS} = \frac{\beta}{2} (V_{GS} - V_T)^2 \quad \text{If } \lambda \text{ is } V \cdot \text{small}$$

This is constant current source.

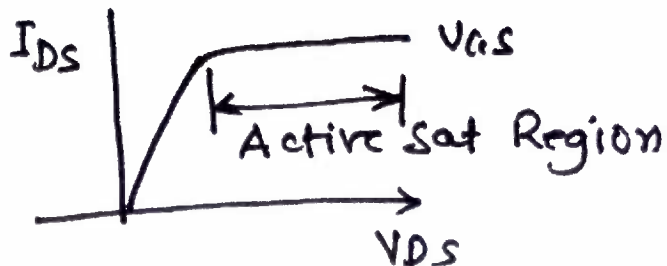

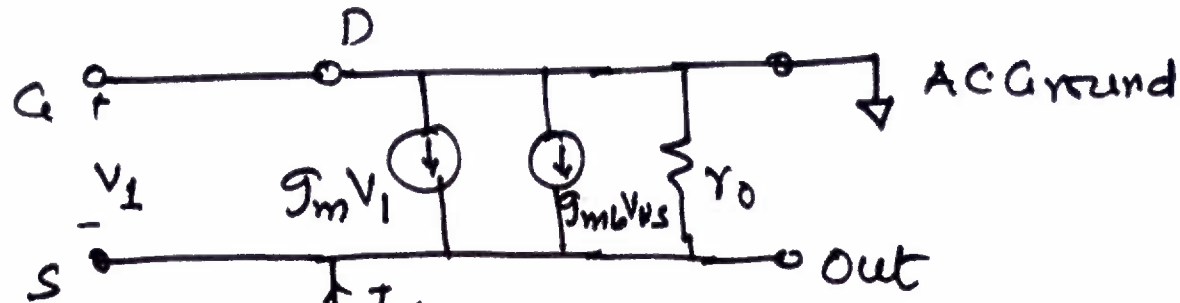Eq. CKT to evaluate R_o of Current Source.



We impress a voltage source at the Output as V_x and let us say I_x is the current

Then $R_o = \frac{V_x}{I_x}$ Here $V_{bs} = 0 - V_x$

$$I_x = + (g_m + g_{mb}) V_x + \frac{V_x}{r_o}$$

$$\therefore I_x = \left[g_m + g_{mb} + \frac{1}{r_o} \right] V_x$$

$$\therefore R_o = \frac{V_x}{I_x} = \frac{r_o}{1 + (g_m + g_{mb}) r_o} \approx \frac{1}{g_m + g_{mb}}$$



CDEEP
IIT Bombay


To improve g_{out} we must reduce g_m of Load transistor. But-

$$g_m = \sqrt{2\beta'(W/L)} (I_{D_S})^{1/2}$$

For a set value of I_{D_S} , reduction in W/L reduces g_m , or increases R_o of load source.

Then Gain = $-g_{m1} R_{out}$

Here $R_{out} = R_{o2} || r_{o1} = \frac{r_{o1}}{g_{m2} + g_{mb2}} / (r_{o1} + \frac{1}{g_m'})$

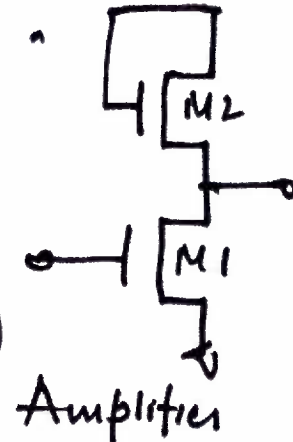

$$\therefore A_{vo} = - \frac{g_{m1} r_{o1}}{g_{m2} (1 + \eta)}$$

$$A_{vo} = - \frac{g_{m1} r_{o1}}{(1 + \eta) g_{m2} r_{o1} + 1}$$

$$\approx - \frac{g_{m1}}{g_{m2}} = - \frac{\sqrt{2\beta'(W/L)_1 I_{D_S}}}{(1 + \eta) \sqrt{2\beta'(W/L)_2 I_{D_S}}}$$

$$\approx A_{vo} = \sqrt{\frac{(W/L)_1}{(W/L)_2}} \cdot \frac{1}{1 + \eta}$$



CDEEP
IIT Bombay

Differential Amplifier


In Single Stage Amplifier (CS, CA or CD),

one of the issue is 'Biasing' for a Q-point.

Since Gain of the Amplifier is constant only if g_m & r_o are constant

However position of V_{bias} along with Input Signal V_{in} , cannot keep these two parameters (g_m & r_o) as constant.

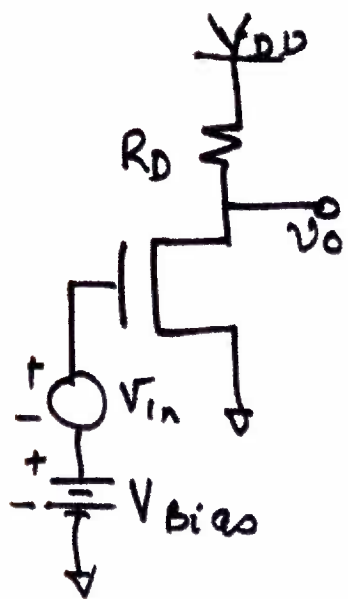Stating Precisely, we observe that output voltage is not constant in particular case of large 'Gain' Amplifier.



CDEEP
IIT Bombay


EE 618 L 10 / Slide 4

If we use constant current biasing, may be this issue can be addressed
A typical Biasing System could be



CDEEP
IIT Bombay

EE 618 L ___ / Slide 5

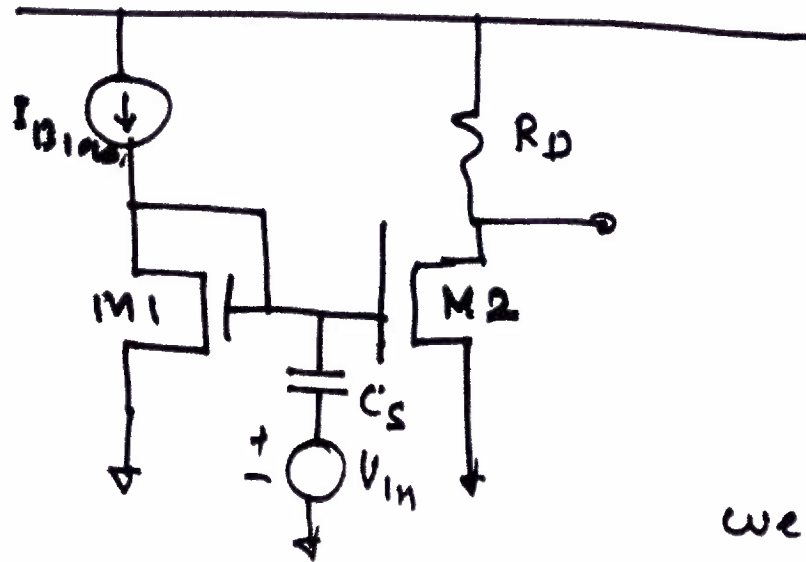

C_S is large series capacitance to block DC from V_{in} .


To achieve better blocking we need a High Pass filter at Input.

Modified Biasing scheme may be



CDEEP
IIT Bombay

EE 618 L / Slide 6

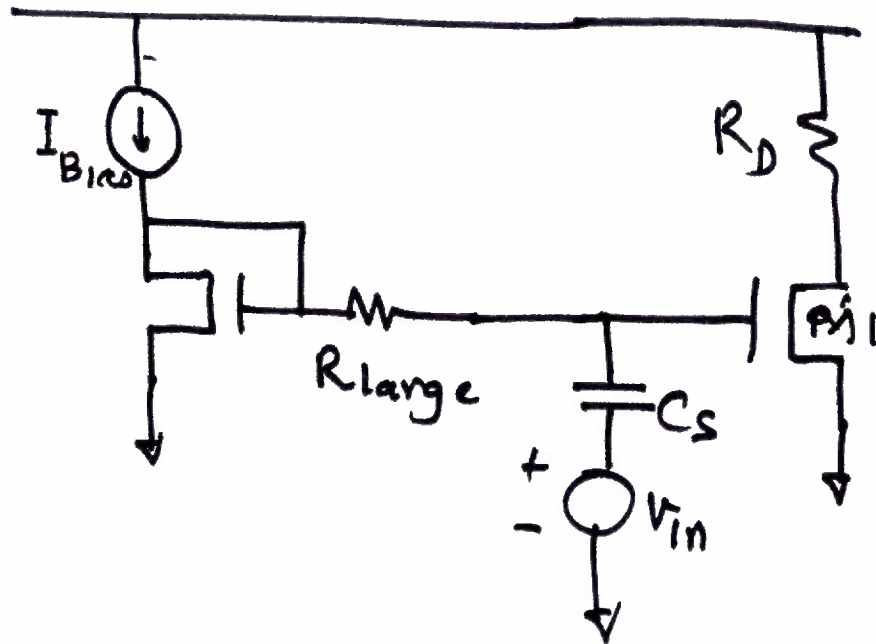

High Pass Filter Cut off frequency

$$f_c = \frac{1}{2\pi R_{\text{large}} C_s}$$

For f_c to be lower both R and C should be v. large.
Which means they will require large Area.


However with this Scheme, g_m of $M1$ will only be decided by I_{Bias} and not by V_{Bias}

Differential Amplifier is a better solution to this Biasing Problem



CDEEP
IIT Bombay

EE 618 L ____ / Slide 7

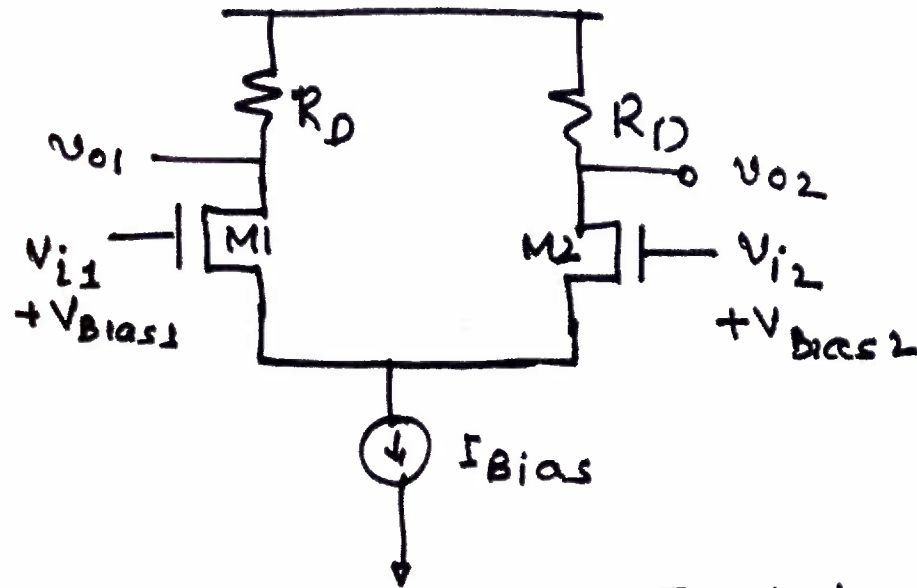

If $V_{Bias1} = V_{Bias2}$

then we see that-


g_m for M1 & M2 are decided by Tail current source I_{Bias}

An interesting outcome is that Difference $(V_{O1} - V_{O2})$ voltage is proportional to Input difference voltage $(V_{i1} - V_{i2})$



CDEEP
IIT Bombay

EE 618 L ____ / Slide 8

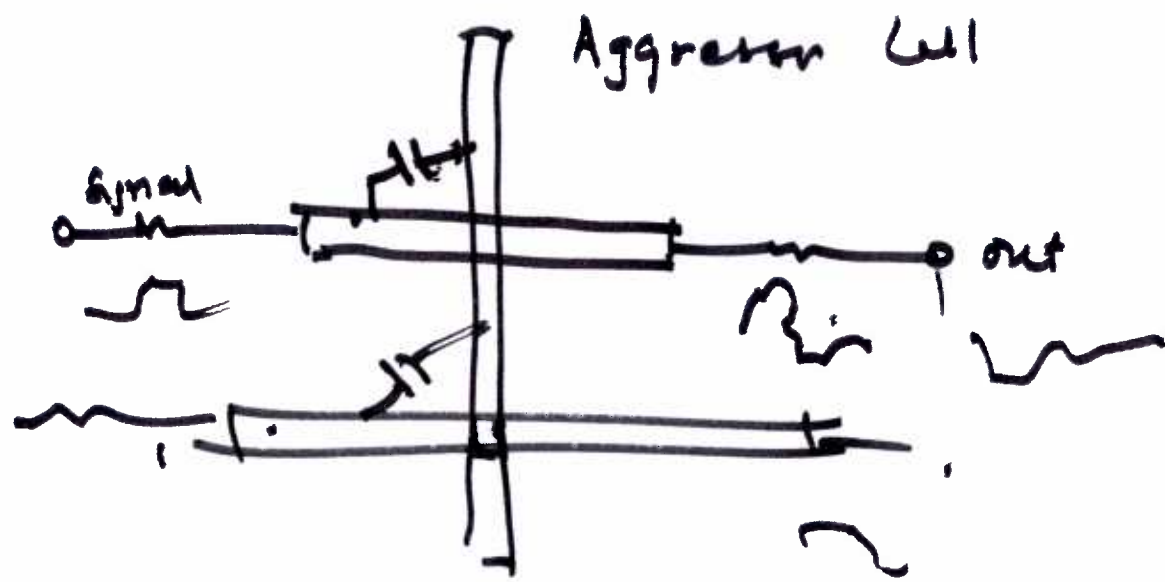

We have

$$I_{DS} = \frac{\beta}{2} (V_{GS} - V_T)^2$$

$$\therefore V_{GS} = \sqrt{\frac{2I_{DS}}{\beta}} + V_T$$

$$\begin{aligned} \therefore V_{in1} - V_{in2} &= \sqrt{\frac{2I_{DS1}}{\beta}} + V_T - \sqrt{\frac{2I_{DS2}}{\beta}} - V_T \\ &= \sqrt{\frac{2I_{DS1}}{\beta}} - \sqrt{\frac{2I_{DS2}}{\beta}} \end{aligned}$$


Further $I_{DS1} + I_{DS2} = I_{SS}$ For all cases.

$$\begin{aligned} (V_{in1} - V_{in2})^2 &= \frac{2I_{DS1}}{\beta} + \frac{2I_{DS2}}{\beta} - \frac{4}{\beta} \sqrt{I_{DS1} I_{DS2}} \\ &= \frac{2}{\beta} (I_{SS}) - \frac{4}{\beta} \sqrt{I_{DS1} I_{DS2}} \end{aligned}$$



CDEEP
IIT Bombay

Large Signal Behavior of DIFFAMP.

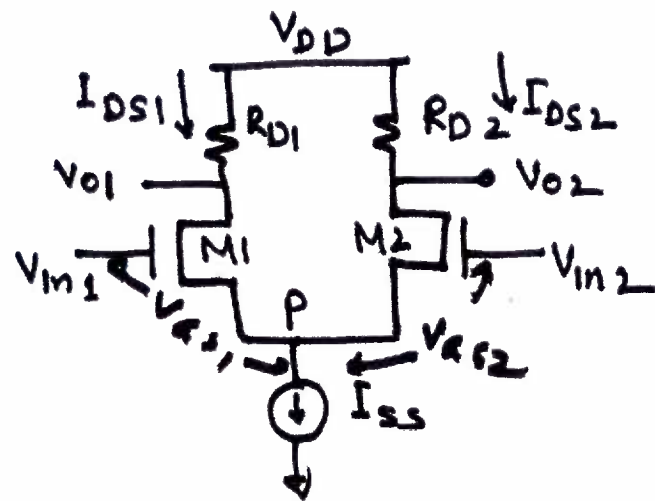

V_{in1} & V_{in2} are inputs to $M1$ & $M2$

By circuit Analysis

$$V_{01} = V_{DD} - I_{DS1} R_{D1}$$

$$V_{02} = V_{DD} - I_{DS2} R_{D2}$$

$$\therefore V_{01} - V_{02} = I_{DS2} R_{D2} - I_{DS1} R_{D1}$$

$$= (I_{DS2} - I_{DS1}) R_D \quad \text{if } R_{D1} = R_{D2} = R_D$$

Further

$$V_{in1} - V_{in2} = V_{gs1} - V_{gs2}$$

We assume for all case now onward that $\lambda=0$ if not stated otherwise.



CDEEP
IIT Bombay