

Frequency Response of Amplifiers

Concepts of Poles & Zeros.

A Transfer Fⁿ.
$$A_v(s) = A_{vo} \cdot \frac{(s/\omega_z + 1)}{(s/\omega_1 + 1)(s/\omega_2 + 1)}$$

ω_z is called 'zero' frequency at which $A_v(s) \rightarrow 0$

ω_1, ω_2 - - are Poles (Pole frequencies) at which $A_v(s) \rightarrow \infty$

In a typical MOS Amplifier we have around
Two 'Poles' and one 'zero'

Two Poles occur from Input side & Output side

These can be termed as ω_{in} and ω_{out}

And ω_z is a 'zero' frequency occurring due to
Feedback.



CDEEP
IIT Bombay

EE 618 L16 / Slide

Ref. : Sedra, Smith & Chandorkar
Page 34 / 35



CDEEP
IIT Bombay

SINGLE POLE TRANSFER FUNCTION

EE 618 L 16 / Slide

34 CHAPTER 1 INTRODUCTION TO ELECTRONICS

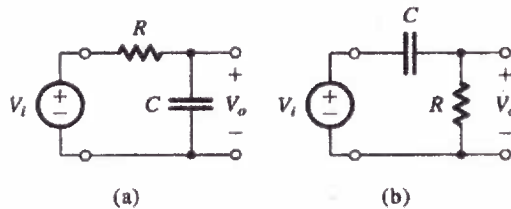


FIGURE 1.22 Two examples of STC networks: (a) a low-pass network and (b) a high-pass network.

TABLE 1.2 Frequency Response of STC Networks

	Low-Pass (LP)	High-Pass (HP)
Transfer Function $T(s)$	$\frac{K}{1 + (s/\omega_0)}$	$\frac{Ks}{s + \omega_0}$
Transfer Function (for physical frequencies) $T(j\omega)$	$\frac{K}{1 + j(\omega/\omega_0)}$	$\frac{K}{1 - j(\omega_0/\omega)}$
Magnitude Response $ T(j\omega) $	$\frac{ K }{\sqrt{1 + (\omega/\omega_0)^2}}$	$\frac{ K }{\sqrt{1 + (\omega_0/\omega)^2}}$
Phase Response $\angle T(j\omega)$	$-\tan^{-1}(\omega/\omega_0)$	$\tan^{-1}(\omega_0/\omega)$
Transmission at $\omega = 0$ (dc)	K	0
Transmission at $\omega = \infty$	0	K
3-dB Frequency	$\omega_0 = 1/\tau$; τ = time constant $\tau = CR$ or L/R	
Bode Plots	in Fig. 1.23	in Fig. 1.24

BODE PLOTS of STC

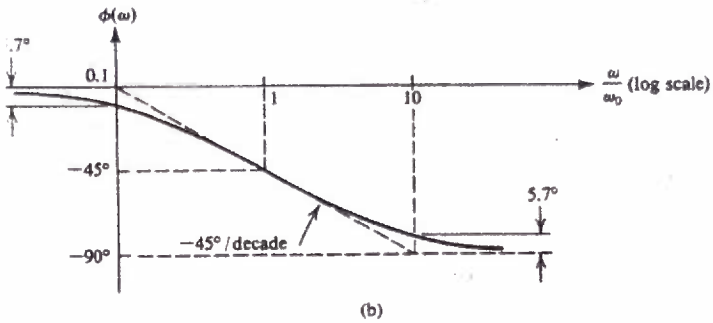
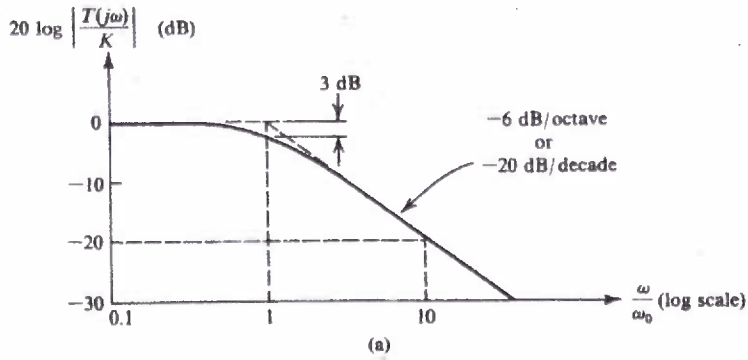


FIGURE 1.23 (a) Magnitude and (b) phase response of STC networks of the low-pass type.


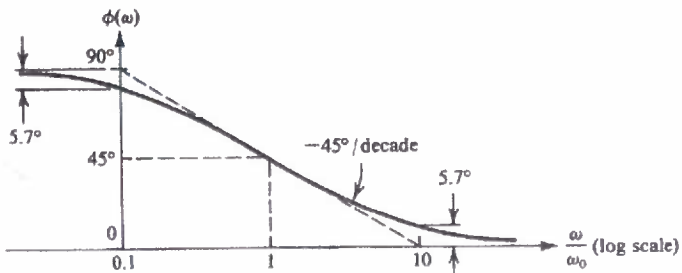


FIGURE 1.24 (a) Magnitude and (b) phase response of STC networks of the high-pass type.

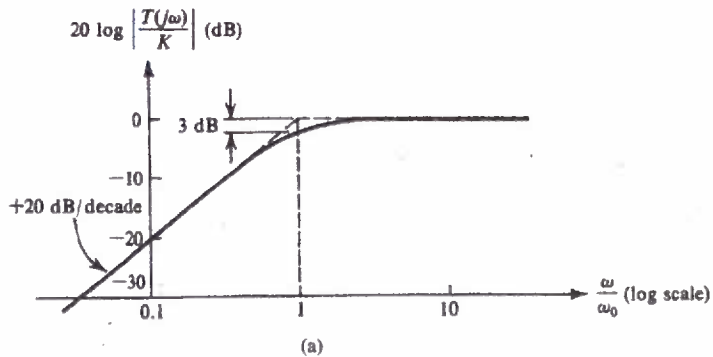

CDEEP
IIT Bombay


EE 618 L 16 / Slide





CDEEP
IIT Bombay

EE 618 L 16 / Slide

Input pole & Output Pole

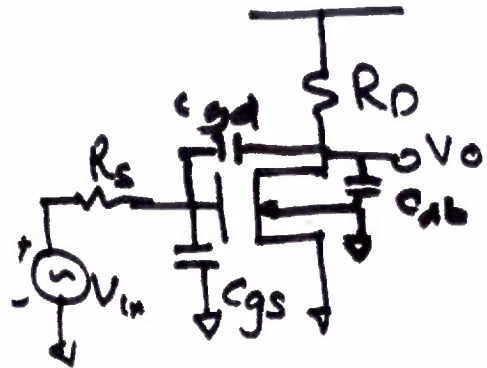

$$\omega_{in} = \frac{1}{R_s C_{gs}}$$

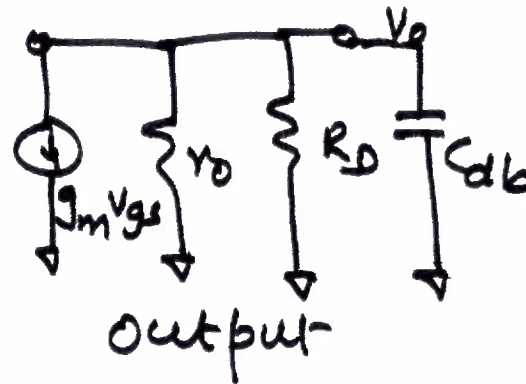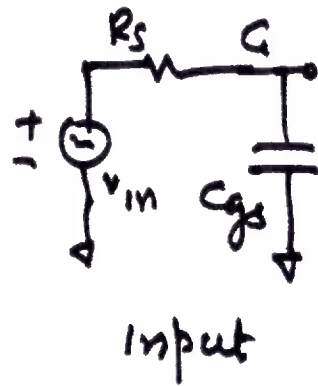


$$r_o \parallel R_D \approx R_D$$

$$\omega_{out} = \frac{1}{R_D C_{db}}$$

However in equivalent ckt of Amplifier we also have capacitance C_{gd}

Then E_s ckt looks like

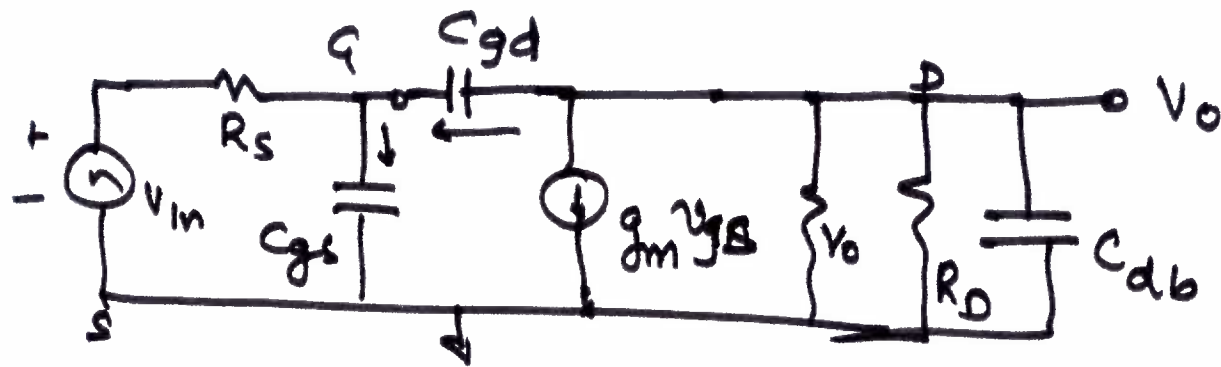

CDEEP
IIT Bombay

Assume EE 618 L 16 / Slide

roll $R_D = R_D$

Also C_{db} effect is neglected

$$v_{gs} = \frac{\frac{1}{C_{gs} \cdot s}}{\frac{1}{s C_{gs}} + R_s} v_{in} = \frac{v_{in}}{1 + s \cdot R_s C_{gs}}$$

C_{gs} may include C_{gb} as it may occur in saturation.

$$\text{Then } A'_v(s) = \frac{v_o(s)}{v_{gs}(s)} = - \left\{ g_m R_D \right\} \left\{ \frac{1 - \cancel{g_m} C_{gd} \cdot s}{g_m} \right\}$$

$$A_v(s) = \frac{v_o(s)}{v_{in}(s)} = - (g_m R_D) \frac{(1 - s \cdot C_{gd} / g_m)}{(1 + s R_s C_{gs}) (1 + s \cdot R_D C_{gd})}$$

Approximately looking at denominator we see

$$D = g_m (1 + s R_s C_{gs}) (1 + s R_D C_{gd})$$

$$\approx (1 + s R_s C_{gs}) (g_m + s \cdot g_m R_D C_{gd})$$

$$= (1 + s R_s C_{gs}) (g_m + (-A_{vo}) s \cdot C_{gd})$$

$$\approx 1 + s \{ C_{gs} + (1 + A_{vo}) C_{gd} \} R_s$$

$$= 1 + R_s (C_{gs} + (1 + g_m R_D) C_{gd}) \cdot s$$

$$= 1 + R_s C_{in} \cdot s$$


$$C_{in} = C_{gs} + (1 + g_m R_D) C_{gd}$$

$$\therefore \omega_{in} = \frac{1}{R_s C_{in}}$$




CDEEP
IIT Bombay

EE 618 L 16 / Slide

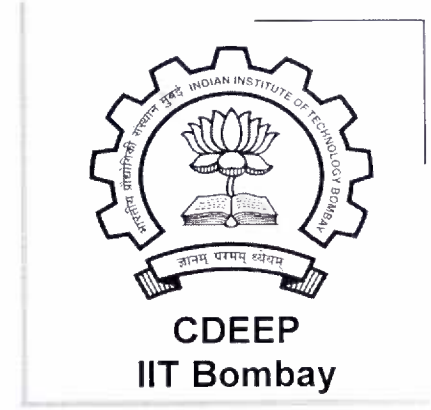


Similar Result we can attain by using Miller's Theorem:

Given

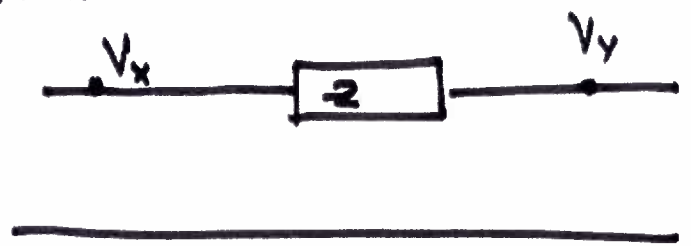

where $A = \frac{V_y}{V_x}$ (Gain FN)

We can convert this to

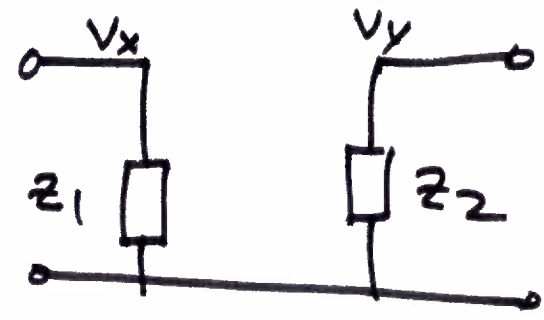


where

$$z_1 = \frac{z}{1-A}$$


$$\& z_2 = \frac{A}{1-A} \cdot z$$

If z is capacitive C_{xy}

Limitations of Miller's Theorem

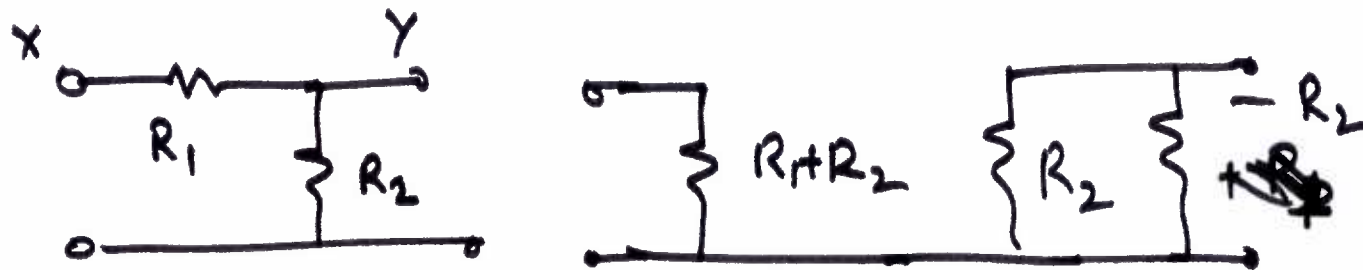

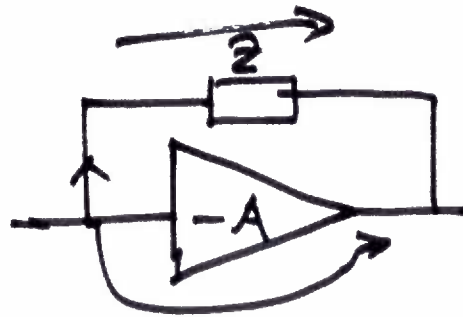We must have Two Paths from Input to Output for validity of Miller's theorem.




CDEEP
IIT Bombay



CDEEP
IIT Bombay

EE 618 L 16 / Slide

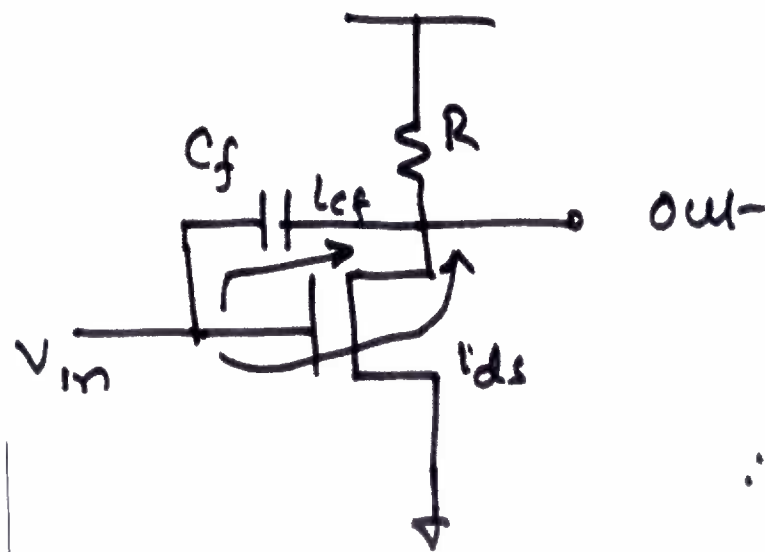Continuing similar argument, we can see that a 'zero' of Transfer Function is only possible if we have two paths from Input to Output and at a frequency the value of current in two paths are equal in magnitude and 180° out of phase.



This is due to effect of
"Feed Forward"

$$I_{Cf} = -I_{ds}$$

$\therefore I = 0 \quad \therefore V_{out} = 0 \rightarrow$ 'Zero' Occurrence





CDEEP
IIT Bombay


EE 618 L 16 / Slide

Returning to our problem of Frequency response of a CS Amplifier, whose HF

model can be shown with ckt as -

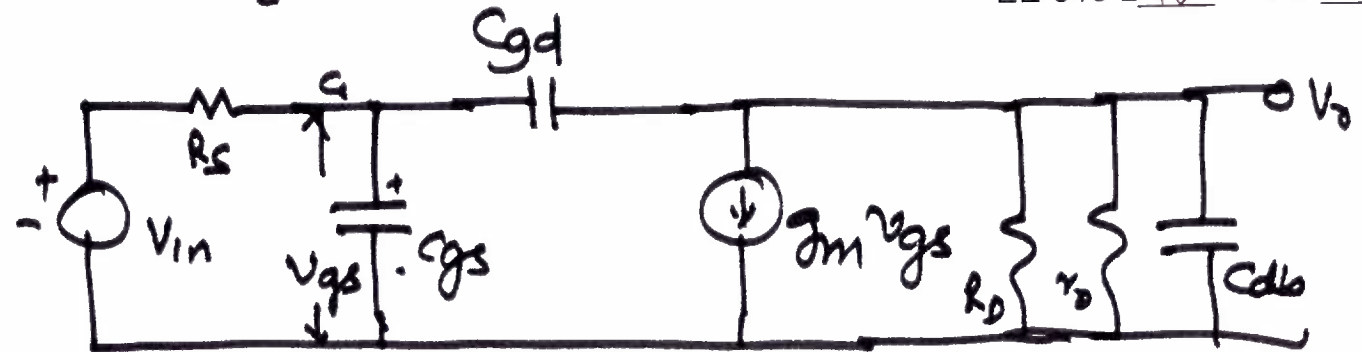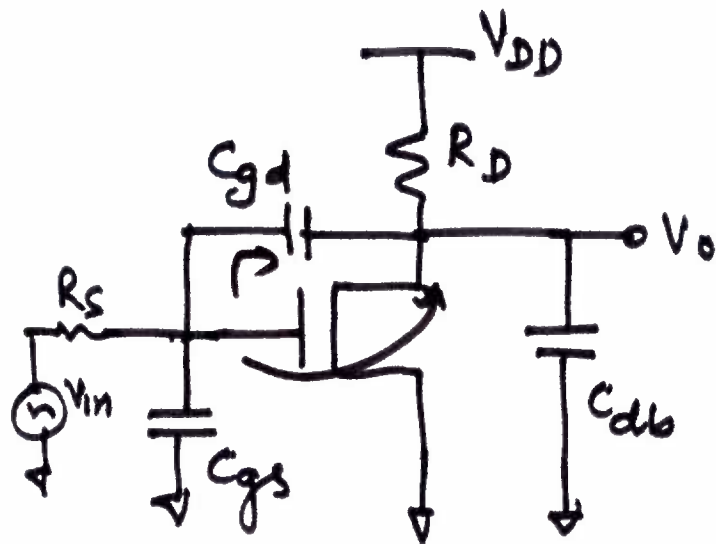

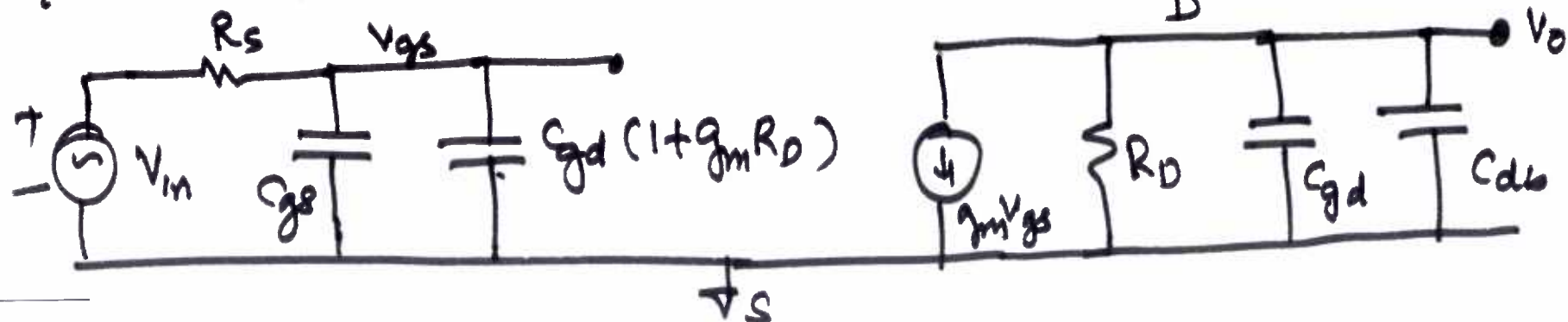Using DC Gain expression $A_{vo} = -g_m R_D$, we see that G_s ckt could be shown using Miller's theorem as :-





CDEEP
IIT Bombay

EE 618 L 16 / Slide

Then

$$\omega_{in} = \frac{1}{R_s [C_{gs} + (1 + g_m R_D) C_{gd}]}$$

$$\& \omega_{out} = \frac{1}{R_D (C_{gd} + C_{db})}$$

And Transfer F^n can be written as

$$A_v(s) = \frac{A_{vo}}{\left(1 + \frac{s}{\omega_{in}}\right) \left(1 + \frac{s}{\omega_{out}}\right)}, \quad A_{vo} = -g_m R_D$$