

Stability studies using Bode's Frequency Plots.

For an Amplifier with feedback, we have

$$\text{T. function: } A_{eL}(s) = \frac{A_o(s)}{1 + A_o(s)\beta(s)}$$

We have defined $L(s)$ as Loop Gain = $A_o(s)\beta(s)$

$$\begin{aligned} \gamma \quad L(j\omega) &= A_o(j\omega)\beta(j\omega) \\ &= |A_o(j\omega)\beta(j\omega)| e^{j\phi(\omega)} \quad \text{Phasor} \end{aligned}$$

$\phi(\omega)$ is the Phase angle

If $\phi(\omega_0) = 180^\circ$ then $|A_o(j\omega_0)\beta(j\omega_0)| \cdot e^{j(180^\circ)}$

which means $L(j\omega_0) = -\underline{\text{Real}}$

Thus we can say Positive feedback commences,



CDEEP
IIT Bombay

EE 618 L 18 / Slide 1



CDEEP
IIT Bombay



EE 618 L 19 / Slide 2

As then we observe that the Denominator reduces $[1 - \{A_o(j\omega_o)\beta(j\omega_o)\}]$, and thus

$$\text{Then } A_{CL}(j\omega_o) > A_o(j\omega_o)$$

$A_o \equiv$ open loop Gain.

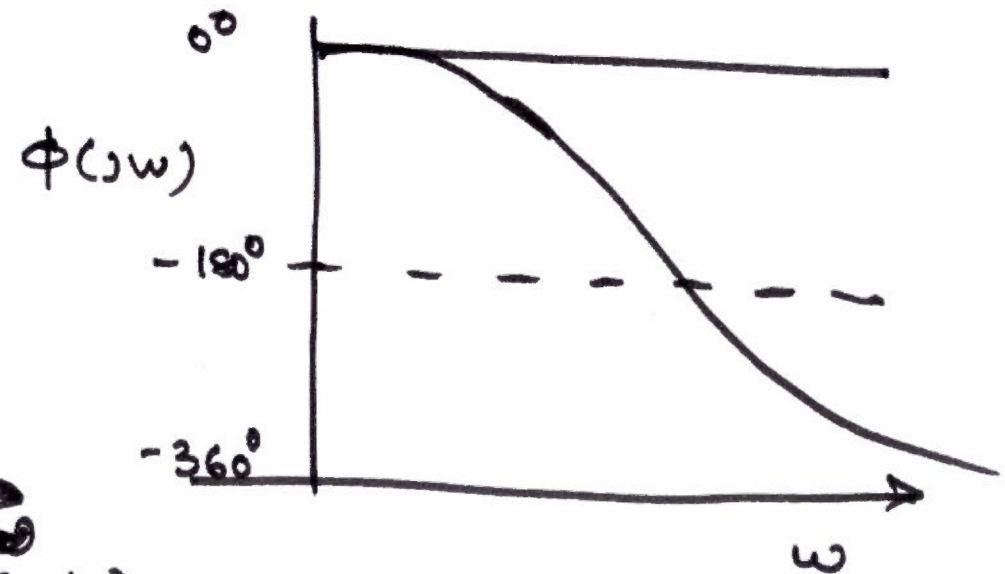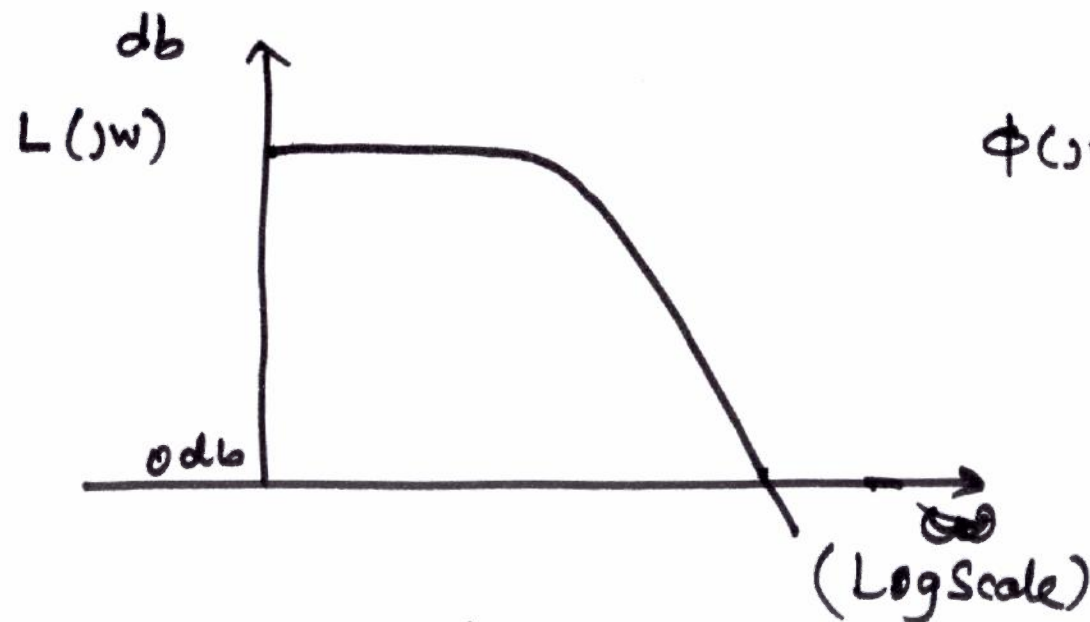This is the case of Positive feedback which will then make Amplifier Unstable.




Bode's Plot for Loop Gain

If this condition is met, the feedback system is said to be stable




CDEEP

EE618: 20-15
SI. No. 3

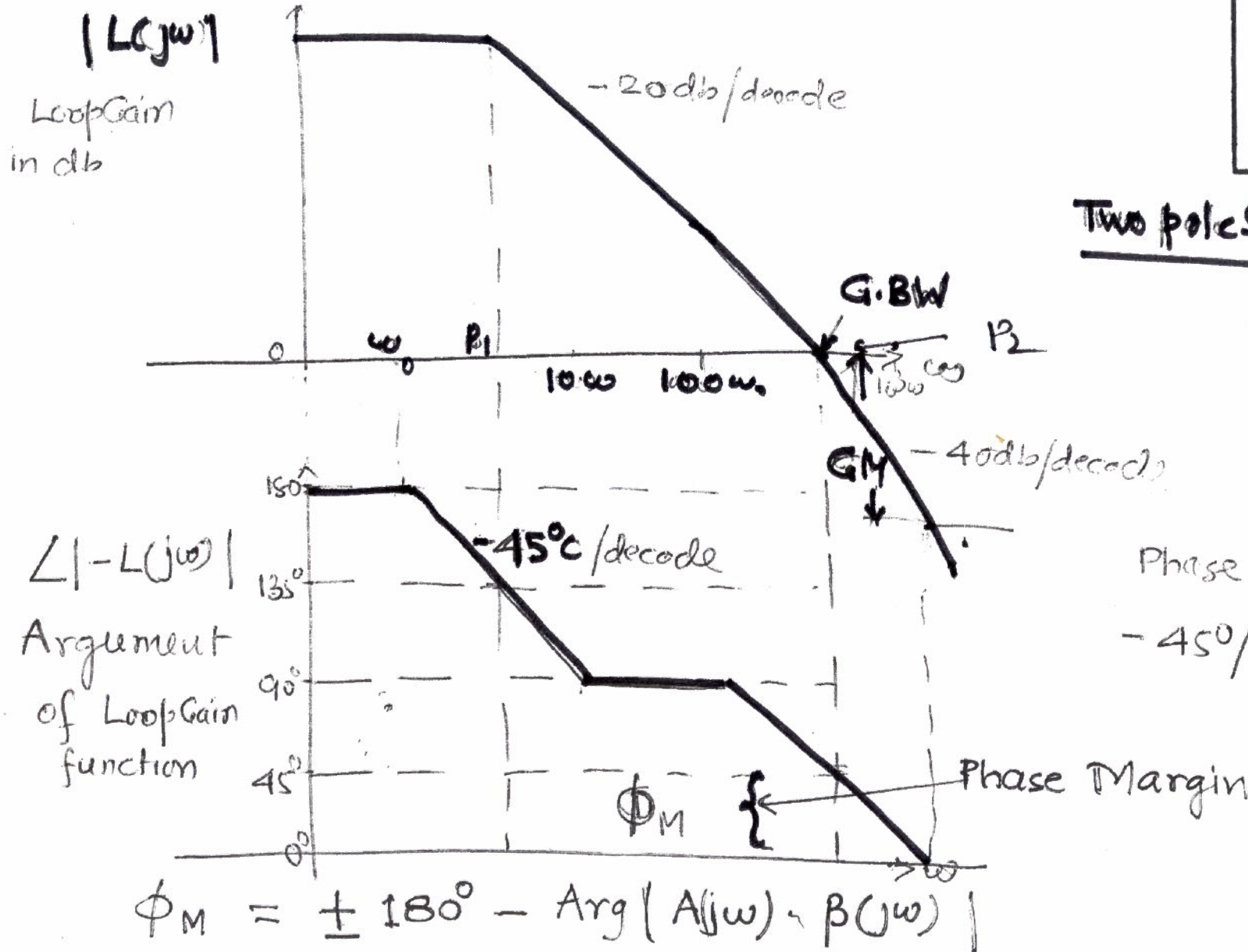

Stability looking from open-loop Bode plot
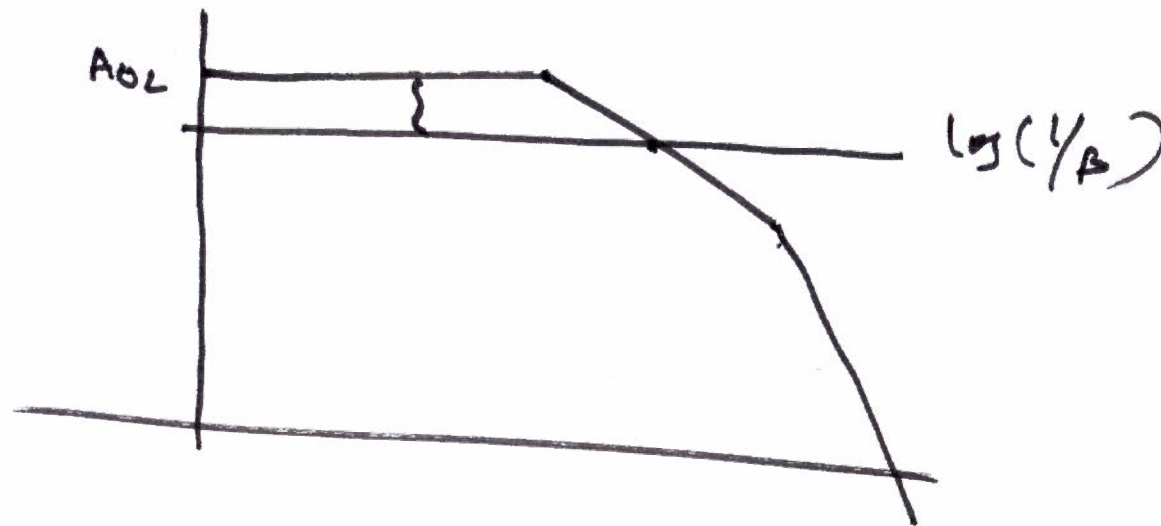
$$\log(A\beta) = \log A - \log(1/\beta)$$



CDEEP
IIT Bombay