



CDEEP
IIT Bombay

EE 618 L 22 / Slide 01

OTA Applications

OTA use in Realisation of Active Filters
Continuous (Analog) Filters are mostly
used in cases which have lower cut-off.

For example a RC filter is a passive continuous filter.

The cut-off frequency is function of RC time constant.

For higher frequency cut-offs, one must get v. small
values of R and C. R realisation on silicon has limits

of getting extreme value of R (larger & v. smaller).

Thus frequency response of filters are limited

bandwidths one.


On silicon an Active filter can satisfy both input-
output relations by realising Resistors by $1/q_m$ values.



Such filters are also called g_m -C continuous filters.

OTA is a device, whose output could be controlled 'transconductance'.

Take an OTA as shown

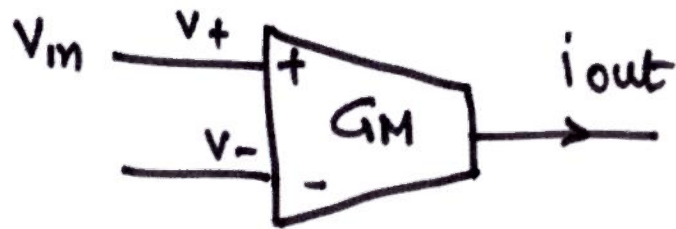

$$i_{out} = G_M \cdot (V_+ - V_-)$$

If we put $V_- = 0$

$$\text{Then } i_{out} = G_M \cdot V_{in}$$




CDEEP
IIT Bombay

EE 618 L 22 / Slide 03



CDEEP
IIT Bombay


EE 618 L 22 / Slide 04

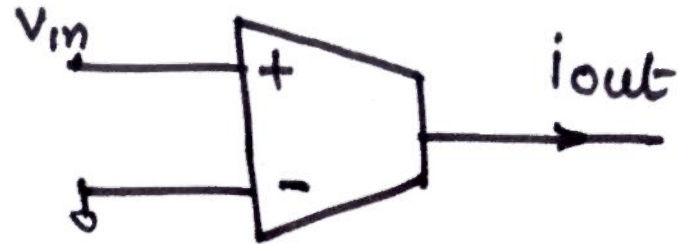

$$G_m = g_{m1}$$


Unloaded

$$i_{out} = g_{m1} V_{in}$$

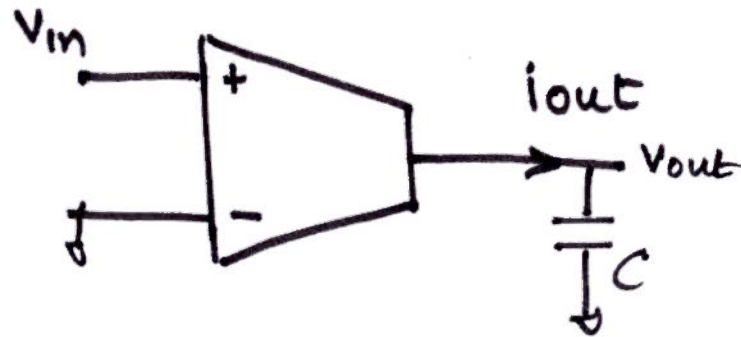

Loaded

$$V_{out} = i_{out} / j\omega C$$

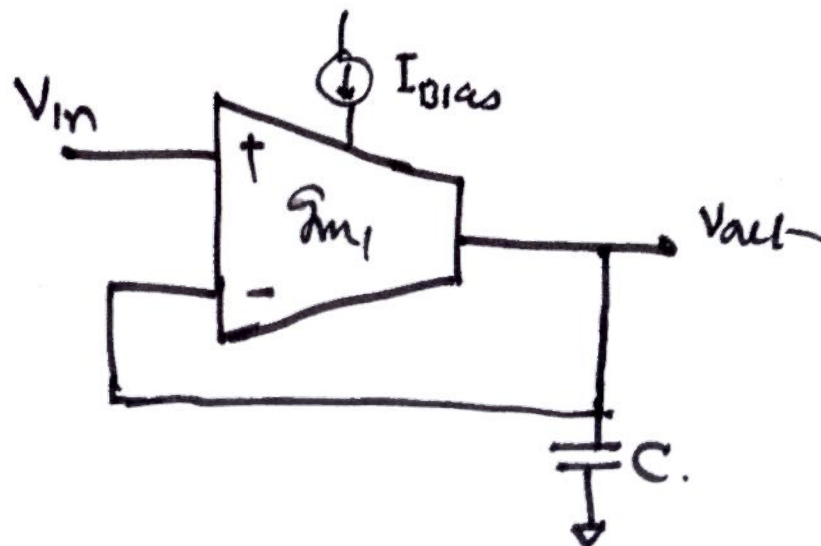

Loaded with -ve
Feedback