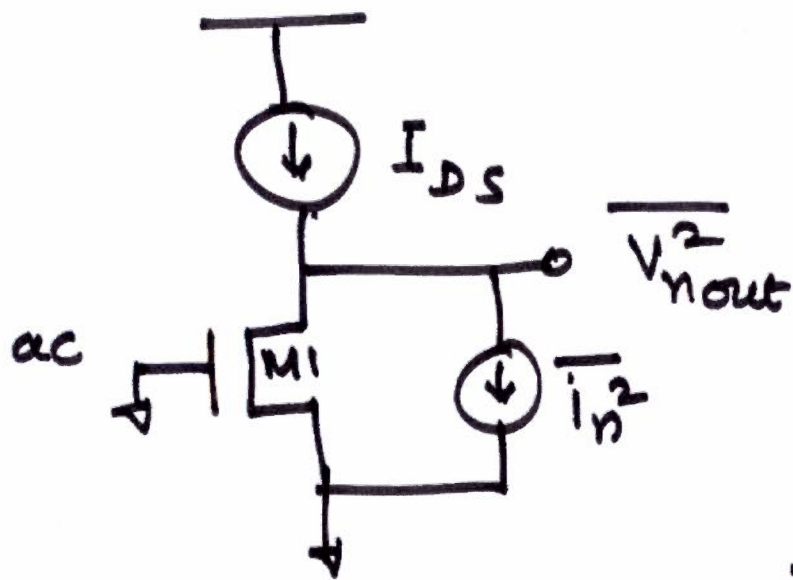




CDEEP
IIT Bombay

A simple CS Amplifier noise can be now evaluated.



If R_{out} is output resistance of $M1$ (r_{o1})
 & Current source has $R_{out} \rightarrow \infty$
 then Noise current $\sqrt{i_n^2}$ flows through r_{o1} output resistance

$$\therefore \overline{V_{nout}^2} = \overline{i_n^2} \cdot r_{o1}^2$$

$$= 4kT \left(\frac{2}{3} g_m \right) r_{o1}^2$$

$$\text{or } \sqrt{\overline{V_{nout}^2}} = \sqrt{\frac{8}{3} kT g_m} \cdot r_{o1} \quad V/\sqrt{Hz}$$

\therefore Low Noise \Rightarrow low g_m , (Lower Gains)

1/f Noise

- Famously known as Flicker Noise.
- Most Believe that this Noise is due to random carrier trapping at Interface States (Insulator / Semiconductor Interface) in MOS device.
- It is difficult to accurately predict the Noise Power due to 1/f Noise , as 'Interface' property is strongly dependent on Process Technology.
- This noise power is seen to follow 1/f relation with frequency.



CDEEP
IIT Bombay

EE 618 L 25 / Slide 01



CDEEP
IIT Bombay

EE 618 L 25 / Slide 02

- In general one models this noise by Noise Voltage source in series to Gate terminal.

- Typically it can be represented as

$$\overline{V_{n1/f}^2} = \frac{K}{C_{ox} W \cdot L} \cdot \frac{1}{f}$$
$$\Delta \quad \overline{i_{n1/f}^2} = \frac{K}{C_{ox} W \cdot L} \cdot g_m^2 \cdot \frac{1}{f}$$

- The spectral density of Flicker Noise current source is given by

$$\overline{i_{n1/f}^2} = \int_{f_1}^{f_2} \frac{K_1}{L^2} \cdot \frac{I_{DS}}{C_{ox}} \frac{df}{f}$$

$$\overline{i_{n,1/f}^2} = \frac{K_1}{L^2} \frac{I_{DS}}{C_{OX}} \ln(f_2/f_1)$$

$$\overline{i_{n,1/f}^2} = \frac{K_2}{L^2} \frac{I_{DS}}{C_{OX}} \log(f_2/f_1)$$

We also know that Thermal Noise ~~voltage~~ ^{current} in a frequency band can be written as

$$\overline{i_{n,th}^2} = 4KT \left(\frac{2}{3} g_m \right)$$

At a frequency f_c called $1/f$ Noise corner frequency

the two noise voltages are equal

$$\text{or } 4KT \left(\frac{2}{3} g_m \right) = \frac{K}{C_{OX} W \cdot L} \cdot \frac{1}{f_c} g_m^2$$

$$\text{or } f_c = \frac{K g_m}{C_{OX} W \cdot L} \cdot \frac{3}{8 kT}$$



CDEEP
IIT Bombay

EE 618 L 25 / Slide 03.