

OSCILLATORS


$$A_{CL}(s) = \frac{H(s)}{1 + H(s)}$$

Unity Gain
Feedback

If $s = j\omega_0$ and $H(j\omega_0) = -1$

then $A_{CL}(j\omega_0) = \infty$ at $\omega = \omega_0$

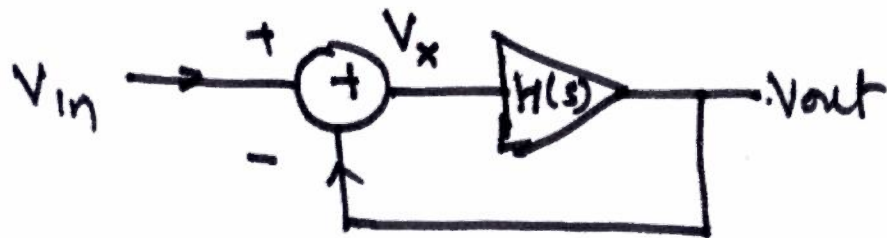This condn is essentially condition for oscillations.



Negative
A typical feedback
system is shown
here. Here

$$V_x = V_{out} + |H(j\omega_0)|V_{out} + |H(j\omega_0)|^2 V_{out} + \dots$$

(Geometric series)



CDEEP
IIT Bombay

EE 618 L 27 / Slide 07

If $|H(j\omega_0)| > 1$, then V_x is having a Diverging Series.

while $|H(j\omega_0)| < 1$, then V_x has converging series representation, and its magnitude is finite.

We write

$$V_x = \frac{V_{out}}{1 - |H(j\omega_0)|} = \text{finite} \left\{ \text{if } |H(j\omega_0)| < 1 \right\}$$

Barkhausen Criteria :

In a Negative feedback System, if

Two conditions \rightarrow $|H(j\omega_0)| \geq 1$
 $\angle H(j\omega_0) = 180^\circ$ are satisfied

then the system will Oscillate



CDEEP
IIT Bombay

EE 618 L 27 / Slide 02




CDEEP
IIT Bombay

EE 618 L 27 / Slide 03

Ring Oscillator

1.

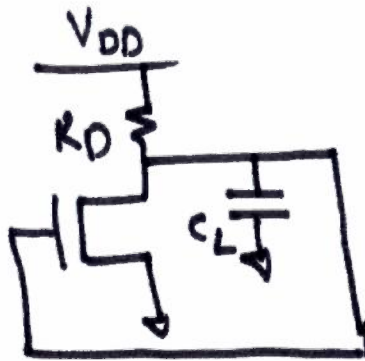


$$\text{pole } p_1 = \frac{1}{R_D C_L}$$

Phase shift at pole is 45°
& total Phase shift is 90° ,
plus 180° from Transistor = 270°

Hence Loop does not sustain oscillation.


2.

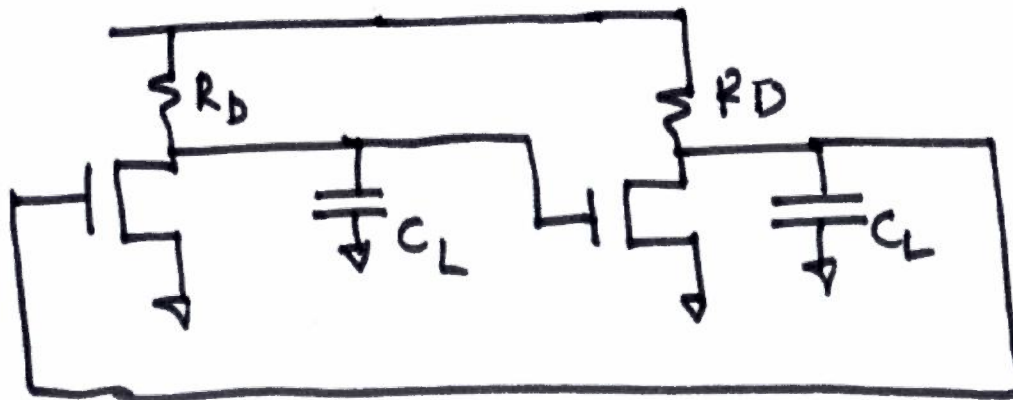

2 poles will give
total phase shift of
 $180^\circ + 180^\circ = 360^\circ$. This
satisfies Oscillation Condⁿ!
However one does not
observe Oscillations here.

The Feedback satisfies Barkhausen Criterion only at
 $\omega_0 = 0$. The circuit therefore exhibits Latch Action.

3.

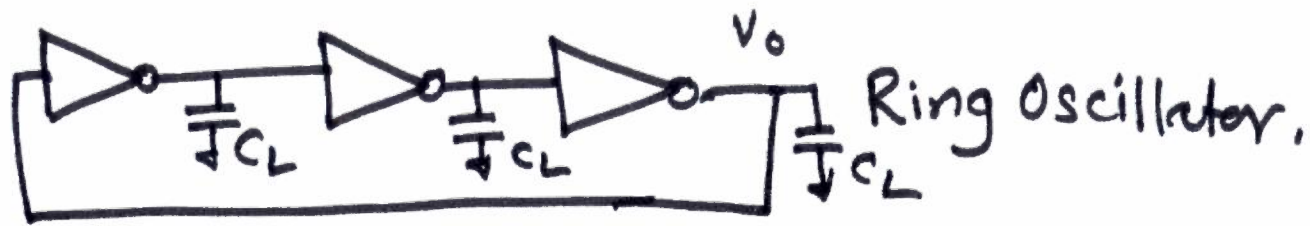

$\omega_0 = \frac{1}{R_D C_L}$ and transfer function show
Triple pole at ω_0 .

$$\text{or } H(s) = \frac{-A_{V0}^2}{\left[1 + \left(\frac{s}{\omega_0}\right)\right]^3}$$

We can see that for Oscillation to sustain,

$$A_{V0} = 2 \quad \text{and} \quad \omega_{osc} = \sqrt{3} \omega_0$$

It means that each stage must contribute 60° from one RC combination



CDEEP
IIT Bombay

EE 618 L 27 / Slide 04