
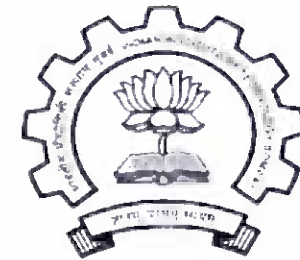


Slide No: 1


OPAMP as Circuit Element

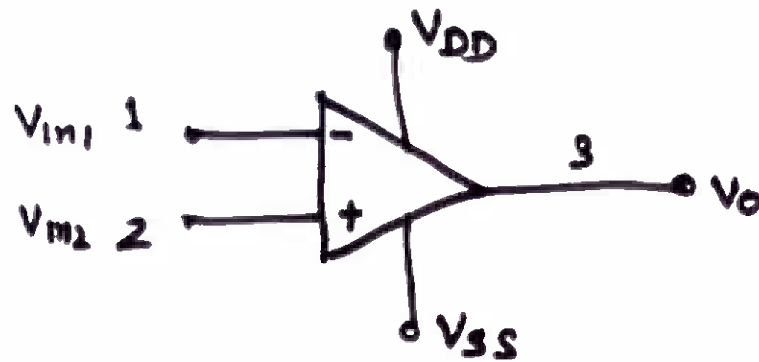

CDEEP
IIT Bombay




Equivalent Circuit

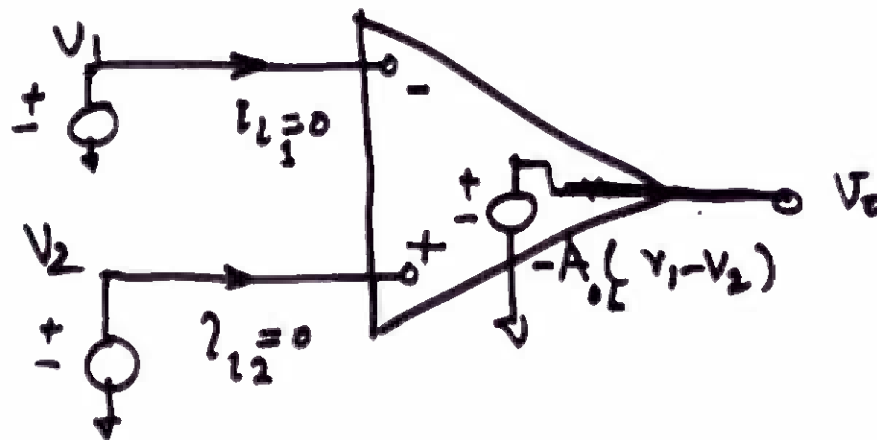


Slide No: 2

Inverting & Non Inverting Amplifier

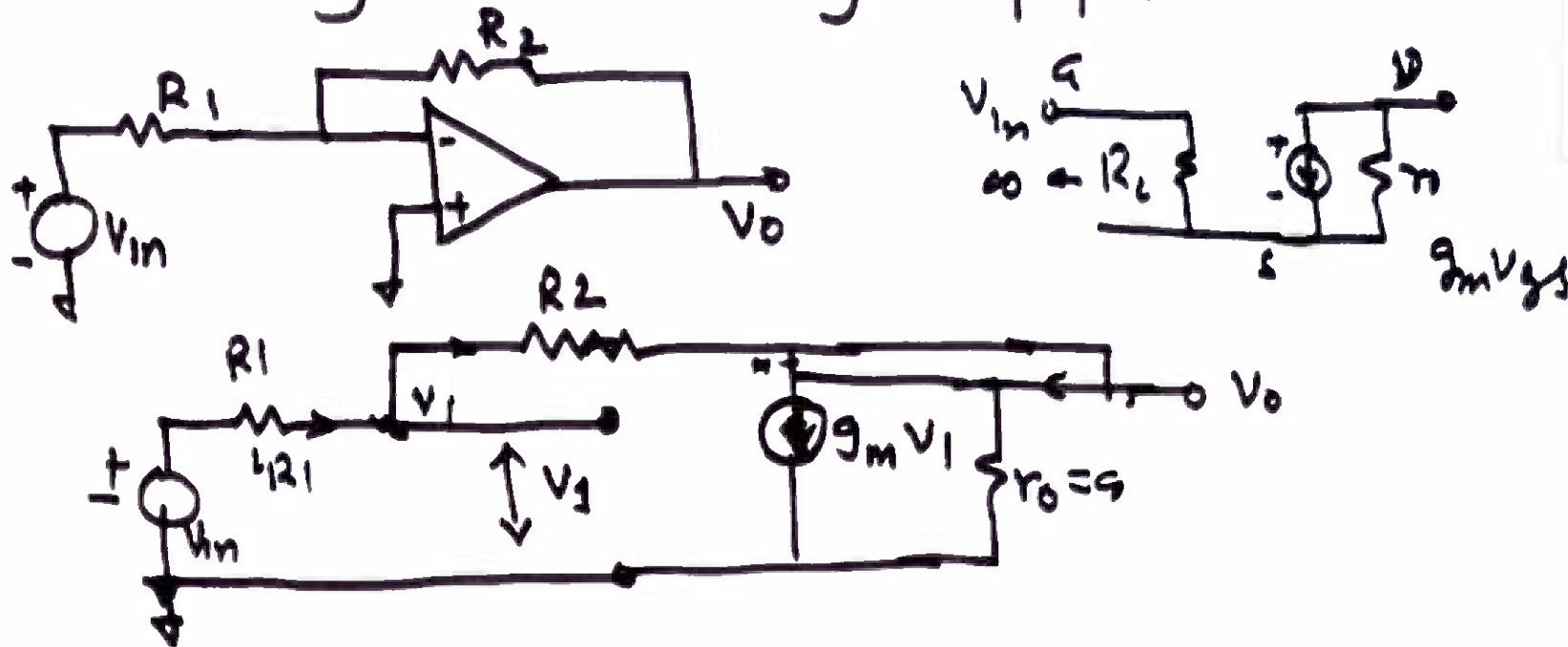
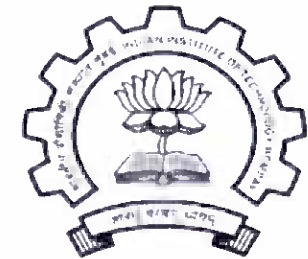
$$\frac{V_{in} - V_1}{R_1} = \frac{V_1 - V_0}{R_2} \quad \text{or} \quad \frac{V_{in}}{R_1} + \frac{V_0}{R_2} = \underline{V_1} \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$




CDEEP
IIT Bombay

Ideal Parameters


$$R_i \rightarrow \infty$$

$$r_o \rightarrow 0$$

A_v is very large

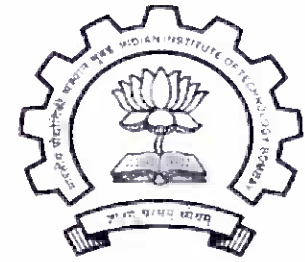

CDEEP
IIT Bombay

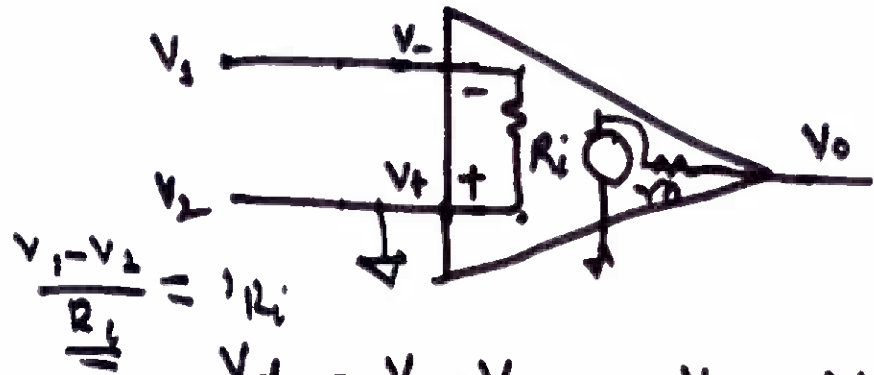

$$V_d = V_1 - V_2 = V_- - V_+$$

$$V_o = -A_v (V_- - V_+) = -A_v V_d$$

$$\text{or } V_d = -\frac{V_o}{A_v} \quad \text{If } A_v \rightarrow \infty \quad V_d \rightarrow 0$$

$$\boxed{\text{Then } V_- = V_+}$$


Hence if we Ground $V_+ \Rightarrow 0$

$$\text{Then } V_- = 0$$

This is Concept of Virtual Ground.

Slide No: 4

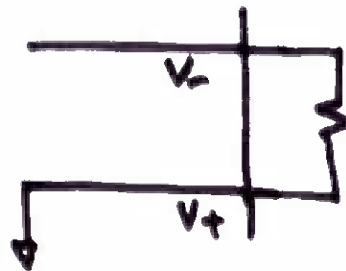Alternatively as $R_i \rightarrow \infty$, no current passes through it



As $I_i = 0$


$\therefore V_- = V_+ = 0$

V_- getting 'Zero' potential.. This is called Virtual Ground.




CDEEP
IIT Bombay

Slide No: 5

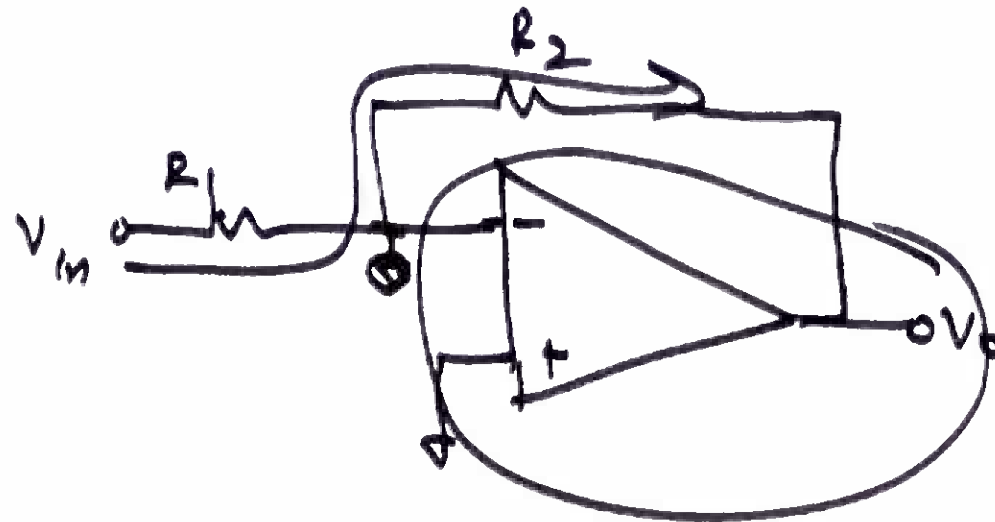


$$V_o = -\frac{R_2}{R_1} V_{in}$$

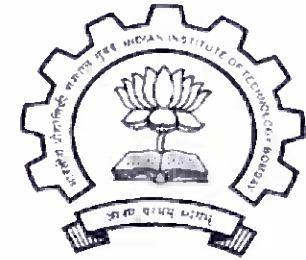

CDEEP
IIT Bombay

Amplifier with T-network in Feedback

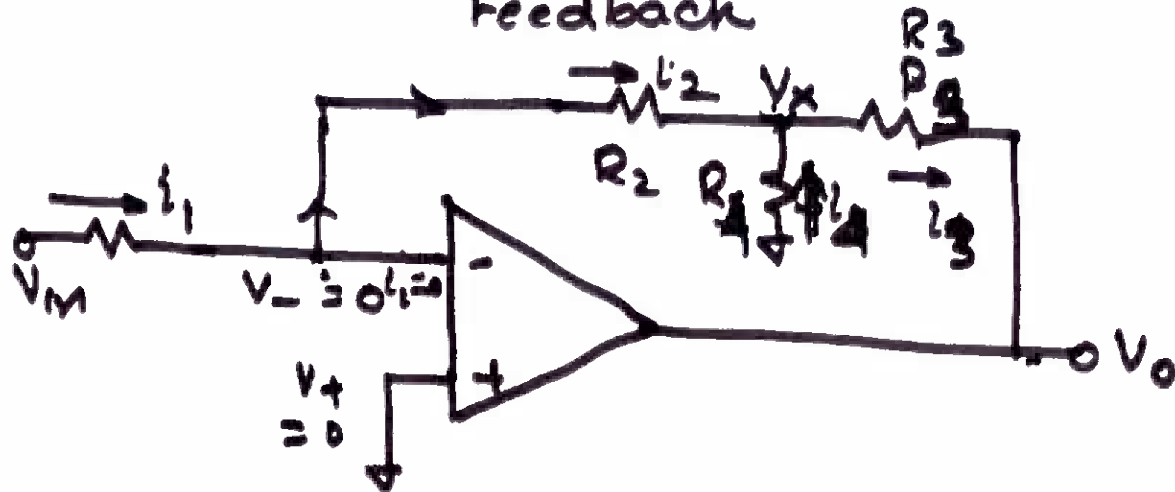


$i_1 = i_2$ as $V_- = 0$
 (V_A)
 No current enters
 OPAMP inputs.

$$V_x = 0 - i_2 R_2 = -i_1 R_2 = -\frac{V_{in}}{R_1} \cdot R_2$$

At node V_x $i_2 + i_4 = i_3$
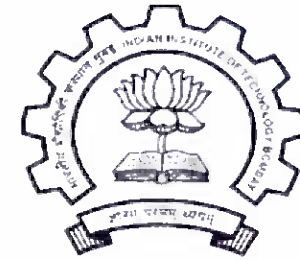
$$-\frac{V_x}{R_2} - \frac{V_x}{R_4} = \frac{V_x - V_O}{R_3} \quad \text{or} \quad V_x \left[\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right] = \frac{V_O}{R_3}$$



Slide No: 7

$$\approx -\frac{V_{in}}{R_1} R_2 \left[\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right] = \frac{V_o}{R_3}$$

$$\approx \frac{V_o}{V_{in}} = A_v = -\frac{R_2}{R_1} \left[1 + \frac{R_3}{R_4} + \frac{R_3}{R_2} \right]$$

Why T-Network ?


Larger Gain with . . .
values of Resistors.



CDEEP
IIT Bombay

Slide No: 8

NonInverting Amplifier

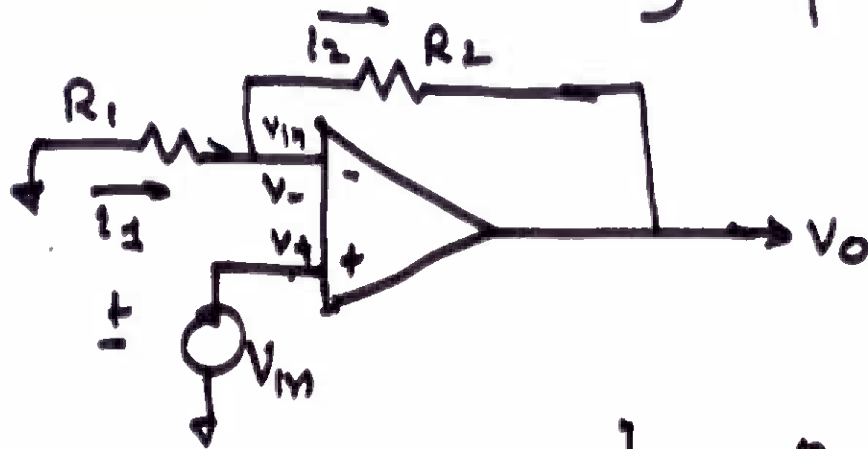

Assumption :


$R_1 \rightarrow \infty \therefore$ no current enters
OPAMP inputs. $\therefore V_- = V_+$

$$i_1 = \frac{0 - V_-}{R_1} = -\frac{V_-}{R_1} = -\frac{V_+}{R_1} = -\frac{V_{in}}{R_1}$$

Then $i_2 = \frac{V_- - V_o}{R_2} = \frac{V_{in} - V_o}{R_2}$



But $i_1 = i_2$
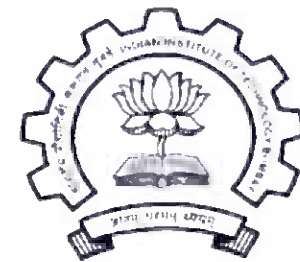
$$\therefore \frac{V_{in} - V_o}{R_2} = -\frac{V_{in}}{R_1} \quad \therefore \frac{V_o}{V_{in}} = \left(1 + \frac{R_2}{R_1}\right)$$



CDEEP
IIT Bombay

Interesting Circuit

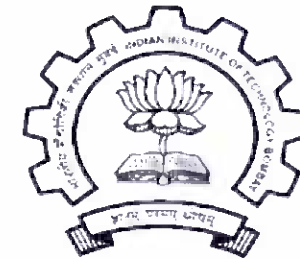
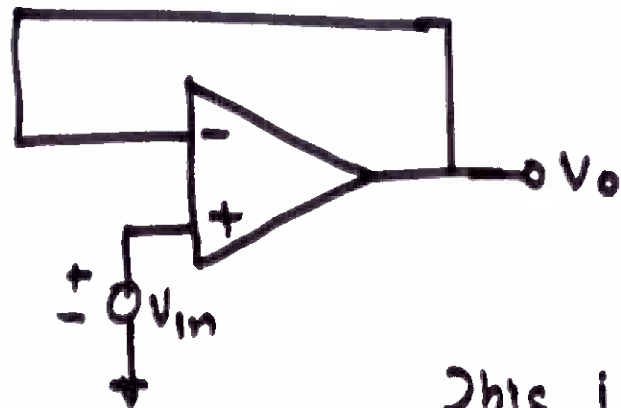
CDEEP
IIT Bombay

$$\text{Here } V_o = V_- = V_+$$

$$\text{or } V_o = V_{in}$$

$$\therefore A_v = \frac{V_o}{V_{in}} = 1$$

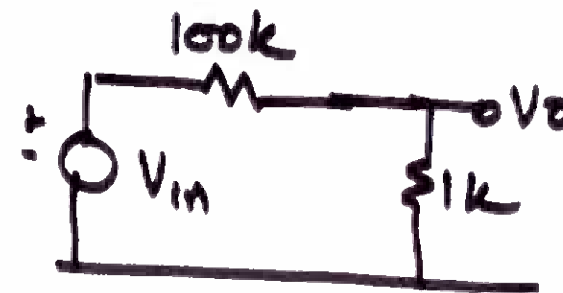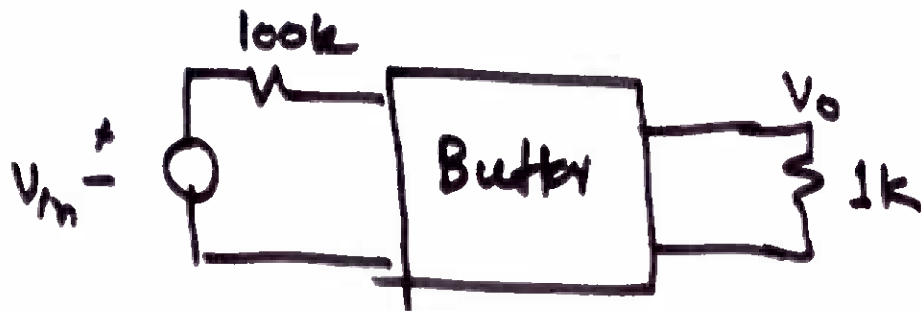
This is called Voltage Follower or Buffer



$$\frac{V_o}{V_{in}} = \frac{1k}{101k} = 0.01$$


Severe Loading

Slide No: 10

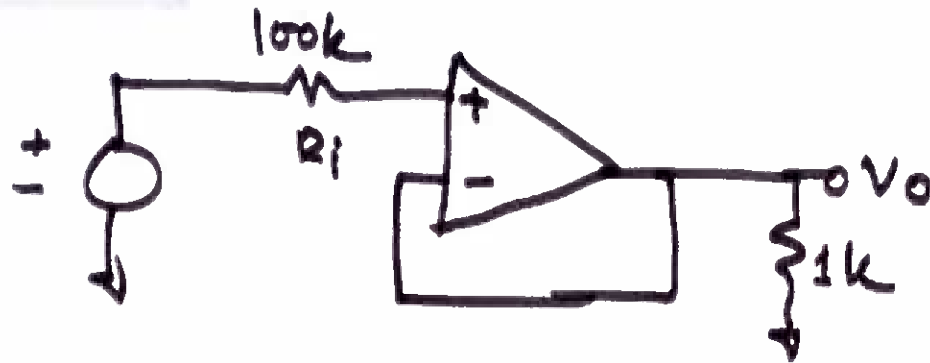

$$R_o \gg 100k \quad \therefore V_o \approx V_{in}$$

(ii) I-V Converter

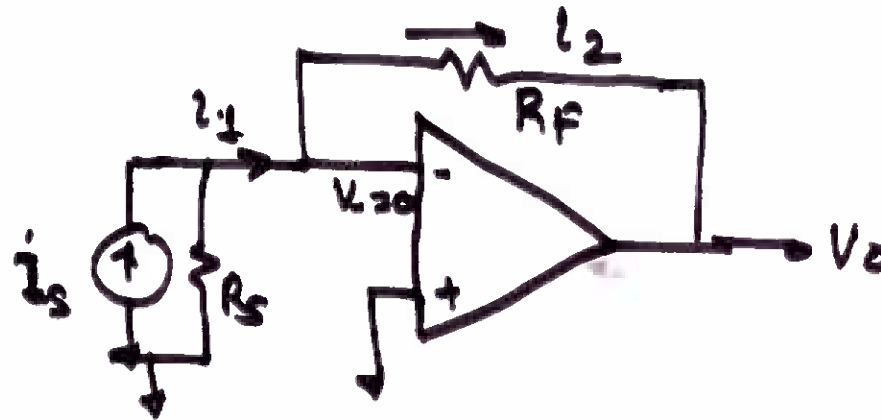

$$i_1 = i_2 = i_s$$

$$\text{But } i_2 = \frac{0 - V_o}{R_f}$$


$$\therefore V_o = -i_2 R_f = -i_s R_f$$




CDEEP
IIT Bombay

V-I Converter

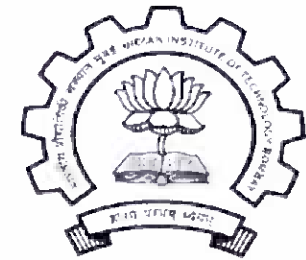Requirement: I in Load should be independent of Load Value.



CDEEP
IIT Bombay

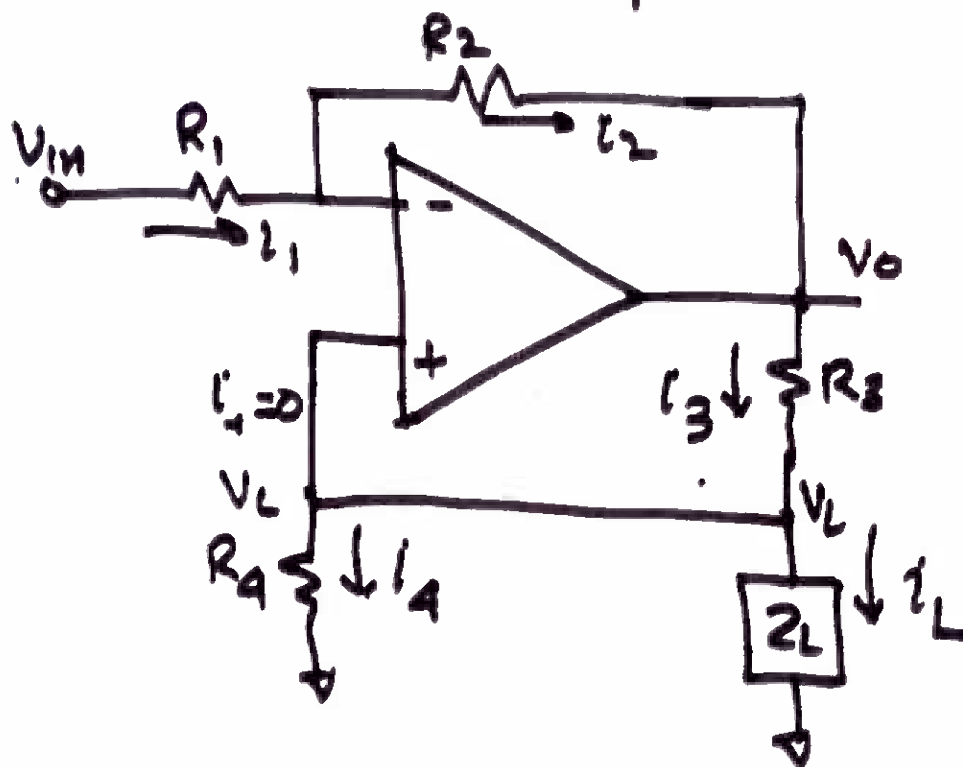

Clearly $V_- = V_+ = V_L \neq 0$

$$\therefore V_- = V_+ = i_L Z_L = V_L$$

Also $i_1 = i_2$

(No current enters)
inputs

Slide No: 12

$$\sim \frac{R_2}{R_1} \cdot \left(i_L z_L - V_{in} \right) = i_L + \frac{i_L z_L}{R_4}$$


$$i_L \left[\frac{R_2}{R_1} z_L - 1 - \frac{z_L}{R_4} \right] = V_{in} \frac{R_2}{R_1 R_3}$$

for i_L to be independent of z_L

$$\frac{R_2}{R_1 R_3} = \frac{1}{R_4}$$


Then

$$i_L = - \frac{1}{R_4} \cdot V_{in}$$

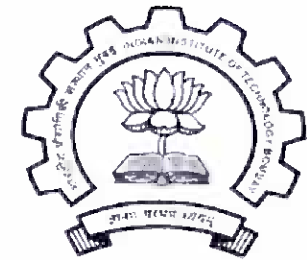


CDEEP
IIT Bombay


OPAMP Differentiator & Integrator

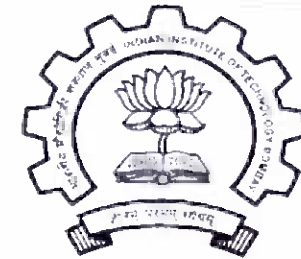

CDEEP
IIT Bombay

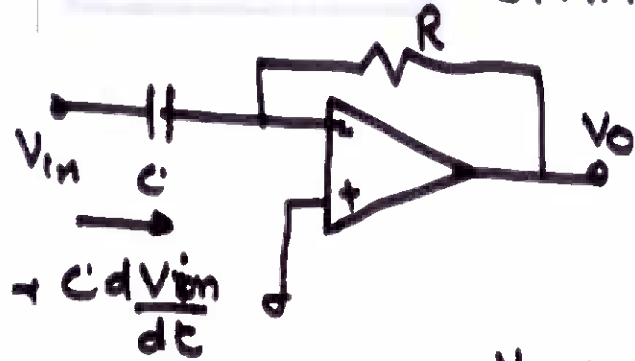

$$V_o(t) = -RC \frac{dV_{in}}{dt}$$

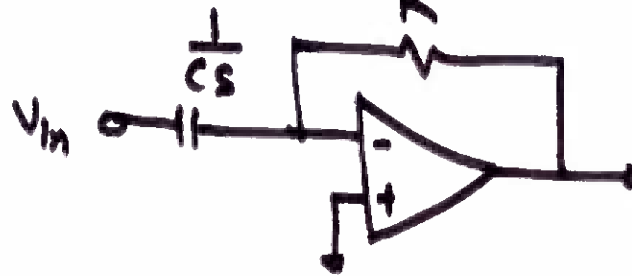

$$\frac{V_{in} - 0}{1/Cs} = \frac{0 - V_o}{R}$$

or $V_o = -RCs V_{in}$

$$\frac{V_o(s)}{V_{in}(s)} = RCs = -j\omega RC$$


$$\left| \frac{V_o(s)}{V_{in}(s)} \right| = \omega RC$$

$$\phi = \tan^{-1} \frac{\omega RC}{0} = -\tan^{-1} \infty = -\pi/2$$

$$H(s) = \frac{V_o(s)}{V_{in}(s)} = RC \cdot s$$



$RC \Rightarrow$ Time constant

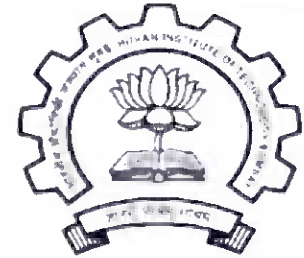

$$\therefore \frac{V_{in} - V_L}{R_1} = \frac{V_L - V_0}{R_2}$$

$$\text{or } \frac{V_{in} - i_L Z_L}{R_1} = \frac{i_L Z_L - V_0}{R_2} \quad - (1)$$


$$i_3 = \frac{V_0 - V_L}{R_3} = \frac{V_0 - i_L Z_L}{R_3} \quad - (2)$$

$$\text{But } i_3 = i_L + i_4$$

$$\text{But } i_4 = \frac{i_L Z_L}{R_4}$$

$$\therefore \frac{V_0 - i_L Z_L}{R_3} = i_L + \frac{i_L Z_L}{R_4} \quad - (3)$$

Slide No. 15

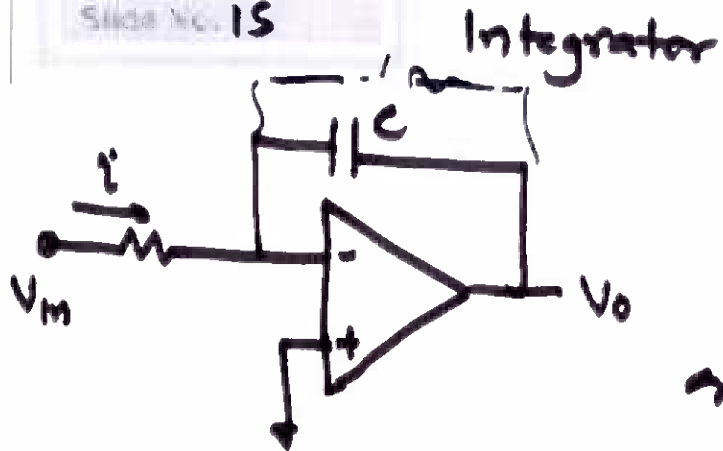



$$\frac{V_{in}}{R} = -C \frac{dV_o}{dt}$$

$$\Rightarrow V_o = -\left[\frac{1}{RC} \int V_{in} dt + V_{co} \right]$$

$$\frac{V_o(s)}{V_{in}(s)} = -\frac{1}{sRC} = -\frac{1}{j\omega RC}$$

$$\left| \frac{V_o}{V_{in}} \right| = \frac{1}{\omega RC}$$

$$\& \phi = +90^\circ$$

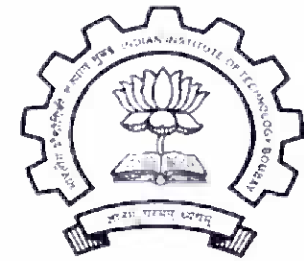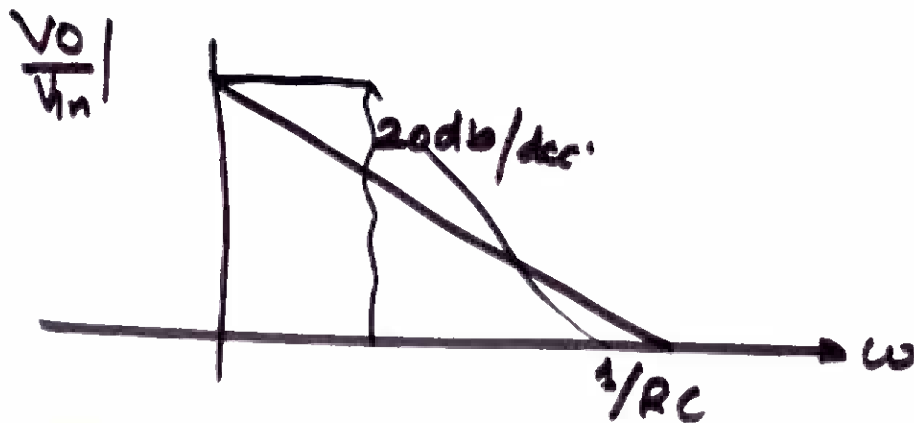


CDEEP
IIT Bombay


Precision Half Wave Rectifier



CDEEP
IIT Bombay

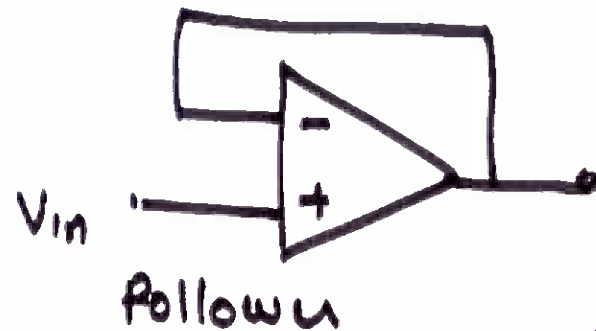

Modified V. Follower
Circuit

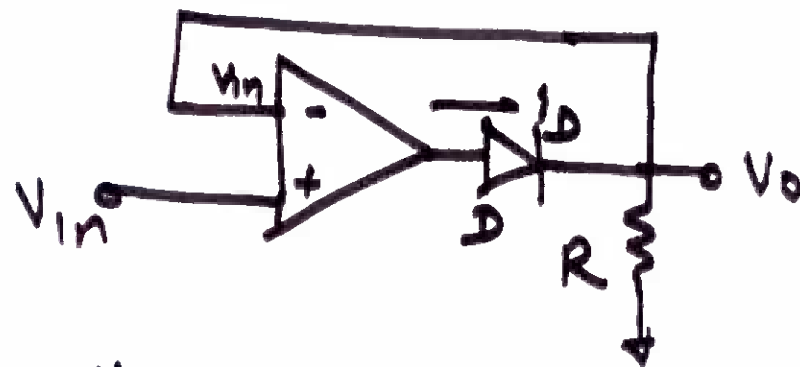

Diode current $I = I_s \left(e^{\frac{qV_f}{\eta kT}} - 1 \right) \approx I_s e^{\frac{qV_f}{\eta kT}}$

$$\therefore \log I = \log I_s + \frac{qV_f}{\eta kT}$$

$$\therefore V_f = \frac{\eta(kT)}{q} \left[\log I - \log I_s \right]$$


$V_m = + \text{tive}$

$V_{+} = V_{in} = V_{-}$

Slide No:

12

Logarithmic Amplifier

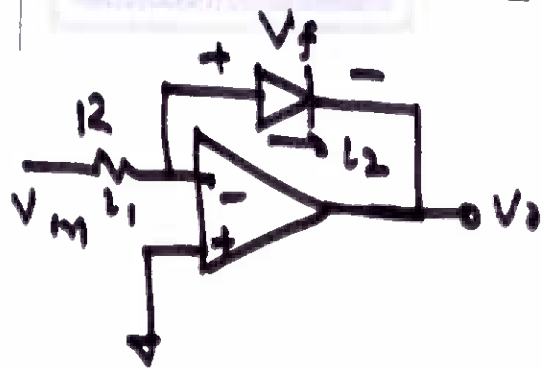

$$i_1 = \frac{V_{in}}{R} = i_2 = i_D$$

If $i_D = 0$ then $i_1 = 0$
then $V_0 = 0$


But if Diode conducts ($V_- > V_0$)

Then $V_f + V_0 = 0$ or $V_0 = -V_f = -\frac{\eta kT}{q} [\log i_2 - \log I_s]$

$$\therefore V_0 = -\frac{\eta kT}{q} [\log V_{in} - \log R - \log I_s]$$

$$V_0 = -\frac{\eta kT}{q} \left[\log \frac{V_{in}}{R I_s} \right]$$

$$\therefore V_0 \propto \log(V_{in})$$

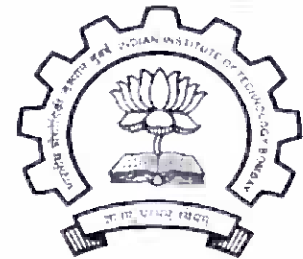


CDEEP
IIT Bombay

Slide No: 18

Antilog Amplifier

Basic amplifier

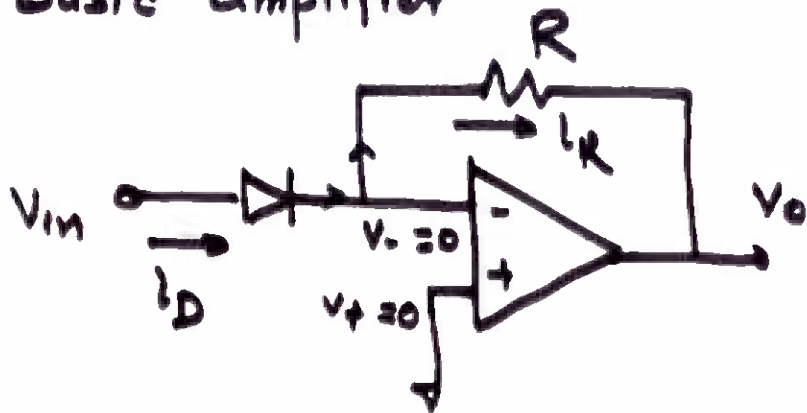


We have

$$i_D = I_S \exp\left(\frac{qV_f}{\eta kT}\right)$$

As $v_+ = 0$, Hence $i_R \cdot R = -v_0 = + i_D \cdot R$
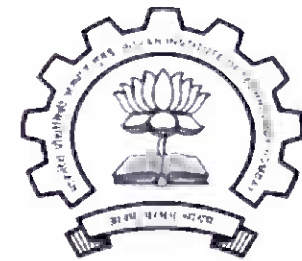
$$\therefore v_0 = -I_S R \exp\left(\frac{qV_f}{\eta kT}\right) \quad \therefore v_0 \propto \exp(V_f)$$



CDEEP
IIT Bombay


Analog Multiplier

Mathematically $\log(AB) = \log A + \log B$

$$\begin{aligned} \text{Also } AB &= \text{Antilog}(AB) \\ &= \text{Antilog}[\log A + \log B] \end{aligned}$$


Clearly we can get Multiplication of AB by using three amplifier and an Adder.

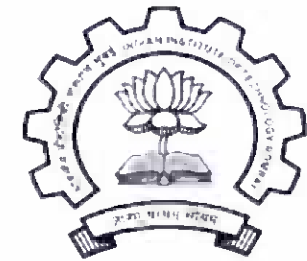- ① Create $\log A$
- ② Create $\log B$
- ③ Create $(\log A + \log B)$
- ④ Create Antilog of $[\log A + \log B]$



Slide No. 20

We want Multiplication of V_1 & V_2

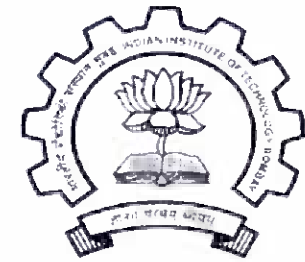

CDEEP
IIT Bombay

