

Bipolar Transistor Models

$$I_E = I_B + I_C \quad (\text{Universal}) \quad - (1)$$

$$I_C = \alpha I_E \quad \alpha = \alpha_T \gamma \quad - (2)$$


$$\frac{I_C}{I_B} = \beta \quad \therefore \beta = \frac{\alpha}{1-\alpha} \quad - (3)$$

β is called Forward Current Gain

$$I_C = \alpha I_E + I_{CO} \quad - (4)$$

$$I_{CO} = I_{CS} (1 - \alpha_F \alpha_R) \quad - (5)$$

$$V_{CE} = V_{BE} + V_{BC} \quad - (6)$$

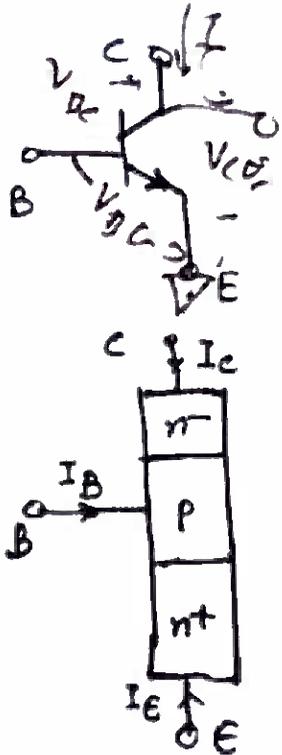


Small-Signal Model of BJT

$$I_b = i_b + I_B$$

Total = Small Signal + DC

$$I_c = i_c + I_C$$

$$v_{BE} = V_{BE} + v_{be}$$


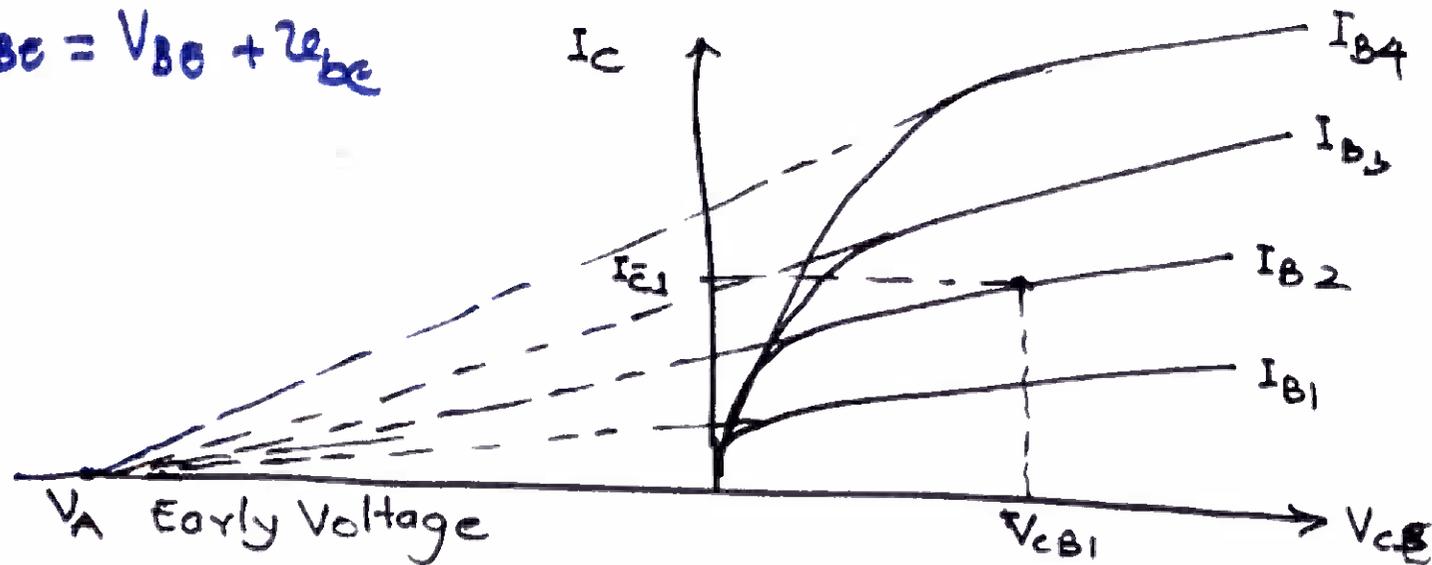


CDEEP
IIT Bombay

Slide No: 5-



CDEEP
IIT Bombay

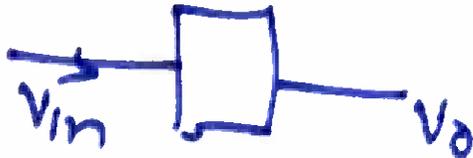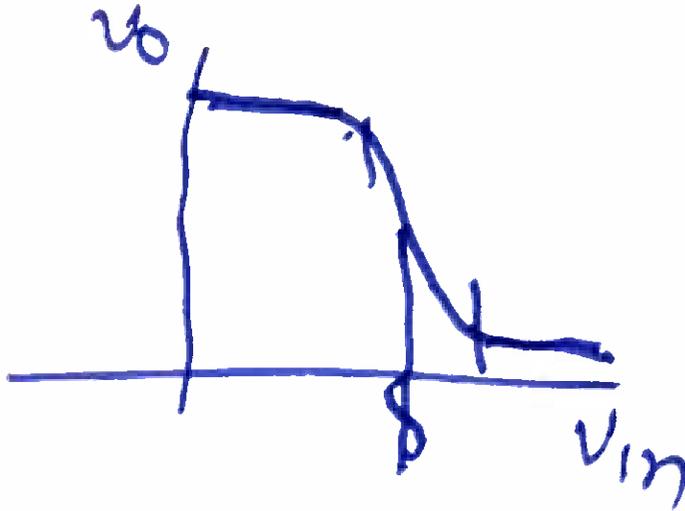

Course Name

Analog Circuits

Lecture No.

Instructor's Name

Prof. A. N. Chandorkar

Slide No: 6

Small Signal Model (cont.)

Most important parameter of Transistor is

Transconductance $g_m = \frac{\partial I_c}{\partial V_{BE}}$ — ①

($I_c = I_s \exp(V_{BE}/V_T)$)

We have

$$\Delta I_c = \frac{dI_c}{dV_{BE}} \cdot \Delta V_{BE}$$

OR


$$\Delta I_c = g_m \Delta V_{BE}$$

i.e.

$$i_c = g_m v_{be}$$

$$\frac{v_o}{v_{be}} = -\beta_0 \frac{R_L}{R_i}$$

$$r_b \cdot R_i = v_{be}$$

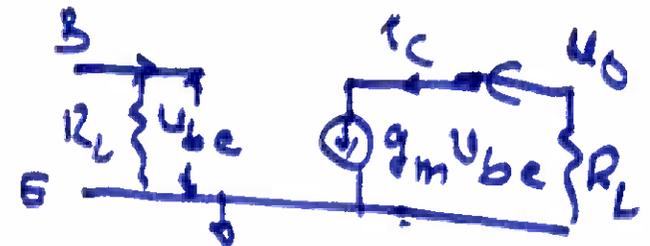

② $v_o = -i_c R_L$
 $v_o = -\beta_0 i_b R_L$



CDEEP
IIT Bombay

Course Name

Analog Circuits

Lecture No.

Instructor's Name

Prof. A. N. Chandorkar

We have $I_C = I_S \exp(V_{BE}/V_T)$

$$\therefore g_m = \frac{d}{dV_{BE}} [I_S \exp(V_{BE}/V_T)]$$

$$= \frac{I_S}{V_T} \exp(V_{BE}/V_T) = \frac{I_C}{V_T} = \frac{I_C}{(kT/q)} = \frac{qI_C}{kT}$$

$$\therefore g_m = \frac{qI_C}{kT} \quad \text{--- (3)}$$

Typically at 27°C (Room Temp.) $\frac{kT}{q} \approx 26 \text{ mV}$


\therefore at $I_C = 1 \text{ mA}$ (say)

$$g_m \approx 38 \text{ mA/V}$$





Example of CE Amplifier

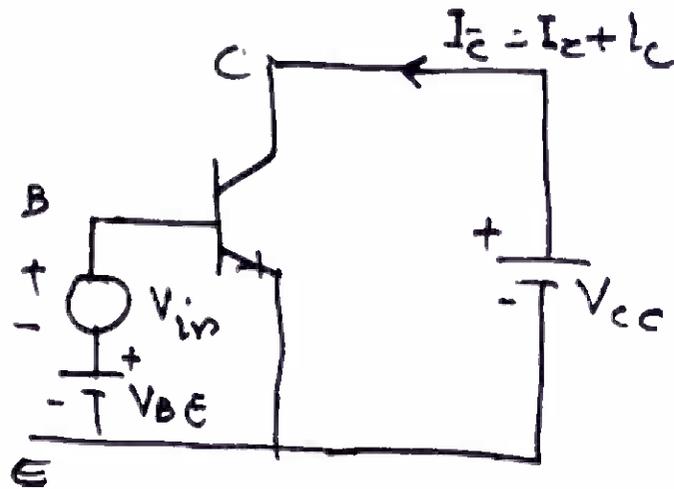

$$I_e = I_s \exp\left[\frac{V_{BE} + V_{in}}{V_T}\right] \quad \text{Total}$$

$$I_c = I_s \exp\left[\frac{V_{BE}}{V_T}\right] \quad \text{DC}$$

$$\therefore I_e = I_c \exp(V_{in}/V_T)$$

If $V_{in} < V_T$

$$I_e = I_c \left[1 + \frac{V_{in}}{V_T} + \frac{1}{2} \left(\frac{V_{in}}{V_T}\right)^2 + \frac{1}{6} \left(\frac{V_{in}}{V_T}\right)^3 + \dots \right]$$

$$\text{As } i_c = I_e - I_c$$

Slide No: 9

$$\text{Hence } i_c = \frac{I_c}{V_T} v_{in} + \frac{1}{2} \frac{I_c}{V_T^2} v_{in}^2 + \frac{1}{6} \frac{I_c}{V_T^3} v_{in}^3 \dots$$

If $v_{in} \ll V_T$ Then Higher Order terms are negligible

$$\therefore i_c = \frac{I_c}{V_T} \cdot v_{in} \quad \& \quad \text{then } g_m = \frac{i_c}{v_{in}} = \frac{I_c}{V_T} = \frac{2I_c}{kT}$$

Hence for Small Signal operation

$$v_{in} \ll 26 \text{ mV}$$



CDEEP
IIT Bombay

Course Name

Analog Circuits

Lecture No.

Instructor's Name

Prof. A. N. Chandorkar

BJT Model (cont.): CapacitanceCDEEP
IIT Bombay

If a small signal voltage v_{in} is applied over dc value V_{BE} , then we say

$$\Delta V_{BE} = v_{in} \quad \Delta Q_e = q_e$$

and $\Delta Q_b = q_b$

Then small signal (ac) capacitance across BE jn is given by

$$C_{be} = \frac{q_b}{v_{in}}$$

from Transistor theory, we know minority charge in Base is

$$Q_e = I_c \tau_B \quad \text{where } \tau_B \text{ is called Base Transit time}$$

$$\text{or } \Delta Q_e = \tau_B \Delta I_c \quad \text{From charge neutrality case } \Delta Q_e = \Delta Q_b$$




$$\therefore \Delta Q_b = \Delta I_c \tau_B$$

$$\therefore q_b = i_c \tau_B \quad (\text{small signal representation})$$

$$\text{Therefore } C_{be} = \frac{i_c \tau_B}{v_{in}} = \left(\frac{i_c}{v_{in}} \right) \tau_B = g_m \tau_B$$
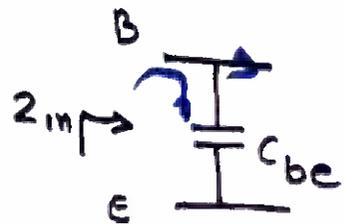
$$C_{be} = C_{\pi}' = \frac{q I_c}{kT} \cdot \tau_B \quad \left(\tau_B = \frac{W_B^2}{2 D_n} \text{ for npn} \right)$$



At lower frequency $Z_{in} = \frac{1}{j\omega C_{be}}$ is large

as C_{be} is normally very small (\ll pf range)

\therefore At low frequency, this shunting capacitance can be neglected.

Input resistance

We have $I_c = \beta I_B$

$$\text{or } I_B = \frac{1}{\beta} I_c$$

$$\text{or } \Delta I_B = \frac{d}{dI_c} \left(\frac{I_c}{\beta} \right) \Delta I_c$$

We define ac β as $\beta_0 = \frac{\Delta I_c}{\Delta I_B} = \frac{i_c}{i_b} = \left[\frac{d}{dI_c} \left(\frac{I_c}{\beta} \right) \right]^{-1}$


β_0 is called Small Signal Current Gain

If β is constant, $\beta_0 = \beta_{DC}$ else β_0 is different from β .

Then, Input Resistance $r_{\pi} = \frac{v_{in}}{i_b} = \frac{v_{in}}{i_c} \cdot \beta_0 = \frac{\beta_0}{g_m}$

$$\therefore \boxed{\beta_0 = g_m r_{\pi}}$$
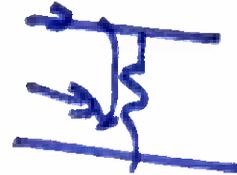
$$\text{or } \frac{i_c}{i_b} = \left(\frac{kT}{qI_c} \right)^{-1} \cdot r_{\pi} = \frac{I_c}{I_B} \therefore \boxed{r_{\pi} = \frac{kT}{qI_B}}$$



CDEEP
IIT Bombay


Output Resistance

We have found earlier

$$\Delta I_c = \frac{\Delta I_c}{\Delta V_{CE}} \Delta V_{CE}$$

$$\Rightarrow \frac{\Delta V_{CE}}{\Delta I_c} = \frac{V_A}{I_c}$$

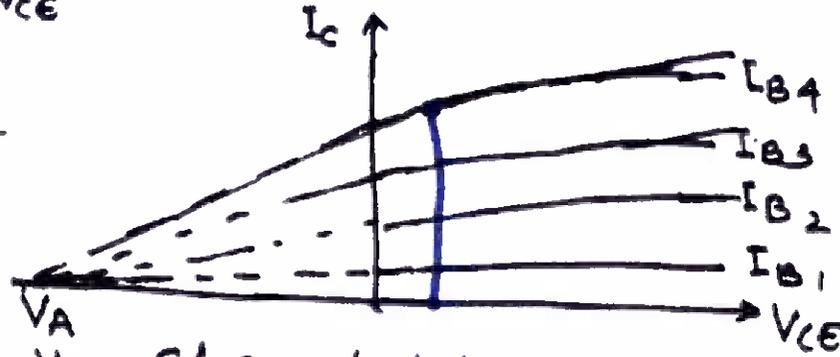
$\frac{\Delta V_{CE}}{\Delta I_c}$ is slope of I_c - V_{CE} characteristics



\therefore Output Resistance $r_o = \frac{\Delta V_{CE}}{\Delta I_c} = \frac{V_{CE}}{i_c} = \frac{V_A}{I_c}$
 where V_A is Early Voltage



CDEEP
IIT Bombay

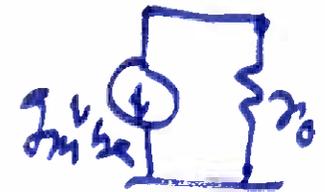

Slide No: 14

We define a parameter η is

$$\begin{aligned}\eta &= \frac{kT}{q} \cdot \frac{1}{V_A} \\ &= \frac{kT}{qI_C} \cdot \frac{I_C}{V_A} = \frac{1}{g_m} \cdot \frac{1}{r_o}\end{aligned}$$

$$\text{or } \boxed{g_m r_o = \frac{1}{\eta}}$$

Typically V_A varies between 50 to 100 Volts
Further at $T=300^{\circ}\text{K}$, $\eta \approx 2.6 \times 10^4$ for above $V_A=100\text{V}$
For operating current of $I_C = 1\text{mA}$, we get $r_o = \frac{100}{10^{-3}} = 100\text{k}\Omega$



CDEEP
IIT Bombay

Course Name:
Analog Circuits

Lecture No.

Instructor's Name:
Prof. A. N. Chandorkar

Slide No: 15

Base-Emitter J^n Capacitance C_{je}

As we did evaluation for C_{μ} , we do the same for C_{je} which is BE J^n capacitance

$$C_{je} = \frac{C_{je0}}{\left(1 - \frac{V_{BE}}{\phi_0}\right)^n} \quad \text{But this is not value which is valid.}$$

BE J^n is FB and hence this formulae is not correct

Typically we take


$$C_{je} = 2 \cdot C_{je0}$$

Then Input Capacitance

$$C_{\pi} = C_{be} + C_{je}$$



CDEEP
IIT Bombay

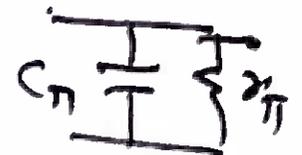

Course Name

Analog Circuits

Lecture No.

Instructor's Name

Prof. A. N. Chandorkar

Slide No: 16

Base-Collector J^n capacitance C_{μ}

$C_{\mu} \Rightarrow$ varies with variation in V_{CB}
as junction is in Reversed-Biased State.

We know RB J^n capacitance of a diode (with Step J^n)
is given by

$$C_j = \frac{C_{j0}}{\left(1 - \frac{V}{\phi_0}\right)^{1/2}}$$

($1/2$ may become $1/3$
for linearly graded
junction)

$$\phi_0 = \text{Built-in Potential} = \frac{kT}{q} \ln \frac{N_a N_d}{n_i^2}$$

Hence in Transistor

$$C_{\mu} = C_{\mu 0} / \left(1 - \frac{V_{CB}}{\phi_0}\right)^n \quad (n = 1/2 \text{ or } 1/3)$$



CDEEP
IIT Bombay

Course Name
Analog Circuits

Lecture No

Instructor's Name
Prof. A. N. Chandorkar

Collector - Base resistance r_{μ}

As V_{BE} gets modulated due to V_{in} , the Base-Collector junction bias too get modulated
That V_{CE} changes due to change in I_B

We define



$$r_{\mu} = \frac{\Delta V_{CE}}{\Delta I_B} = \frac{\Delta V_{CE}}{\Delta I_C} \cdot \frac{\Delta I_C}{\Delta I_B} = \frac{V_{CE}}{I_C} \cdot \frac{I_C}{I_B}$$


$$\therefore \boxed{r_{\mu} = r_o \cdot \beta_o}$$

Base and Collector regions.



CDEEP
IIT Bombay

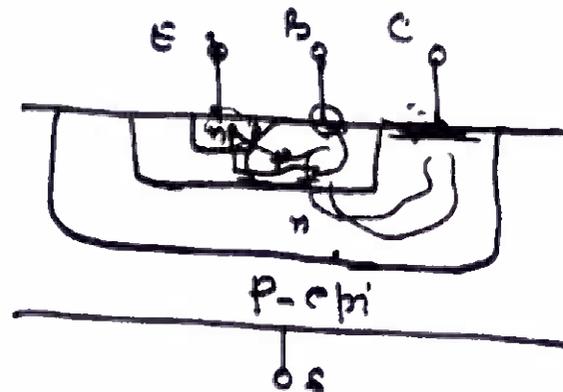


Collector Substrate Capacitance C_{cs} 

Since in an IC, collector is a diffused region in substrate, one observes presence of a collector-substrate junction with capacitance

$$C'_{cs} = \frac{C_{cs0}}{\left(1 - \frac{V_{cs}}{\phi'_0}\right)^m}$$



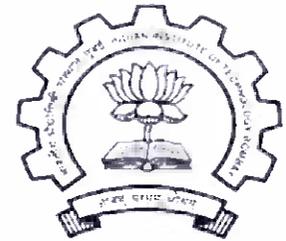Normally substrate is grounded. Hence C_{cs} is the collector capacitance between collector terminal & ground



Parasitic Resistances $r_{bb'}$, r_{es} & r_c CDEEP
IIT Bombay

1. $r_{bb'}$:- Base Resistance
2. r_{es} :- Emitter Region Resistance
3. r_c :- Collector Region Resistance.

Using these parameters we can now create the Small Signal Equivalent Circuit of a Bipolar Transistor.

Equivalent Circuit of BJT



CDEEP
IIT Bombay

