

# Unit 7 - Week 5 : Unit 5

Course outline
How to access the portal
Week 0 Assignment 0
Week 1
Week 2 : Unit 2
Week 3 : Unit 3
Week 4 : Unit 4
Week 5 : Unit 5
<ul style="list-style-type: none"> <li>Lecture 21 : Design of Adders (Part I)</li> <li>Lecture 22 : Design of Adders (Part II)</li> <li>Lecture 23 : Design of Adders (Part III)</li> <li>Lecture 24 : Logic Design(Part I)</li> <li>Lecture 25 : Logic Design(Part II)</li> <li>Lecture 26 : Logic Design(Part III)</li> <li>Lecture Material of Week 5</li> <li>Feedback for Week 5</li> <li>Quiz : Week 5 Assignment 5</li> </ul>
Week 6
Week 7
Week 8
Week 9
Week 10
Week 11
Week 12
Download Videos
Text Transcripts
Detail Solution
Live Session

## Week 5 Assignment 5

The due date for submitting this assignment has passed.  
As per our records you have not submitted this assignment.

**Due on 2019-09-04, 23:59 IST.**

1) Suppose you are implementing the CARRY output of a full adder using 2-input AND and OR gates. Assume that the delay of a 2-input AND gate is 3 nanoseconds, and the delay of a 2-input OR gate is 4 nanoseconds. The total propagation delay for generating the CARRY output will be ..... nanoseconds.

No, the answer is incorrect.  
Score: 0  
Accepted Answers:  
(Type: Numeric) 11

1 point

2) The number of 2-input NAND gates required to implement a 2-input exclusive-OR function is at least

- 3
- 4
- 5
- None of these

- a.  
 b.  
 c.  
 d.

1 point

3) For a full adder, suppose that the propagation delays to generate the SUM and CARRY outputs are 12 nanoseconds and 8 nanoseconds respectively. A 4-bit ripple carry adder is constructed using such full adders. The worst-case propagation delay of the 4-bit adder will be

- 32 nanoseconds
- 36 nanoseconds
- 48 nanoseconds
- None of these

- a.  
 b.  
 c.  
 d.

1 point

4) Which of the following statements are true for a carry lookahead adder?

- The carry generate function specifies the condition when a full adder stage can generate a carry irrespective of its carry input.
- The carry propagate function specifies the condition when a full adder stage can generate a carry considering its carry input.
- The carry propagate function specifies the condition when a carry input can propagate to the carry output in a full adder stage.
- The cost of the carry lookahead circuit increases rapidly with increase in the number of bits.

- a.  
 b.  
 c.  
 d.

1 point

No, the answer is incorrect.  
Score: 0  
Accepted Answers:  
a.  
c.  
d.

5) To implement any arbitrary 5-variable function, we need

- A 16-to-1 multiplexer and a NOT gate.
- A 16-to-1 multiplexer and an AND gate.
- A 16-to-1 multiplexer and an OR gate.
- None of these.

- a.  
 b.  
 c.  
 d.

1 point

No, the answer is incorrect.  
Score: 0  
Accepted Answers:  
a.

6) The minimum number of 2-to-1 multiplexers required to build a 16-to-1 multiplexer will be .....

No, the answer is incorrect.  
Score: 0  
Accepted Answers:  
(Type: Numeric) 15

1 point

7) A 16-bit adder is designed by cascading four 4-bit carry lookahead adder (CLA) modules. If the delay of a 4-bit CLA module (including carry generate and propagate circuits) is 15 nanoseconds, and the delay of an exclusive-OR gate is 7 nanoseconds, the worst-case delay of the adder will be

- 60 nanoseconds
- 67 nanoseconds
- 88 nanoseconds
- None of these

- a.  
 b.  
 c.  
 d.

1 point

No, the answer is incorrect.  
Score: 0  
Accepted Answers:  
b.

8) In addition to a parallel adder in the last stage, what will be the minimum number of carry save adders required to add 10 numbers?


- 6
- 7
- 8
- 9

- a.  
 b.  
 c.  
 d.

1 point

No, the answer is incorrect.  
Score: 0  
Accepted Answers:  
c.

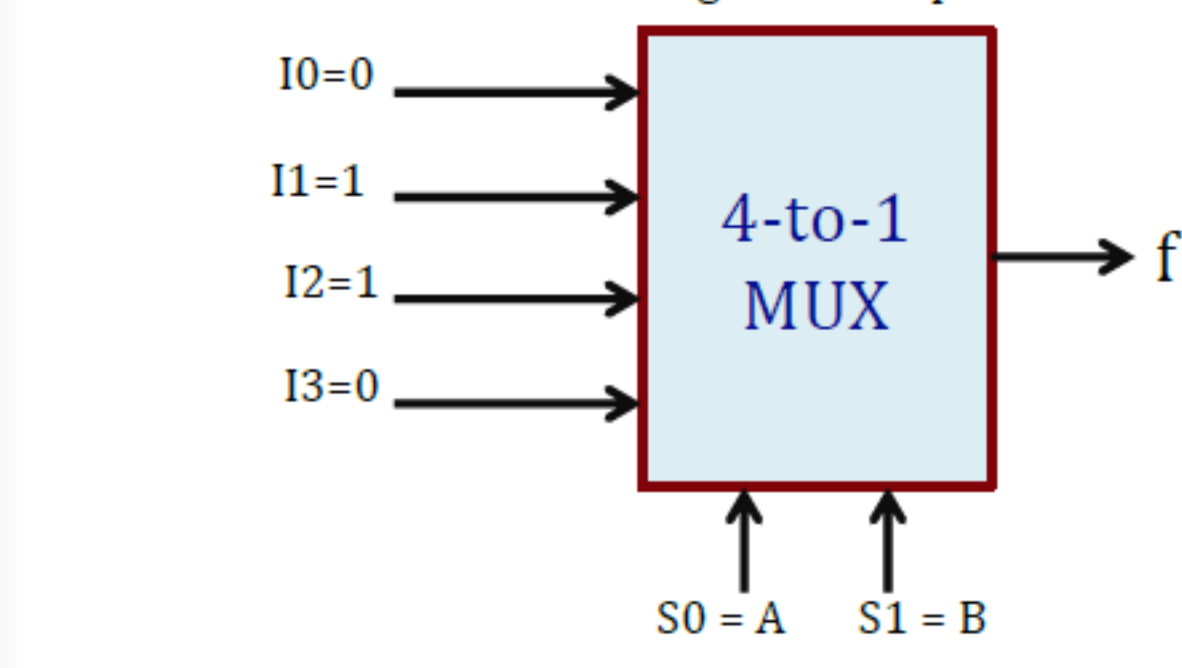9) What function does the following circuit implement?



- 2-input exclusive-OR function of A and B.
- 2-input NAND function of A and B.
- 2-input OR function of A and B.
- None of these.

- a.  
 b.  
 c.  
 d.

1 point

No, the answer is incorrect.  
Score: 0  
Accepted Answers:  
a.

10) For a 7-segment display input, if the output of 1 indicates that a segment will glow, what will be the outputs for displaying the letter 'E'?

- A = 1, B = 0, C = 0, D = 0, E = 1, F = 1, G = 1
- A = 1, B = 0, C = 0, D = 1, E = 1, F = 1, G = 1
- A = 1, B = 1, C = 0, D = 0, E = 1, F = 0, G = 1
- None of these

- a.  
 b.  
 c.  
 d.

1 point

No, the answer is incorrect.  
Score: 0  
Accepted Answers:  
b.