

X

NPTEL

reviewer2@nptel.iitm.ac.in ▼

Courses » Basic Electronics

Announcements

Course

Ask a Question

Progress



Unit 7 - Week 6

Course outline

How to access the portal

Week 1

Week 2

Week 3

Week 4

Week 5

Week 6

- Lecture 31: BJT amplifier-7
- Lecture 32: Introduction to op-amps
- Lecture 33: Op-amp circuits-1
- Lecture 34: Op-amp circuits-2
- Lecture 35: Op-amp circuits-3
- Lecture 36: Difference amplifier
- Week 6 Slides PDF
- Quiz : Assignment 6
- Weekly Feedback Form
- Download Videos
- Assignment-6 Solutions

Week 7

Week 8

Assignment 6

The due date for submitting this assignment has passed. **Due on 2018-03-07, 23:59 IST**
As per our records you have not submitted this assignment.

1) If the emitter resistance R_E in the common-emitter amplifier is partially bypassed,

1 point

- the input resistance decreases.
- the voltage gain increases.
- a larger input voltage can be applied without causing distortion in the output waveform.
- the DC (bias) value of I_C increases.

No, the answer is incorrect.


Score: 0

Accepted Answers:

a larger input voltage can be applied without causing distortion in the output waveform.

2) What is V_0 in the following circuit?

1 point

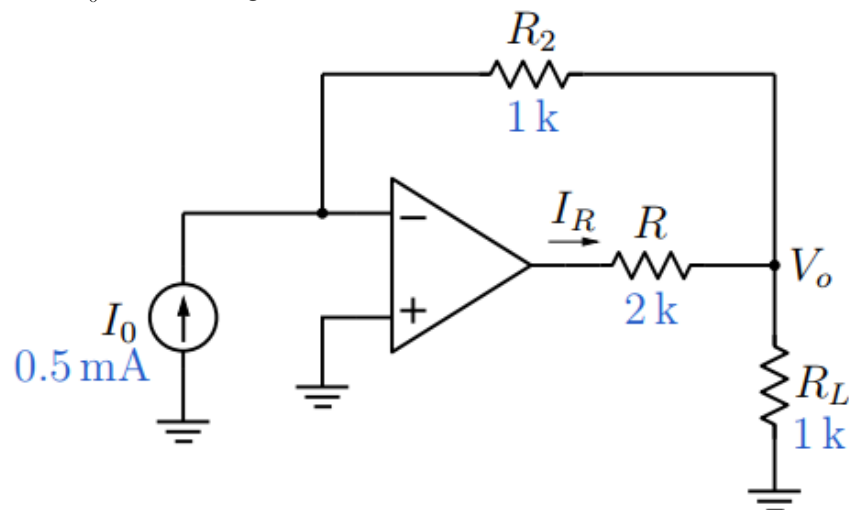

- 0.5V
- 0.5V
- 1V
- 1V

No, the answer is incorrect.

Score: 0

Accepted Answers:

Week 9


Week 10

Week 11

Week 12

 $-0.5V$ 3) In the circuit of Q-2, what is I_R ?


1 point

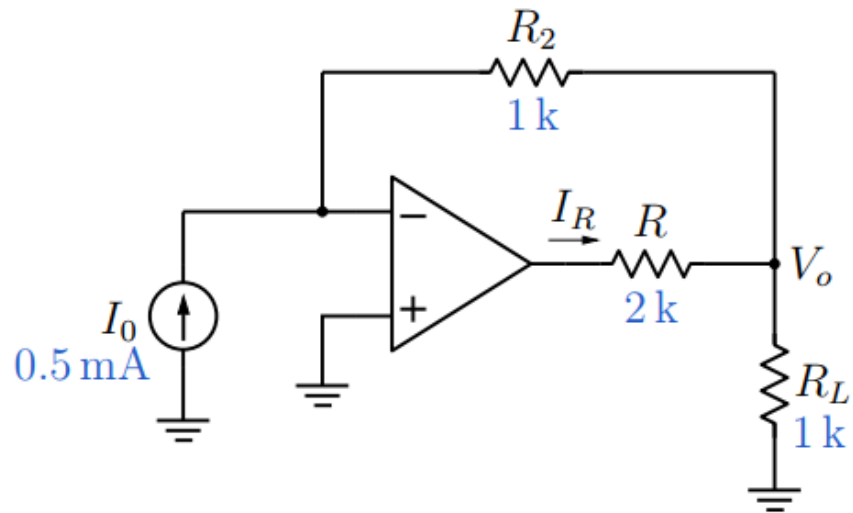

- 0.5mA
- 0.75mA
- 1mA
- 1mA

No, the answer is incorrect.**Score: 0****Accepted Answers:** $-1mA$ 4) In the circuit shown in the figure with $V_i = 2V$, what is V_o ?

1 point

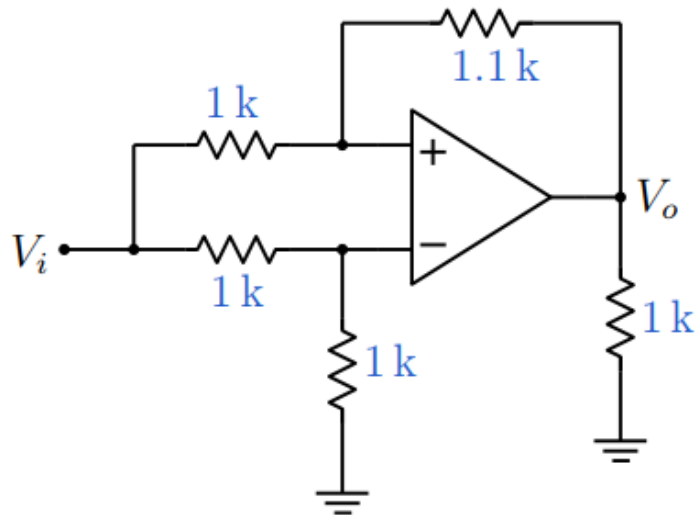

- 0.1V
- 0.2V
- 0.2V
- 0.55V

No, the answer is incorrect.**Score: 0****Accepted Answers:** $-0.1V$

5)

1 point



In the circuit shown in the figure, what is V_o for $V_i = 0.1V$?

- 0.4V
- 0.3V
- 0.6V
- 0.2V


No, the answer is incorrect.

Score: 0

Accepted Answers:

0.3V

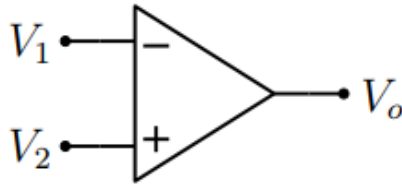6) The figure shows a comparator with inputs V_1 and V_2 , and output V_o where $V_2 = 2V$ (DC), 1 point and V_1 is a triangular signal with a frequency of 1 kHz and peak-to-peak voltage of 10 V. What is the duty cycle of the output voltage?



- 0.6
- 0.33
- 0.45
- 0.7


No, the answer is incorrect.

Score: 0

Accepted Answers:

0.7

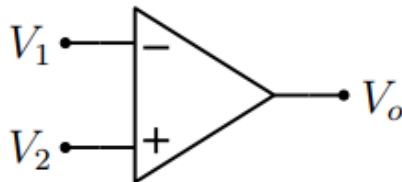7) The figure shows a comparator with inputs V_1 and V_2 , and output V_o where 1 point $V_2 = 2V$ (DC), and V_1 is a sinusoidal signal with a frequency of 1 kHz and peak-to-peak voltage of 10 V. What is the duty cycle of the output voltage?



- 0.63
- 0.45
- 0.72
- 0.28

No, the answer is incorrect.

Score: 0

Accepted Answers:


0.63

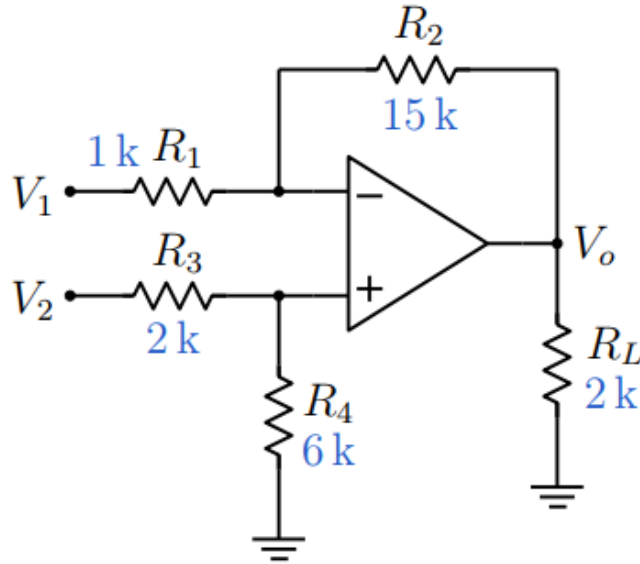8)

1 point



In the circuit shown in the figure $V_1 = 0.1V$, and $V_2 = 0.2V$. What is V_o ?



- 0.6V
- 1.2V
- 0.9V
- 0.3V


No, the answer is incorrect.

Score: 0

Accepted Answers:

0.9V

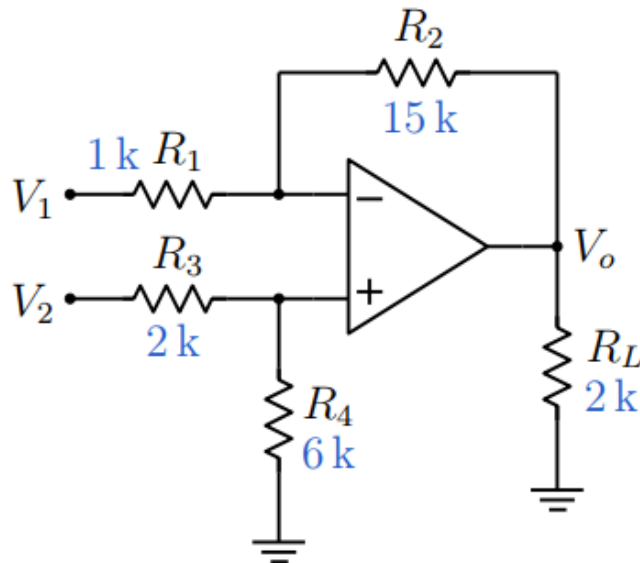9) In the op-amp circuit of Q-8, let $V_1 = 0.2\sin\omega t$ Volts and $V_2 = 0.1\sin\omega t$ Volts. What is V_o (in Volts)? **1 point**



- $0.6\sin\omega t$
- $-1.2\sin\omega t$
- $0.9\sin\omega t$
- $-1.8\sin\omega t$

No, the answer is incorrect.


Score: 0

Accepted Answers:

$-1.8\sin\omega t$

10) In the op-amp circuit shown in the figure, the output voltage is given by $V_o = k_1 V_1 + k_2 V_2$. What are the values of k_1 and k_2 ?

1 point

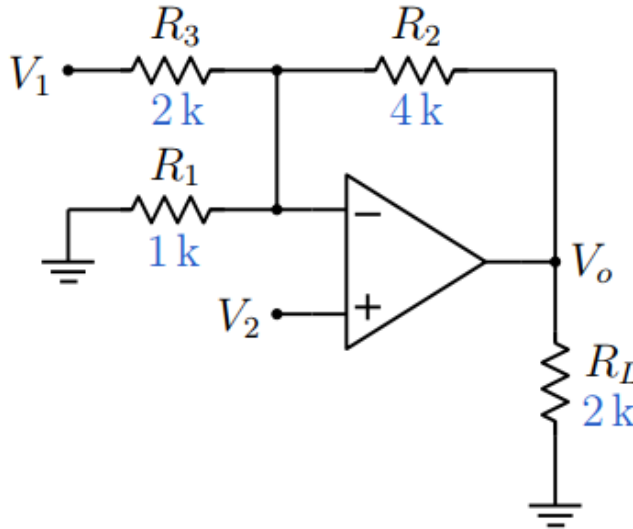

- $k_1 = -3, k_2 = 5$
- $k_1 = -2, k_2 = 7$
- $k_1 = 2, k_2 = 2$
- $k_1 = 3, k_2 = 5$

No, the answer is incorrect.


Score: 0

Accepted Answers:

$k_1 = -2, k_2 = 7$

11) In the op-amp circuit shown in the figure, what input voltage V_i should be applied to get a current $I_L = 50\mu A$ through R_L ?

1 point

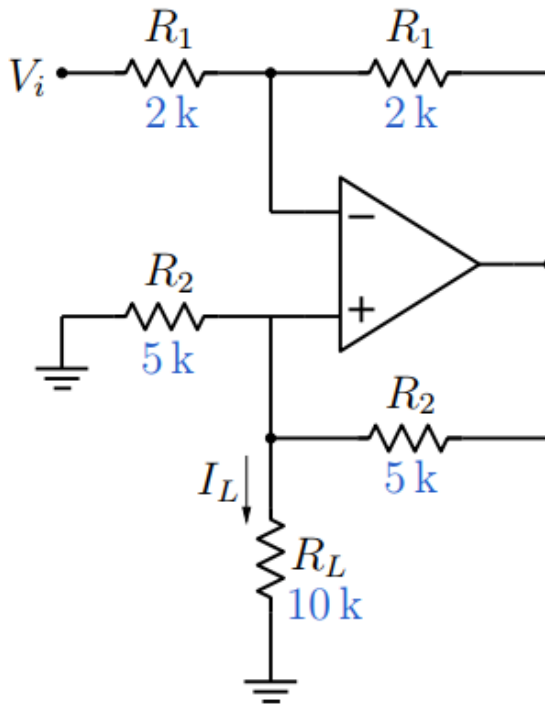

- 0.5V
- 0.6V

- 0.25V
- 0.4V


No, the answer is incorrect.

Score: 0

Accepted Answers:

-0.25V

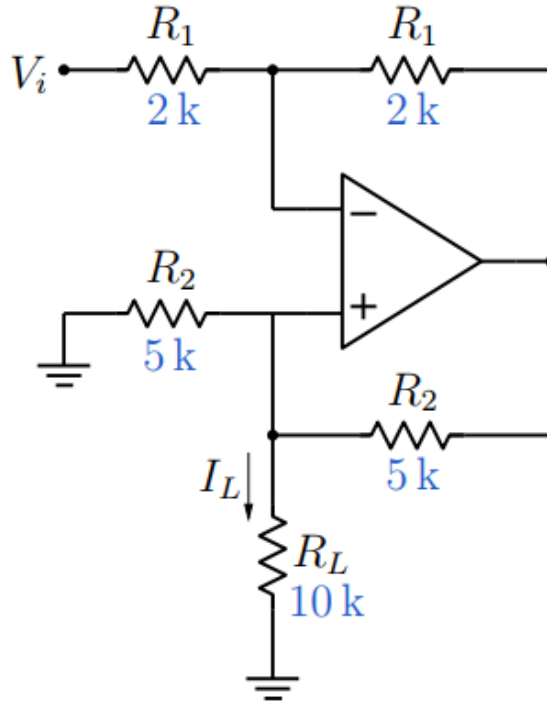12) In the circuit of Q-11, R_1 is changed (i.e., both resistances marked as R_1) from $2k\Omega$ to $4k\Omega$. What input voltage V_i should be applied to get a current $I_L = 50\mu A$ through R_L ? 1 point



- 0.5V
- 0.25V
- 0.5V
- 1V

No, the answer is incorrect.


Score: 0

Accepted Answers:

-0.25V

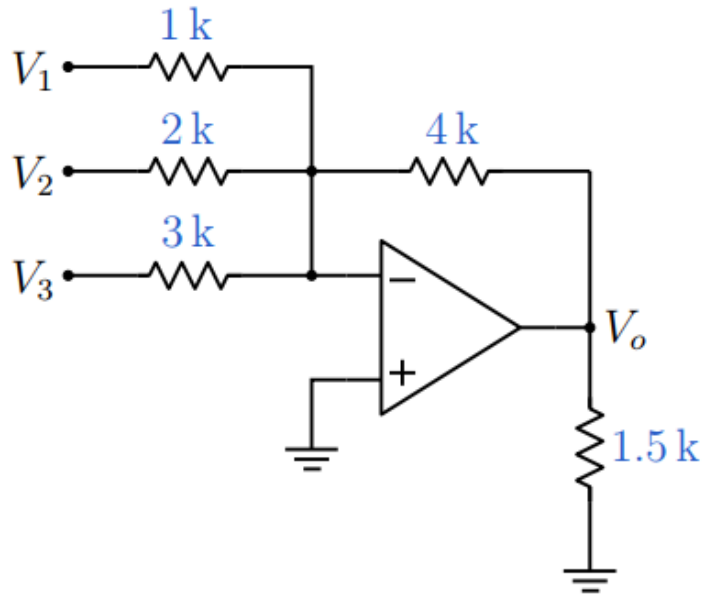13) In the circuit shown in the figure, $V_1 = 0.1V$, $V_2 = 0.2\sin\omega t$, and $V_3 = -0.3V$. Which 1 point of the following options correctly describes the output waveform $V_o(t)$?






- $V_o(t) = -0.4\sin\omega t$
- $V_o(t) = 0.1\sin\omega t + 0.3$
- $V_o(t) = -0.4\sin\omega t + 0.2$
- $V_o(t) = -0.1\sin\omega t - 0.2$

No, the answer is incorrect.
Score: 0

Accepted Answers:
 $V_o(t) = -0.4\sin\omega t$

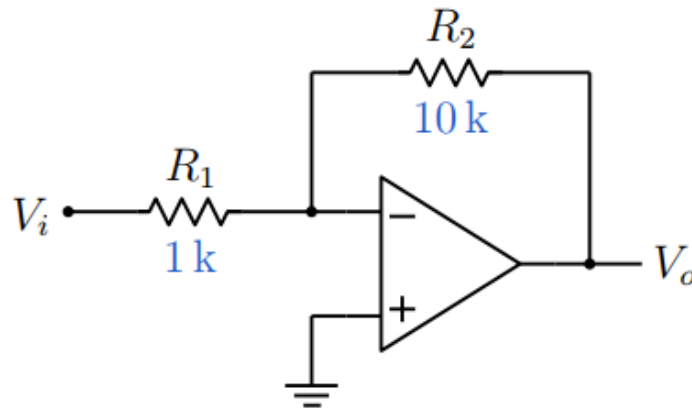14) In the inverting amplifier shown in the figure, the op-amp is ideal except that it has a finite gain $A_V = 100$. For an input voltage $V_i = 0.1\text{ V}$, what is V_o ? 1 point



- 0.95V
- 1V
- 0.9V
- 0.85V

No, the answer is incorrect.
Score: 0

Accepted Answers:
-0.9V



© 2014 NPTEL - Privacy & Terms - Honor Code - FAQs -

A project of



In association with



Funded by



Powered by

