

Unit 5 - Week-3

Course outline
How to access the portal?
Week 0
Week-1
Week-2
Week-3
<input type="radio"/> Analysis of Single Phase Half Controlled Converter-fed Separately Excited DC Motor
<input type="radio"/> Three Phase Full Controlled Converter-fed Separately Excited DC Motor, Multi-quadrant Operation of DC Motor
<input type="radio"/> Dual Converter-fed DC Motor, Multi-quadrant Operation Using Field Current Reversal
<input type="radio"/> DC Chopper-fed Separately Excited DC Motor for Motoring and Braking
<input type="radio"/> Two-quadrant DC Chopper, Four-quadrant DC Chopper
<input checked="" type="radio"/> Quiz : Assignment-3
<input type="radio"/> Assignment-3 Solutions
<input type="radio"/> Feedback For Week 3
Week-4
Week-5
Week-6
Week-7
Week-8
Live Session
Lecture Notes

Assignment-3

The due date for submitting this assignment has passed.
As per our records you have not submitted this assignment.

Due on 2019-08-21, 23:59 IST.

- 1) A half controlled converter can operate in how many quadrants of V-I Plane? 1 point
- One
 Two
 Three
 Four
- No, the answer is incorrect.**
Score: 0
Accepted Answers:
One
- 2) For a half controlled converter, the duration $\pi \leq \omega t \leq \beta$ is known as 1 point
- Duty Interval
 Coasting Interval
 Freewheeling Interval
 Zero Current Interval
- No, the answer is incorrect.**
Score: 0
Accepted Answers:
Freewheeling Interval
- 3) A 220 V, 960 rpm, 10A separately excited DC motor has an armature resistance of 2Ω . It is fed from a single phase half controlled bridge with an input ac supply of single phase 230 V, 50 Hz. If the triggering angle $\alpha = 60^\circ$, the no load speed of the motor is 2 points
- 960 rpm
 1029 rpm
 1423 rpm
 1561 rpm
- No, the answer is incorrect.**
Score: 0
Accepted Answers:
1561 rpm
- 4) If the triggering angle $\alpha = 120^\circ$ for Q3, the no load speed of the motor is 2 points
- 960 rpm
 1051 rpm
 1352 rpm
 1529 rpm
- No, the answer is incorrect.**
Score: 0
Accepted Answers:
1352 rpm
- 5) If the AC input supply frequency is f , the ripple frequency of the output voltage of a three phase fully controlled bridge converter is 1 point
- f
 $2f$
 $3f$
 $6f$
- No, the answer is incorrect.**
Score: 0
Accepted Answers:
6f
- 6) A three phase fully controlled bridge converter is fed from 3 phase, 400 V 50 Hz AC supply. If the triggering angle of the converter is 45° , the average output DC voltage is 2 points
- 231.1 V
 305.6 V
 381.9 V
 421.7 V
- No, the answer is incorrect.**
Score: 0
Accepted Answers:
381.9 V
- 7) A three phase full controlled converter is feeding the armature of a separately excited DC motor. The motor has to operate in quadrant-III. Which of the following methods is suitable? 1 point
- By adjusting the triggering angle α only
 By adjusting the triggering angle α followed by armature connection reversal
 By operating with triggering angle $\alpha > 90^\circ$
 By connecting a freewheeling diode across the armature in addition to adjusting the triggering angle α
- No, the answer is incorrect.**
Score: 0
Accepted Answers:
By adjusting the triggering angle α followed by armature connection reversal
- 8) The intergroup reactor in a circulating current dual converter directly helps in 1 point
- Limiting the circulating current
 Adjusting the output voltage of the converter
 Adjusting the output current of the converter
 Regenerative braking of the dc motor
- No, the answer is incorrect.**
Score: 0
Accepted Answers:
Limiting the circulating current
- 9) A 220 V, 1400 rpm, 50 A separately excited dc motor has an armature resistance of 0.4Ω . The motor is fed from a circulating current dual converter bridge having the ac-input of 3-phase 400 V, 50 Hz. Calculate the firing angles of the dual converter for motor operation at rated torque and 900 rpm. 3 points
- 54° & 126°
 74° & 106°
 80° & 100°
 85° & 95°
- No, the answer is incorrect.**
Score: 0
Accepted Answers:
 74° & 106°
- 10) Calculate the firing angles of the dual converter feeding dc motor as given in Q9, for motor operation at rated torque and -900 rpm. 3 points
- 126° & 54°
 106° & 74°
 100° & 80°
 95° & 85°
- No, the answer is incorrect.**
Score: 0
Accepted Answers:
 106° & 74°
- 11) A class A two-quadrant chopper operates in which quadrants of V-I plane? 1 point
- 1 & 2
 2 & 3
 3 & 4
 4 & 1
- No, the answer is incorrect.**
Score: 0
Accepted Answers:
1 & 2
- 12) A 230 V, 900 rpm, 200 A separately excited dc motor has an armature resistance of 0.05Ω . The motor is fed from a two quadrant chopper which provides motoring and regenerative braking operation. The source has a voltage of 200 V dc. Assuming continuous conduction, calculate the duty cycle of the chopper for operation at rated torque and speed of 500 rpm. 0 points
- 0.54
 0.44
 0.34
 0.24
- No, the answer is incorrect.**
Score: 0
Accepted Answers:
0.54
- 13) The motor in Q12 is operated in regenerative braking mode with rated torque and speed of 600 rpm. Calculate the duty cycle of the switch. 0 points
- 0.29
 0.39
 0.49
 0.59
- No, the answer is incorrect.**
Score: 0
Accepted Answers:
0.59
- 14) Assuming continuous current operation for a single quadrant chopper used for motoring operation of a dc motor, what is the interval $t_{on} \leq t \leq T$ called? 1 point
- Duty interval
 Freewheeling interval
 Coasting interval
 Energy storage interval
- No, the answer is incorrect.**
Score: 0
Accepted Answers:
Freewheeling interval
- 15) A single phase full controlled converter is used to control the armature of a separately excited dc motor. The critical speed which separates continuous and discontinuous current operation is found out to be 720 rpm. Which of the following statements is correct? 1 point
- The converter operates in continuous current operation for speed greater than 720 rpm
 The converter operates in continuous current operation for speed less than 720 rpm
 The converter operates in continuous current operation for speed greater than 360 rpm
 The converter operates in continuous current operation for speed less than 360 rpm
- No, the answer is incorrect.**
Score: 0
Accepted Answers:
The converter operates in continuous current operation for speed less than 720 rpm