

Course outline

How to access the portal

Week 0 Assignment 0

Week 1

- Lecture No 1: Basic Concepts, Examples
- Lecture No 2: Basic Concepts, Examples (Contd.)
- Lecture No 3: Basic Concepts, Examples (Contd.)
- Lecture No 4: Basic Concepts, Examples (Contd.)
- Lecture No 5: Basic Laws
- Lecture Materials
- Feedback for Week 1
- Quiz : Week 1 Assignment 1

Week 2

Week 3

Week 4

Week 5

Week 6

Week 7

Week 8

Week 9

Week 10

Week 11

Week 12


Download Videos

Detail Solution

Week 1 Assignment 1

The due date for submitting this assignment has passed. Due on 2019-08-14, 23:59 IST.
As per our records you have not submitted this assignment.

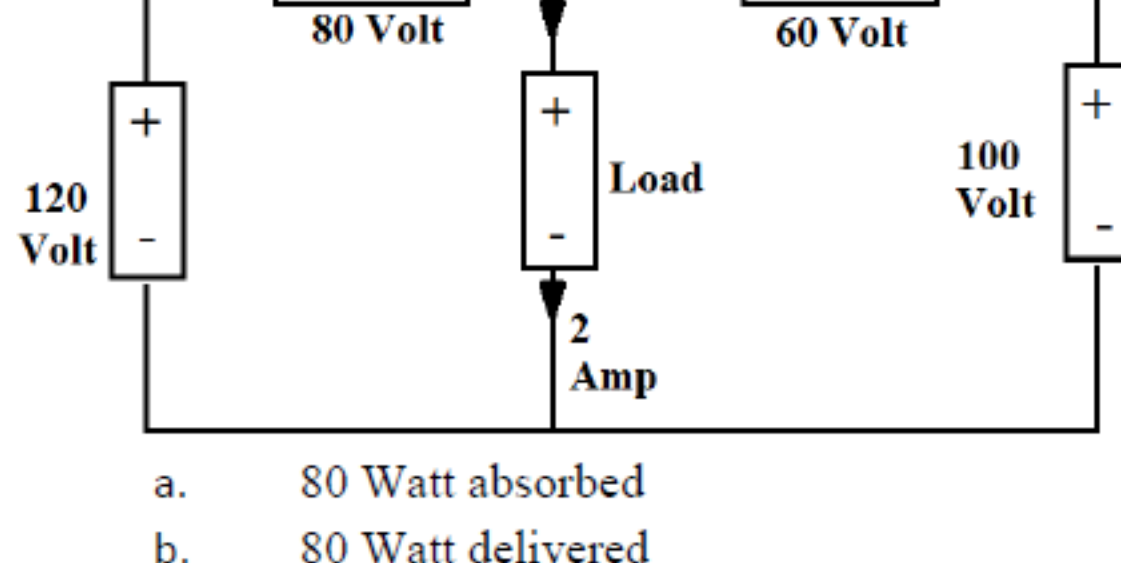1) Determine the amount of power supplied or absorbed by the load in the given circuit. 1 point



- a. 80 Watt absorbed
- b. 80 Watt delivered
- c. 320 Watt delivered
- d. 320 Watt absorbed

- a.
- b.
- c.
- d.

No, the answer is incorrect.
Score: 0

Accepted Answers:

a.

2) For $t \geq 0$, if $q = 0.02(1 - e^{-2000t})$ C then calculate amount of current (in ampere) that will flow through the circuit at time $t=2$ ms. 1 point

- a. 0.60-0.69
- b. 0.70-0.79
- c. 0.80-0.89
- d. 0.90-1.00


- a.
- b.
- c.
- d.

No, the answer is incorrect.
Score: 0

Accepted Answers:

b.

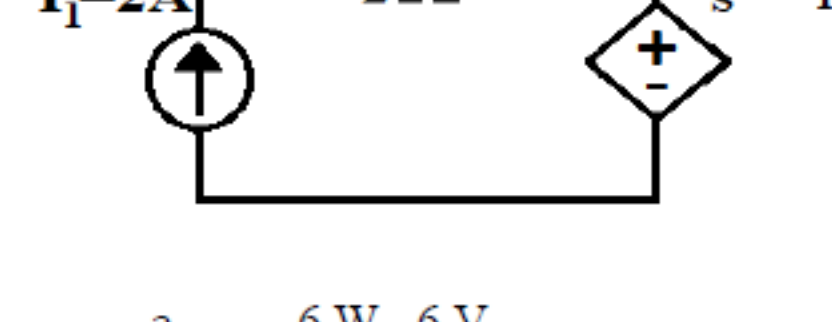3) The Power supplied and voltage across 2A current source is- 1 point



- a. 6 W , 6 V
- b. 8 W , 8 V
- c. 10 W , 8 V
- d. 12 W , 6 V

- a.
- b.
- c.
- d.

No, the answer is incorrect.
Score: 0

Accepted Answers:

d.

4) The voltage and current across an element is given by $100 e^{-250t}$ Volts and $50 e^{-250t}$ Amps. Calculate the energy delivered by it (in joule) for $t \geq 0$. 1 point

- a. 20
- b. 15
- c. 12
- d. 10

- a.
- b.
- c.
- d.

No, the answer is incorrect.
Score: 0

Accepted Answers:

d.

5) The resistance of a wire of length 'l' and diameter 'd', is R. If the length is reduced by 50% and diameter is increased by 100% then new resistance will be- 1 point

- a. R/8
- b. R/4
- c. R/2
- d. 2R

- a.
- b.
- c.
- d.

No, the answer is incorrect.
Score: 0

Accepted Answers:

a.

6) If n nodes, b branches and L independent loops are there in a network then the relation between them is- 1 point

- a. $b = L + 2n - 1$
- b. $b = L + n + 1$
- c. $b = L + n - 1$
- d. $b = L + 2n + 1$


- a.
- b.
- c.
- d.

No, the answer is incorrect.
Score: 0

Accepted Answers:

c.

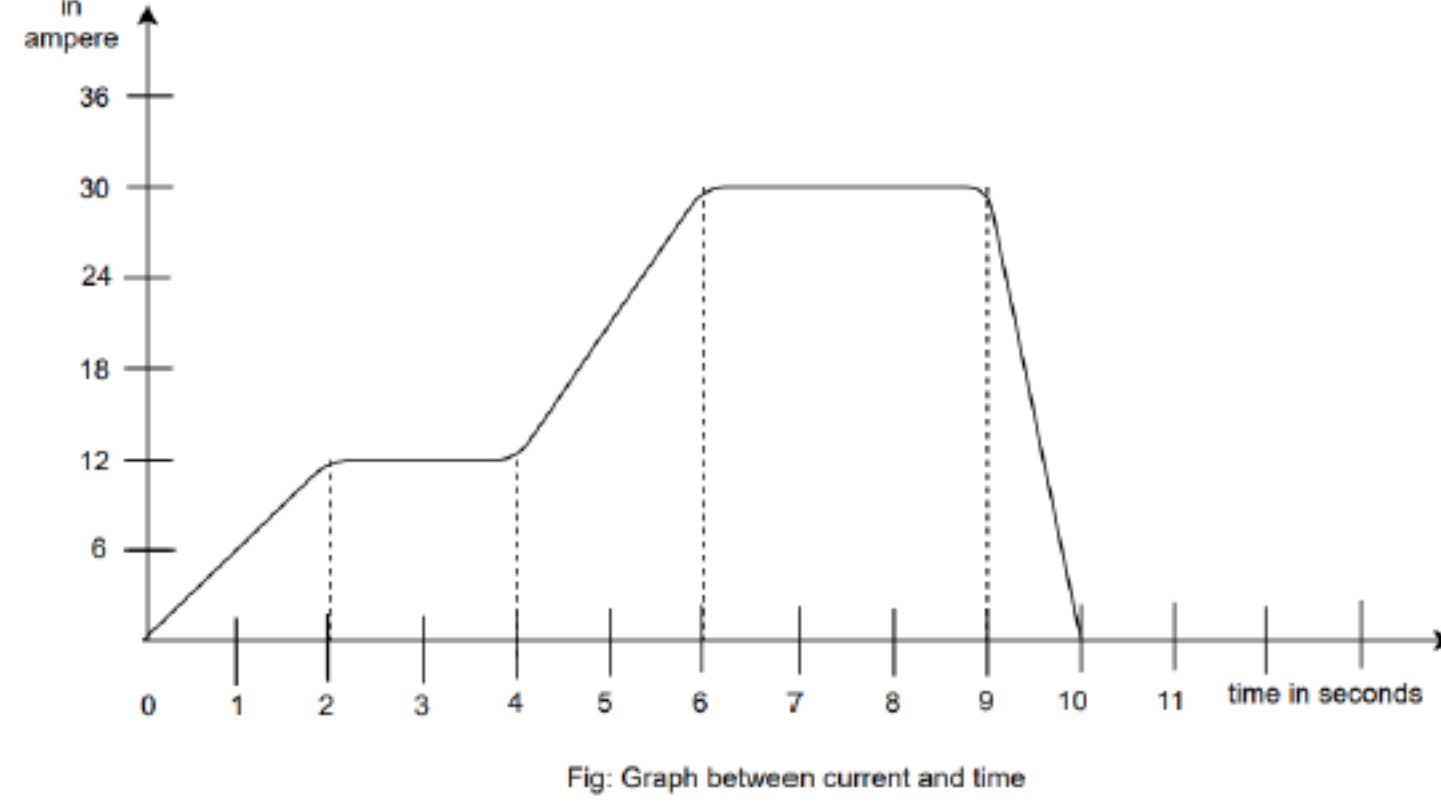7) The current through an element is shown in the given figure. The total charge (in Coulomb) passed through the element from 0-9 seconds is- 1 point



- a. 100-150
- b. 151-200
- c. 201-250
- d. 0

- a.
- b.
- c.
- d.

No, the answer is incorrect.
Score: 0

Accepted Answers:

b.

8) Across any two terminals, in case of open circuit and short circuit, the value of resistance will be (respectively)- 1 point

- a. 0 and infinity
- b. Infinity and 0
- c. 0 and 0
- d. Infinity and infinity

- a.
- b.
- c.
- d.


No, the answer is incorrect.
Score: 0

Accepted Answers:

b.

9) In the given circuit, Calculate current drawn and conductance of the lamp, if battery provides 200 Volt and Power rating of Lamp be 200W. 1 point

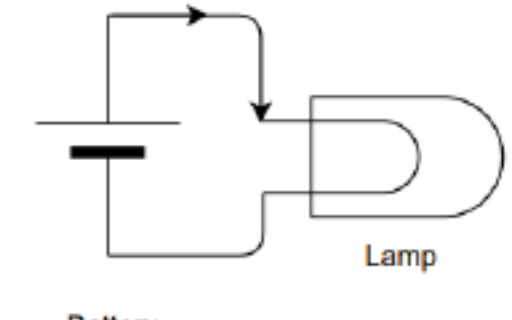- a. 1 Amp, 5 milli Ω
- b. 5 Amp, 1 milli Ω
- c. 1 Amp, 200 Ω
- d. 5 Amp, 200 Ω



- a.
- b.
- c.
- d.

No, the answer is incorrect.
Score: 0

Accepted Answers:

a.

10) In a cyber cafe, total load consists of 6 lamps of 20 W, 4 fans of 75 W, 10 computers of 200 W, 2 air conditioner of 1500 W and 2 printers of 50 W. If the supply is 230 V and basic monthly meter charge is 100/- then for an average loading of 50% throughout a day, what will be the electric bill for 1 month? Assume cost per unit for 1st 500 units be 2/- and after that 4/- . 1 point

- a. 6000/- 6499/-
- b. 6500/- 6999/-
- c. 7000/- 7499/-
- d. 7500/- 8000/-


- a.
- b.
- c.
- d.

No, the answer is incorrect.
Score: 0

Accepted Answers:

c.

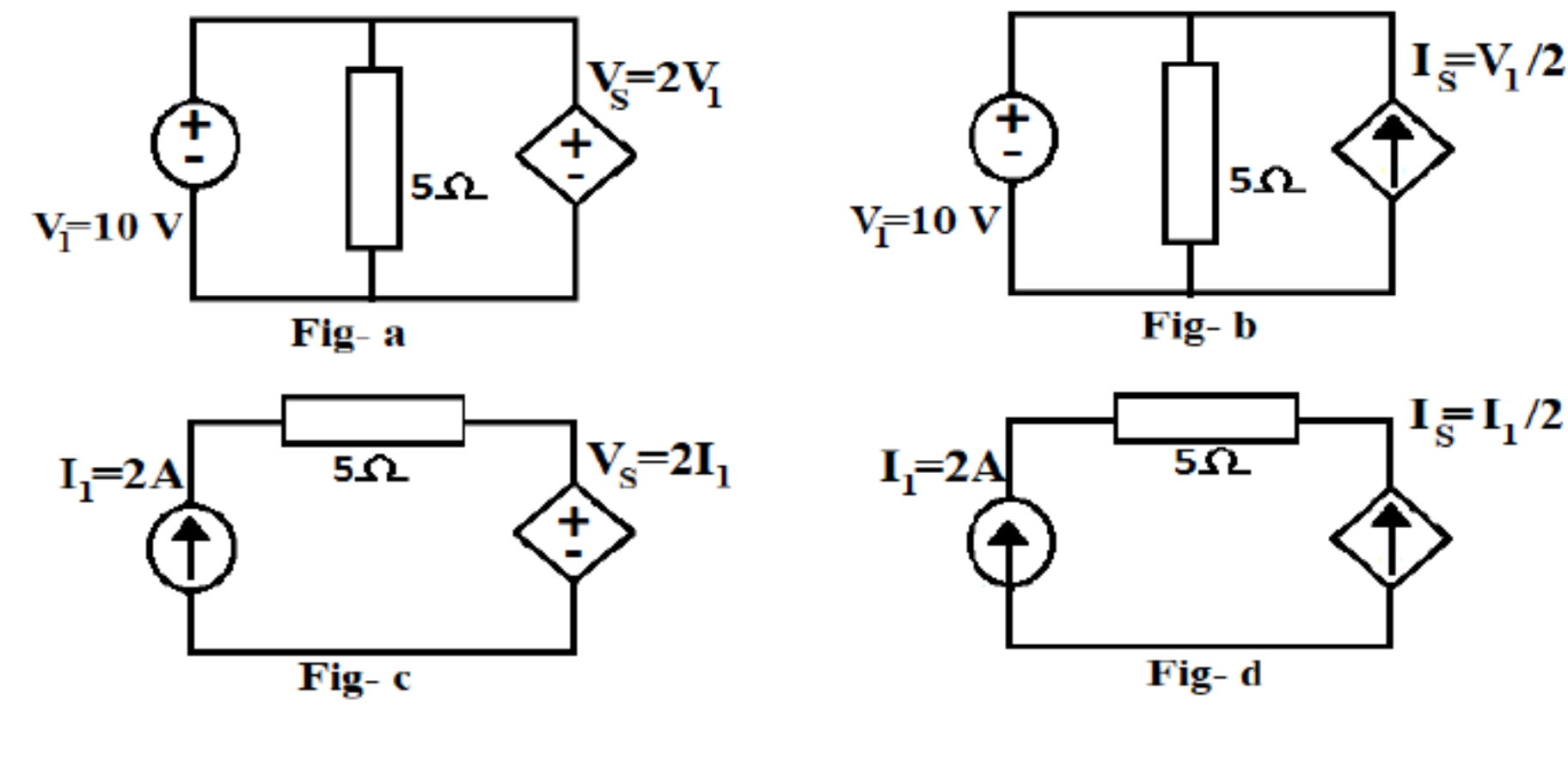11) Which of the following circuits are invalid- 1 point



- a. a, c and d
- b. a and d
- c. c and d
- d. a, b and d

- a.
- b.
- c.
- d.

No, the answer is incorrect.
Score: 0

Accepted Answers:

b.

12) In a house, the net energy consumption in a day is 27.6 kWh. If the supply is 230 V, then what is the current drawn in Ampere - 1 point

- a. 0.2
- b. 5
- c. 3
- d. Data insufficient

- a.
- b.
- c.
- d.

No, the answer is incorrect.
Score: 0

Accepted Answers:

b.