

Unit 6 - Week 4

Course outline

How to access the portal

Week 0 Assignment 0

Week 1

Week 2

Week 3

Week 4

- Lecture No 16: Methods of Circuit Analysis (Contd.)
- Lecture No 17: Methods of Circuit Analysis (Contd.)
- Lecture No 18: Methods of Circuit Analysis (Contd.) and Circuit Theorems
- Lecture No 19: Circuit Theorems (Contd.)
- Lecture No 20: Circuit Theorems (Contd.)
- Lecture Material
- Quiz : Week 4 Assignment 4
- Feedback for Week 4

Week 5

Week 6

Week 7

Week 8

Week 9

Week 10

Week 11

Week 12

Download Videos

Detail Solution

Week 4 Assignment 4

The due date for submitting this assignment has passed. **Due on 2019-08-28, 23:59 IST.**
 As per our records you have not submitted this assignment.

1) The mesh analysis in simple resistive circuit is related to 1 point

- a. Junction currents
- b. Battery emf
- c. IR drops
- d. Both b and c

- a.
- b.
- c.
- d.

No, the answer is incorrect.
 Score: 0
 Accepted Answers: d.

2) Calculate the power delivered (apprx.) by 100V source in the network shown in Fig. 1. 1 point

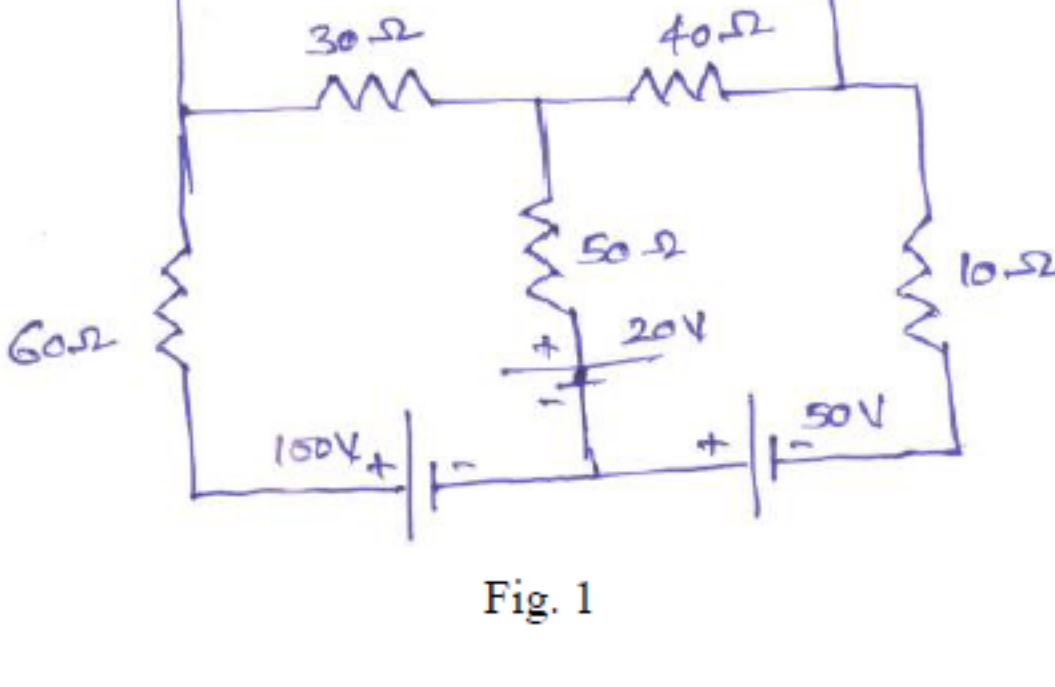


Fig. 1

- a. 162 - 167
- b. 250 - 254
- c. 502 - 506
- d. 326 - 330

- a.
- b.
- c.
- d.

No, the answer is incorrect.
 Score: 0
 Accepted Answers: a.

3) Find the voltage V_{ab} in the network shown in Fig. 2. 1 point

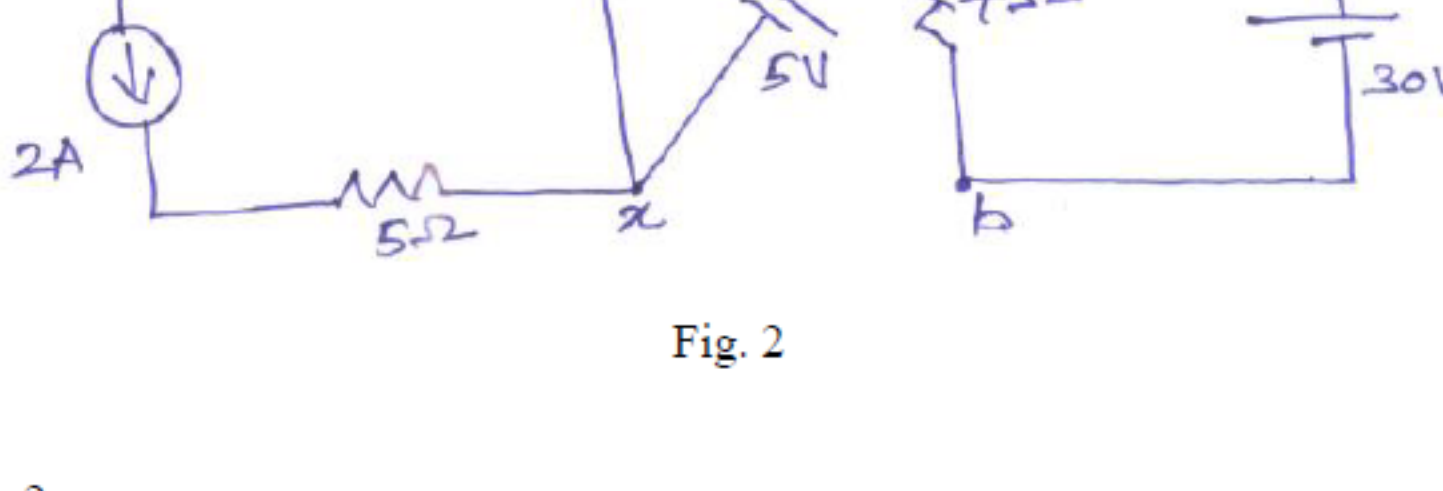


Fig. 2

- a. -2
- b. -3
- c. -4
- d. -5

- a.
- b.
- c.
- d.

No, the answer is incorrect.
 Score: 0
 Accepted Answers: b.

4) 0 points

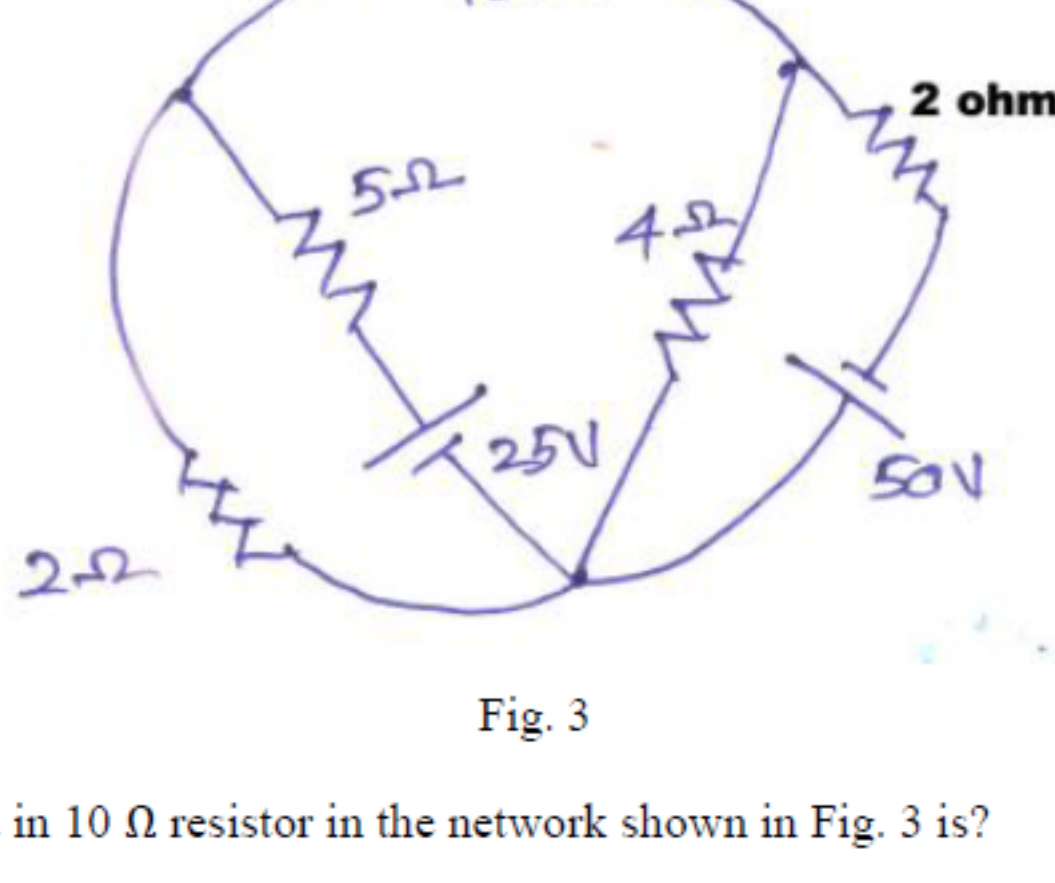


Fig. 3

The power dissipated in 10 Ω resistor in the network shown in Fig. 3 is?

- a. 315 - 319 W
- b. 415 - 419 W
- c. 372 - 376 W
- d. 472 - 476 W

- a.
- b.
- c.
- d.

No, the answer is incorrect.
 Score: 0
 Accepted Answers: a.

5) 1 point

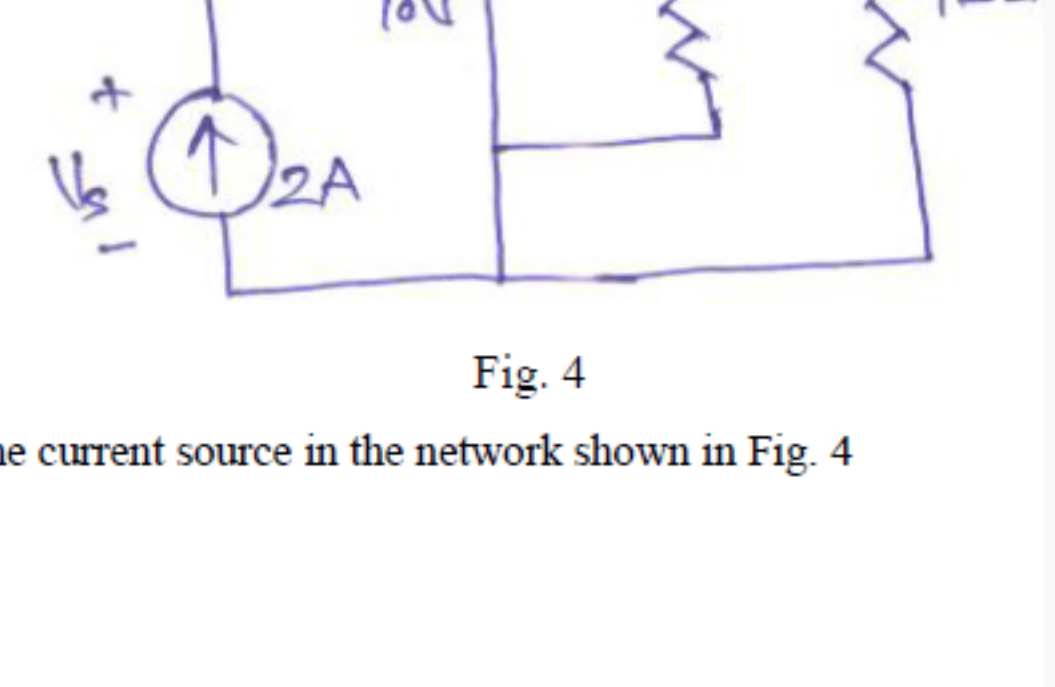


Fig. 4

The voltage V_x across the current source in the network shown in Fig. 4

- a. 5 V
- b. 10 V
- c. 15 V
- d. 20 V

- a.
- b.
- c.
- d.

No, the answer is incorrect.
 Score: 0
 Accepted Answers: d.

6) 1 point

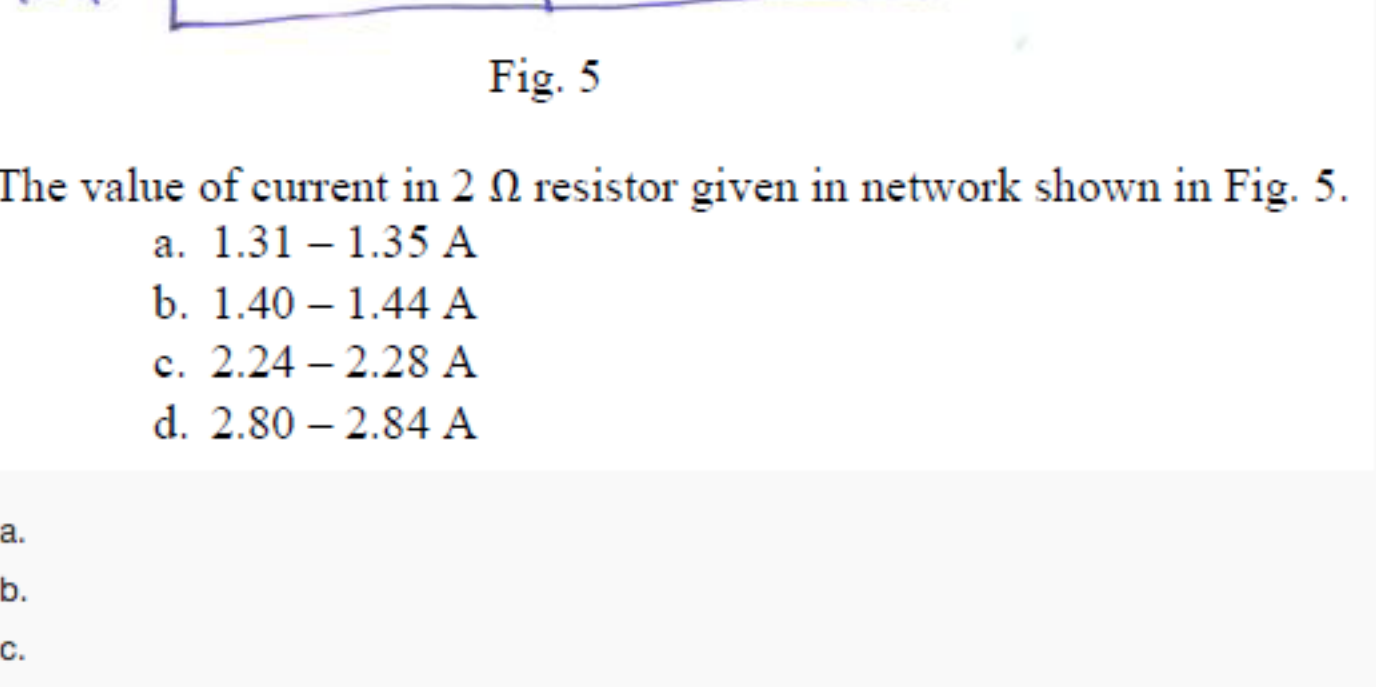


Fig. 5

The value of current in 2 Ω resistor given in network shown in Fig. 5.

- a. 1.31 - 1.35 A
- b. 1.40 - 1.44 A
- c. 2.24 - 2.28 A
- d. 2.80 - 2.84 A

- a.
- b.
- c.
- d.

No, the answer is incorrect.
 Score: 0
 Accepted Answers: a.

7) 1 point

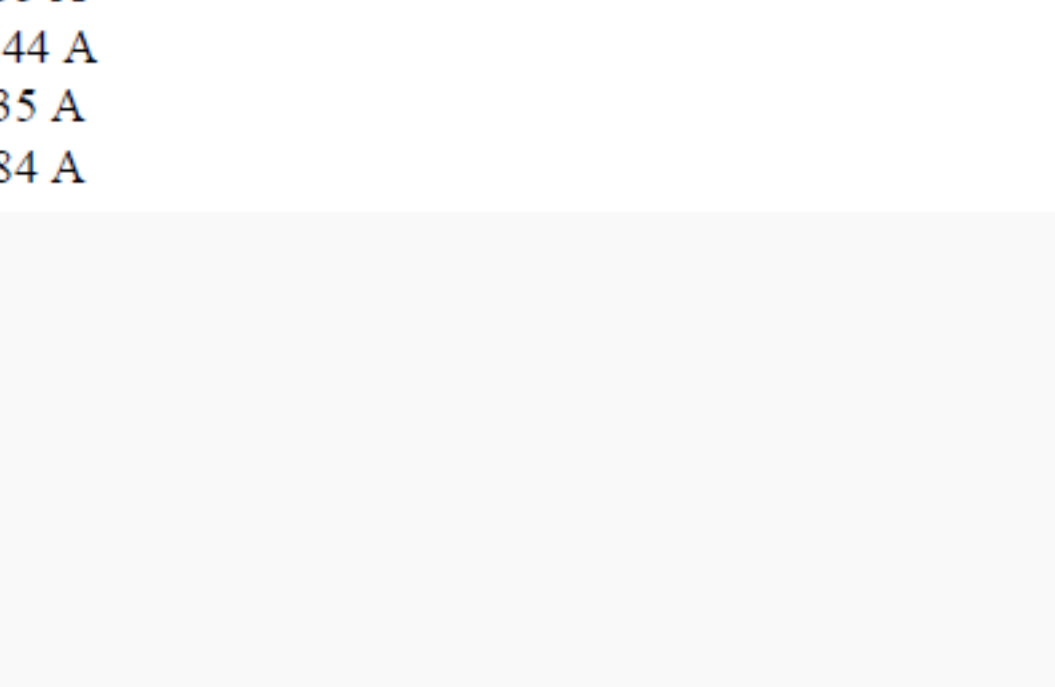


Fig. 6

The value of current in 1 Ω resistor given in network shown in Fig. 6

- a. 1.31 - 1.35 A
- b. 3.40 - 3.44 A
- c. 3.31 - 3.35 A
- d. 3.80 - 3.84 A

- a.
- b.
- c.
- d.

No, the answer is incorrect.
 Score: 0
 Accepted Answers: c.

8) Between the branch voltages of a loop the KVL imposes. 1 point

- a. Nonlinear constraints
- b. Linear constraints
- c. No constraints
- d. None

- a.
- b.
- c.
- d.

No, the answer is incorrect.
 Score: 0
 Accepted Answers: b.

9) 1 point

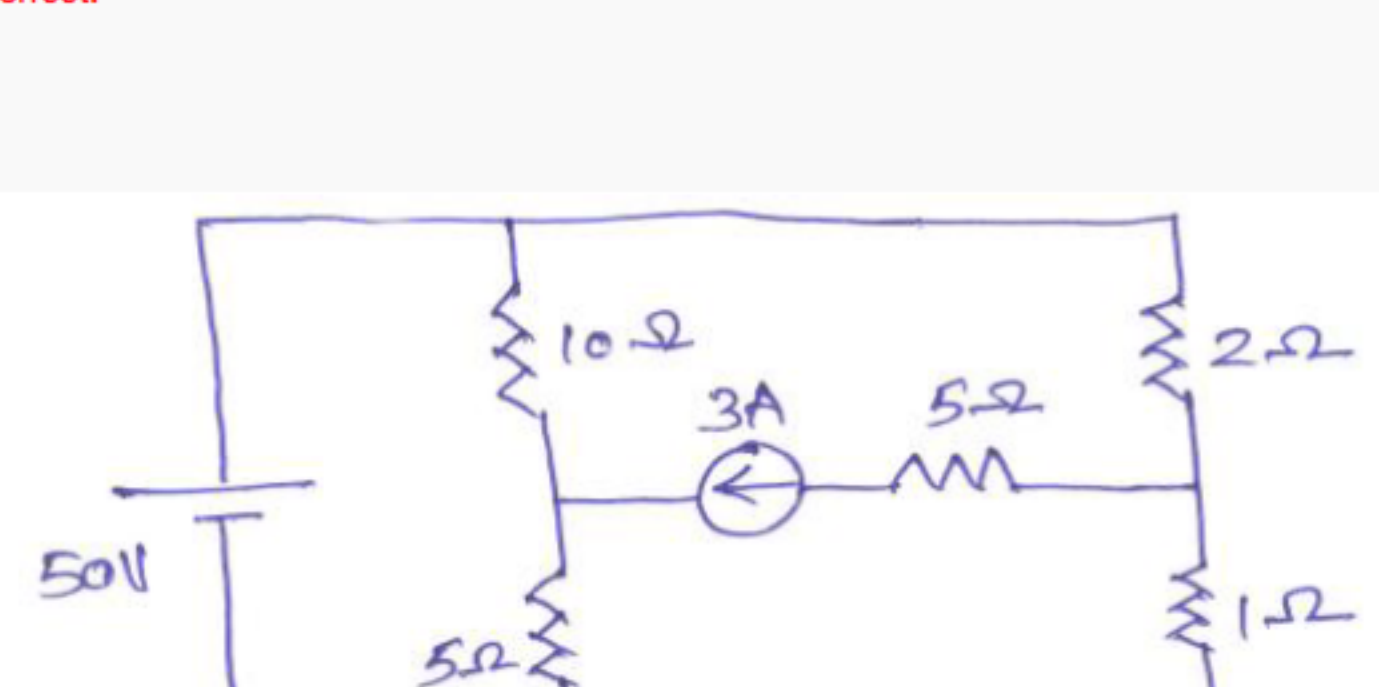


Fig. 7

The current delivered by the 50V source for the network given in Fig. 7.

- a. -20 A
- b. 20 A
- c. -10 A
- d. 10 A

- a.
- b.
- c.
- d.

No, the answer is incorrect.
 Score: 0
 Accepted Answers: b.

10) 1 point

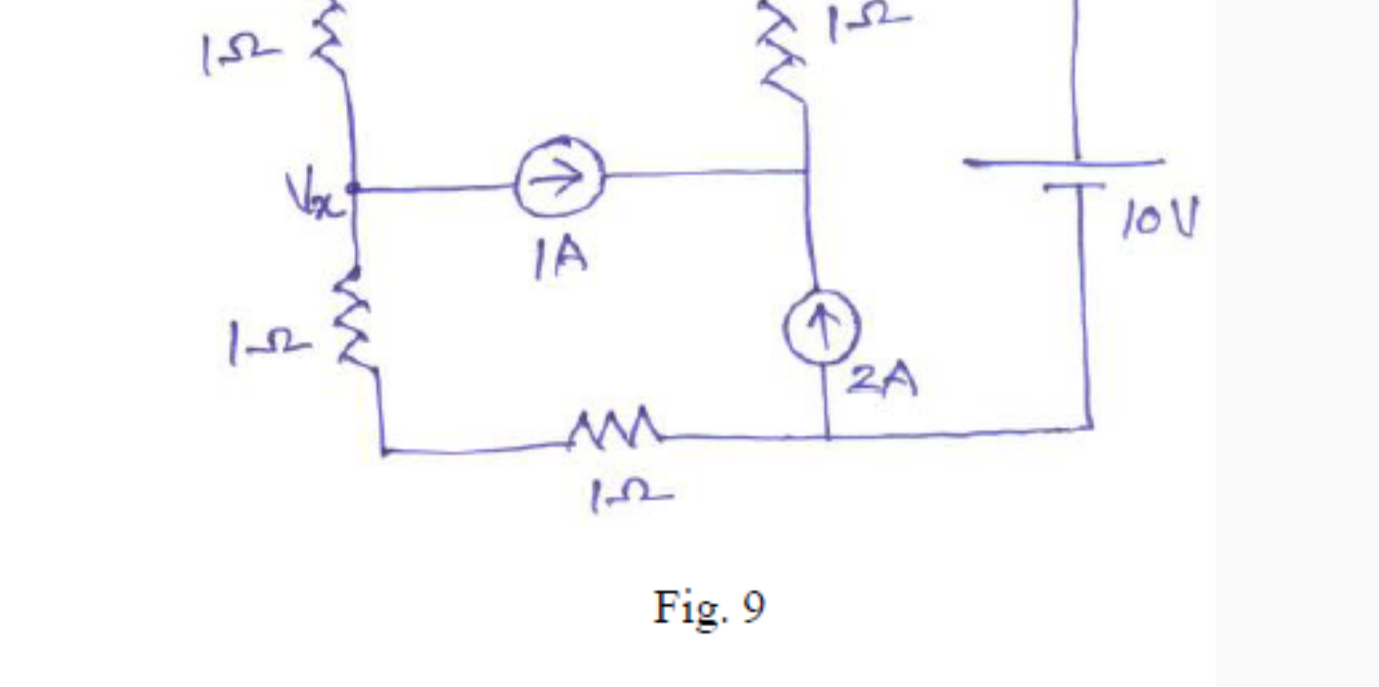


Fig. 8

The current through 2 Ω resistor given in network shown in Fig. 8.

- a. 15.31 - 15.35 A
- b. 27.84 - 27.88 A
- c. 17.64 - 17.68 A
- d. 13.80 - 13.84 A

- a.
- b.
- c.
- d.

No, the answer is incorrect.
 Score: 0
 Accepted Answers: c.

11) 1 point

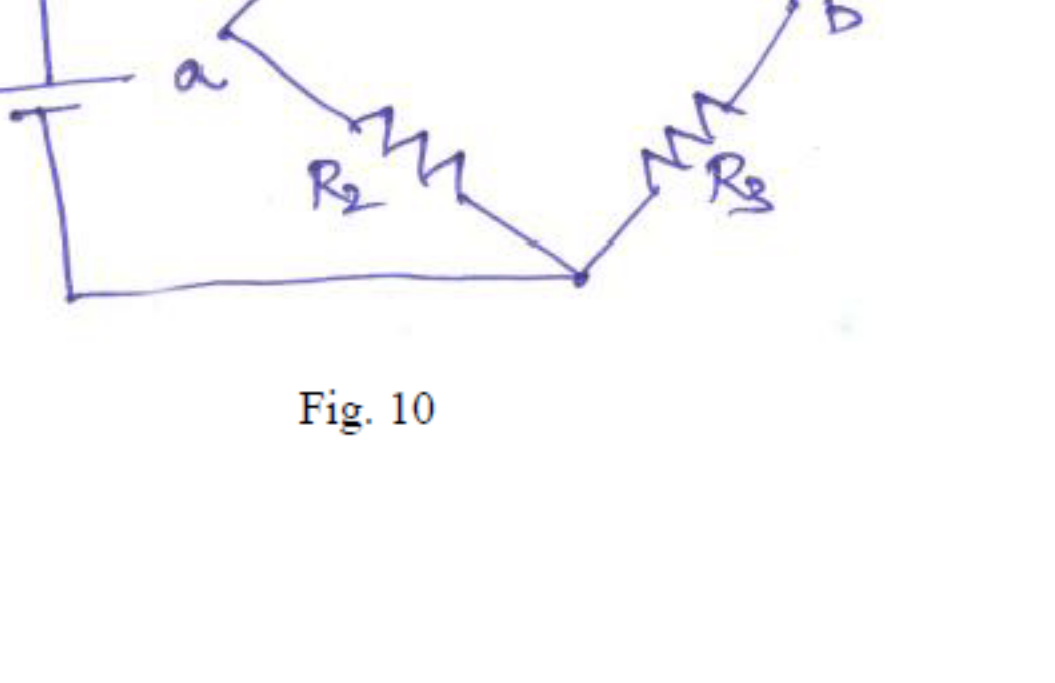


Fig. 9

The voltage V_x given in network shown in Fig. 9 is

- a. 3
- b. 4
- c. 5
- d. 6

- a.
- b.
- c.
- d.

No, the answer is incorrect.
 Score: 0
 Accepted Answers: b.

12) If $R_1 = R_2 = R_4 = R$ and $R_3 = 1.1R$ in the network shown in Fig. 10. The voltage between terminals a and b is? 0 points



Fig. 10

- a. 0.22 - 0.26
- b. 0.54 - 0.58
- c. 0.35 - 0.39
- d. 0.45 - 0.49

- a.
- b.
- c.
- d.

No, the answer is incorrect.
 Score: 0
 Accepted Answers: a.