


Unit 8 - Week 6

Course outline
How to access the portal
Week 0 Assignment 0
Week 1
Week 2
Week 3
Week 4
Week 5
Week 6
<ul style="list-style-type: none"> Lecture No 26:Capacitors & Inductors (Contd.) Lecture No 27:Capacitors & Inductors (Contd.) Lecture No 28:Capacitors & Inductors (Contd.) Lecture No 29:First Order Circuits Lecture No 30:First Order Circuits (Contd.) Lecture Material Feedback for Week 6 Quiz : Week 6 Assignment 6
Week 7
Week 8
Week 9
Week 10
Week 11
Week 12
Download Videos
Detail Solution

Week 6 Assignment 6

The due date for submitting this assignment has passed. As per our records you have not submitted this assignment. **Due on 2019-09-11, 23:59 IST.**

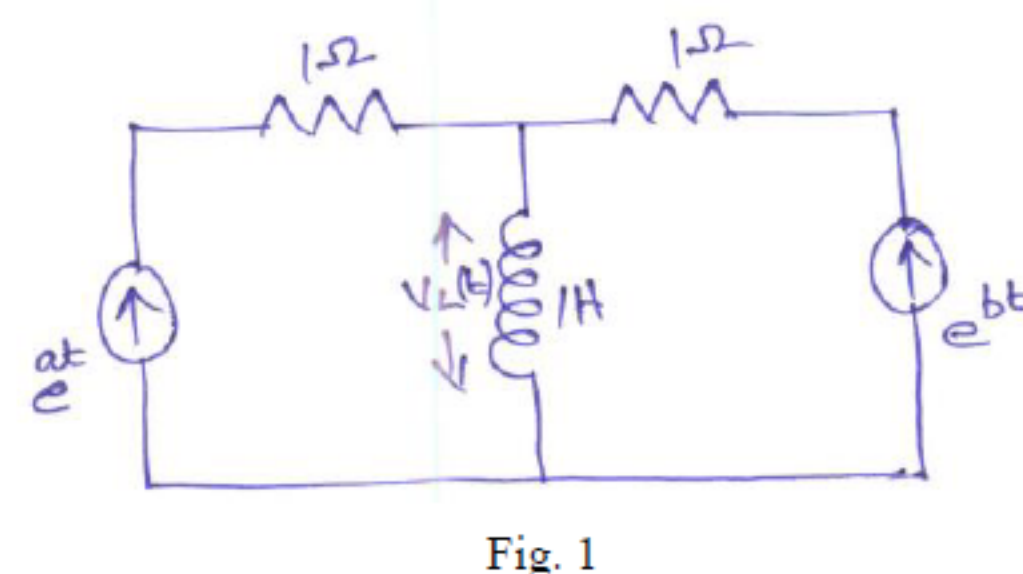1) The voltage $V_L(t)$ (in V) across the inductor in the network shown in Fig. 1 is




- a. $e^{at} - e^{bt}$
- b. $e^{at} + e^{bt}$
- c. $ae^{at} - be^{bt}$
- d. $ae^{at} + be^{bt}$

- a.
- b.
- c.
- d.

No, the answer is incorrect. Score: 0

Accepted Answers: d.

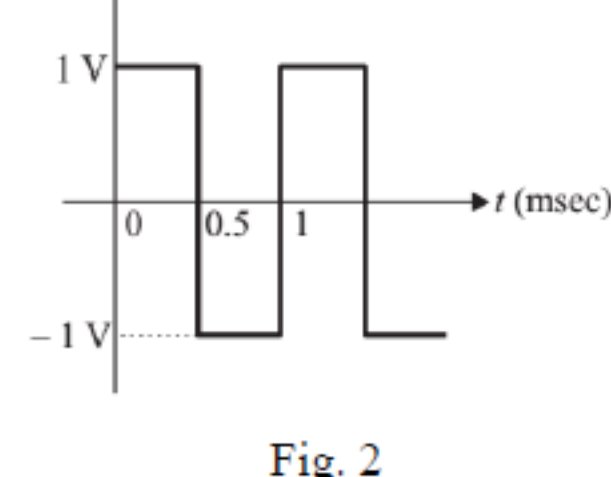2) A square waveform as shown in Fig. 2 is applied across 1 mH ideal inductor. The current through inductor will be?



- a. triangular wave with peak amplitude of 0.5 Amp.
- b. triangular wave with peak amplitude of 1.0 Amp.
- c. triangular wave with peak amplitude of 2.0 Amp.
- d. sine wave with peak amplitude of 0.5 Amp.

- a.
- b.
- c.
- d.

No, the answer is incorrect. Score: 0

Accepted Answers: a.

3) After how many time constants, the transient part in series RL excited with dc voltage will reach more than 99 percent of its final value?


- a. 2
- b. 3
- c. 4
- d. 5

- a.
- b.
- c.
- d.

No, the answer is incorrect. Score: 0

Accepted Answers: d.

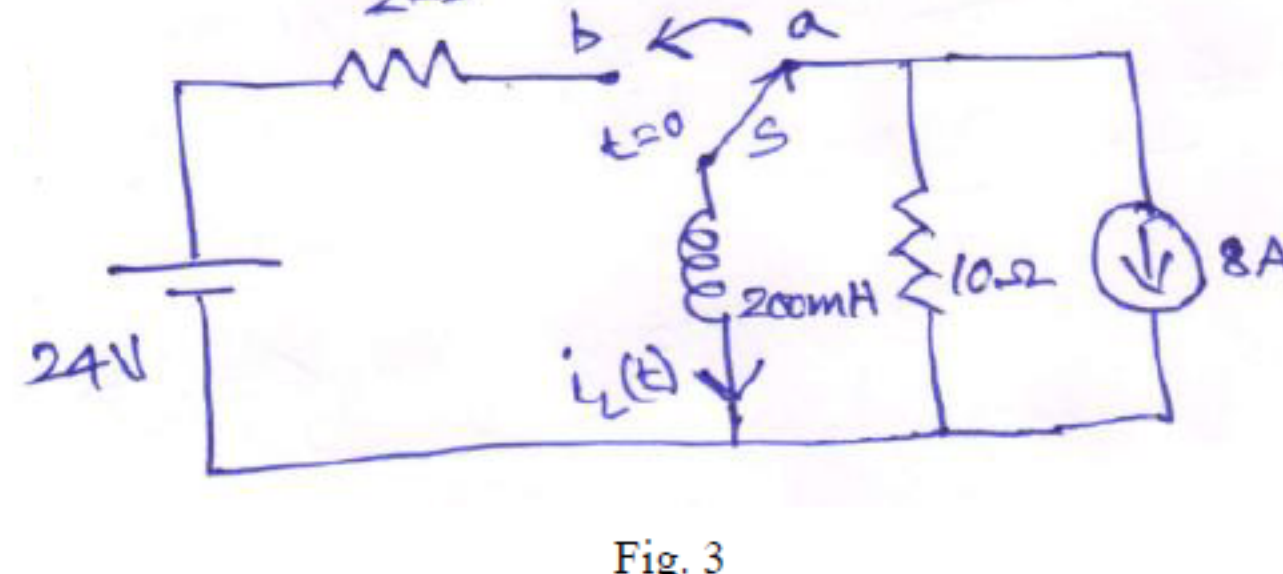4) The switch in the circuit shown in Fig. 3 has been in position 'a' for long time. At $t = 0$, the switch moves from position 'a' to position 'b'. The expression for current in inductor for $t > 0$




- a. $12 - 20e^{-10t}$
- b. $12 + 20e^{-10t}$
- c. $20 - 12e^{-10t}$
- d. $20 + 12e^{-10t}$

- a.
- b.
- c.
- d.

No, the answer is incorrect. Score: 0

Accepted Answers: a.

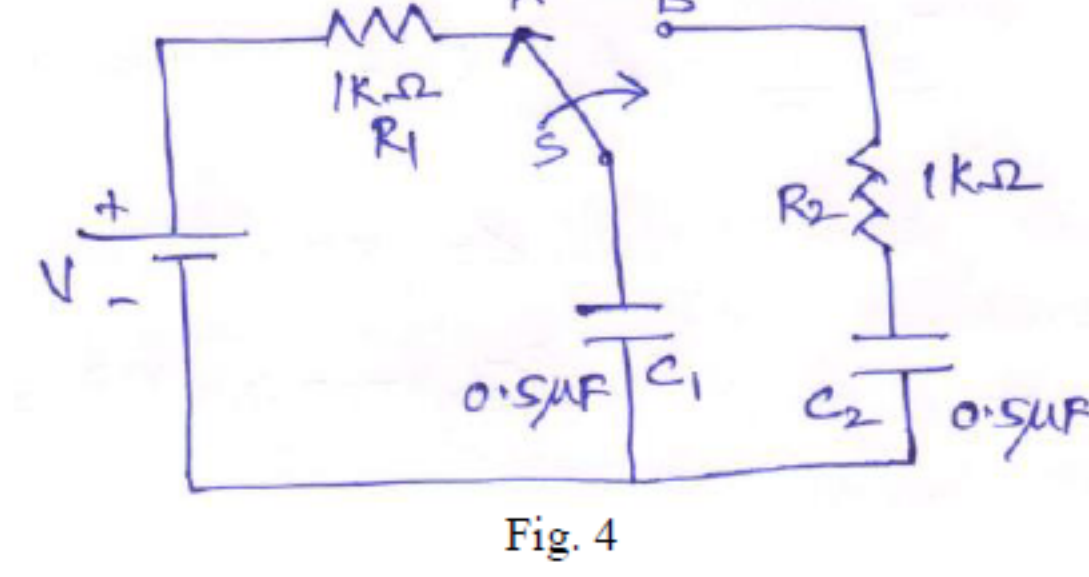5) For the circuit shown in Fig. 4 different time constants (in seconds) are given as



- 1. 0.5×10^{-3}
- 2. 2×10^{-3}
- 3. 0.25×10^{-3}
- 4. 1×10^{-3}

What are the charging and discharging time constants of capacitor C_1 respectively?


- a. 1, 2
- b. 2, 3
- c. 1, 3
- d. 2, 4

- a.
- b.
- c.
- d.

No, the answer is incorrect. Score: 0

Accepted Answers: c.

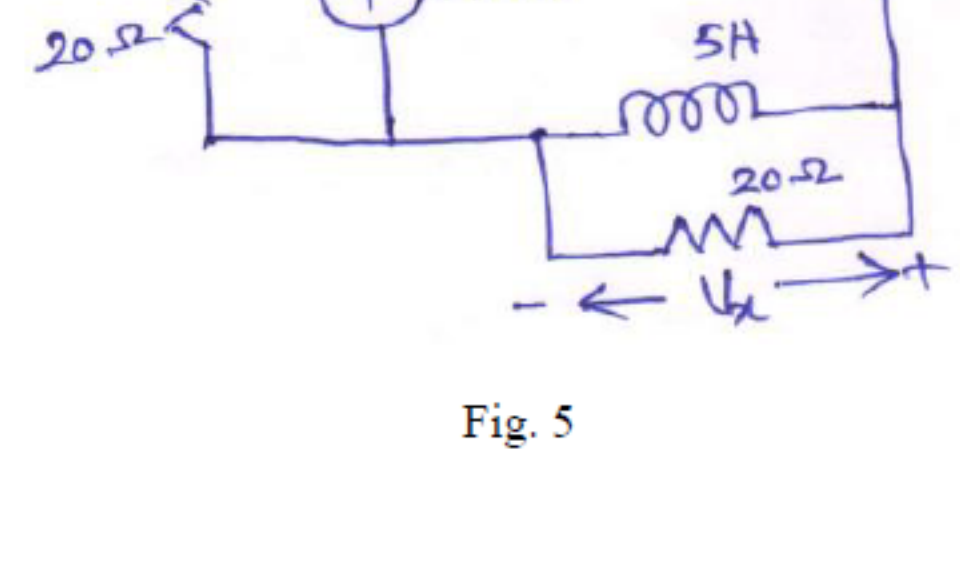6) In Fig. 5, the switch was closed for a long time before opening at $t = 0$. The voltage V_x at $t = 0^+$ will be?




- a. 25 V
- b. 50 V
- c. -50 V
- d. 0 V

- a.
- b.
- c.
- d.

No, the answer is incorrect. Score: 0

Accepted Answers: c.

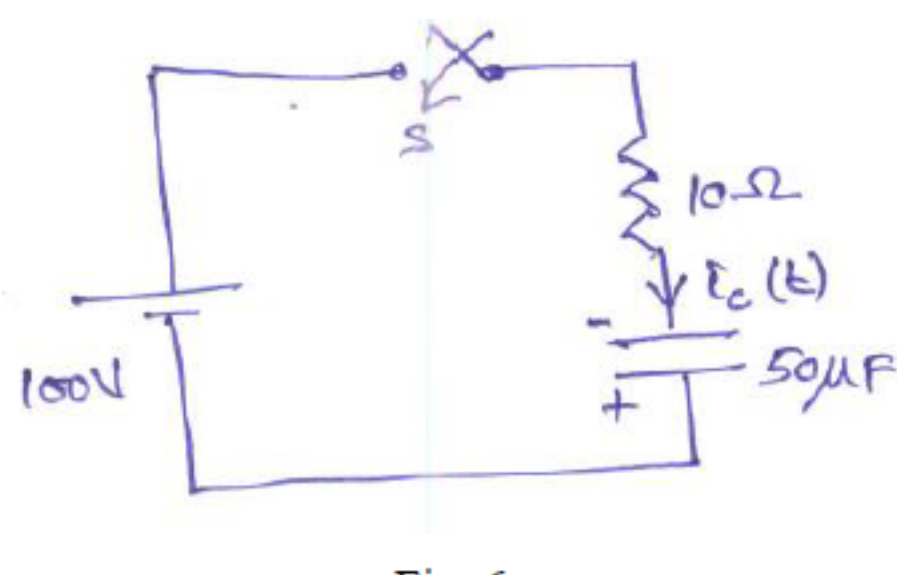7) In the circuit shown in Fig. 6, the initial charge on the capacitor is 2.5 milli Coulombs, with the voltage polarity as indicated. The switch is closed at time $t = 0$. The current $i(t)$ at time t after the switch is closed is




- a. $i(t) = 15e^{-2 \times 10^2 t}$
- b. $i(t) = 5e^{-2 \times 10^2 t}$
- c. $i(t) = 15e^{2 \times 10^2 t}$
- d. $i(t) = 5e^{2 \times 10^2 t}$

- a.
- b.
- c.
- d.

No, the answer is incorrect. Score: 0

Accepted Answers: a.

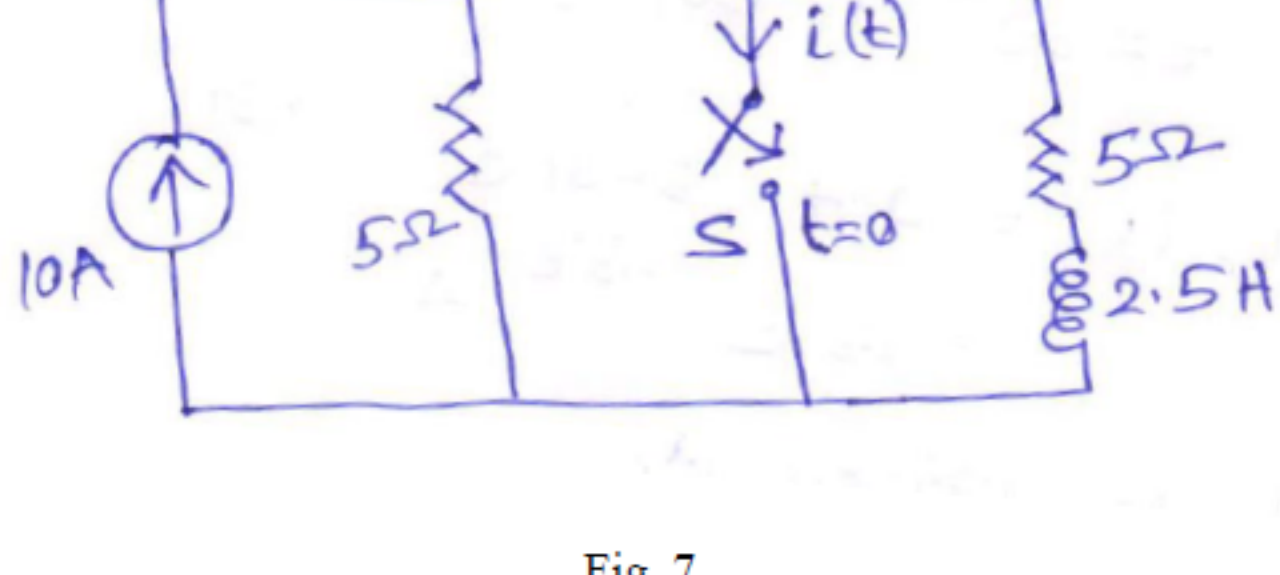8) The switch in the circuit shown in the Fig. 7, was open for a long time and is closed at $t = 0$. The current $i(t)$ flowing through switch (in Ampere) at $t = 0.5$ sec is ?




- a. 15.31 - 15.35 A
- b. 8.14 - 8.18 A
- c. 27.64 - 27.68 A
- d. 53.80 - 53.84 A

- a.
- b.
- c.
- d.

No, the answer is incorrect. Score: 0

Accepted Answers: b.

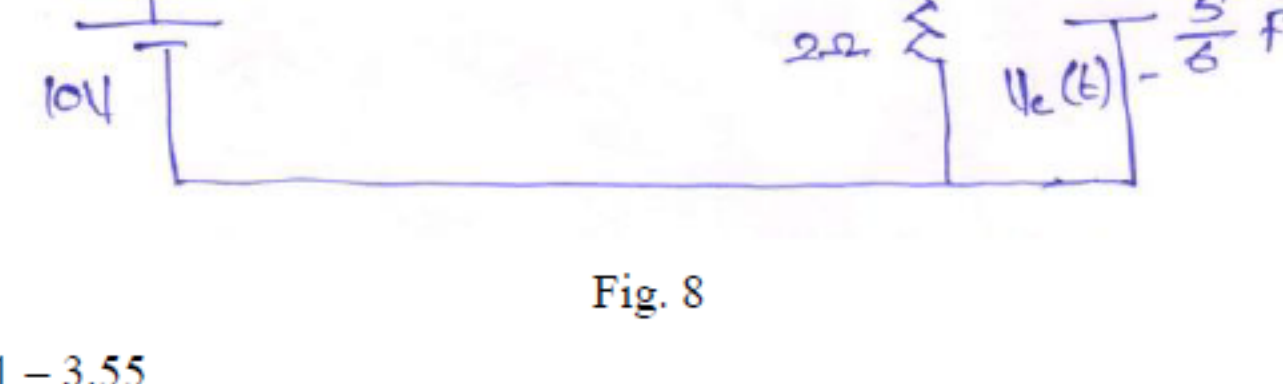9) In the circuit shown in Fig. 8, the switch is closed at $t = 0$. Assuming zero initial conditions the value of $V_c(t)$ (in volts) at $t = 1$ sec is?




- a. 3.51 - 3.55
- b. 2.51 - 2.55
- c. 4.51 - 4.55
- d. 5.51 - 5.55

- a.
- b.
- c.
- d.

No, the answer is incorrect. Score: 0

Accepted Answers: b.

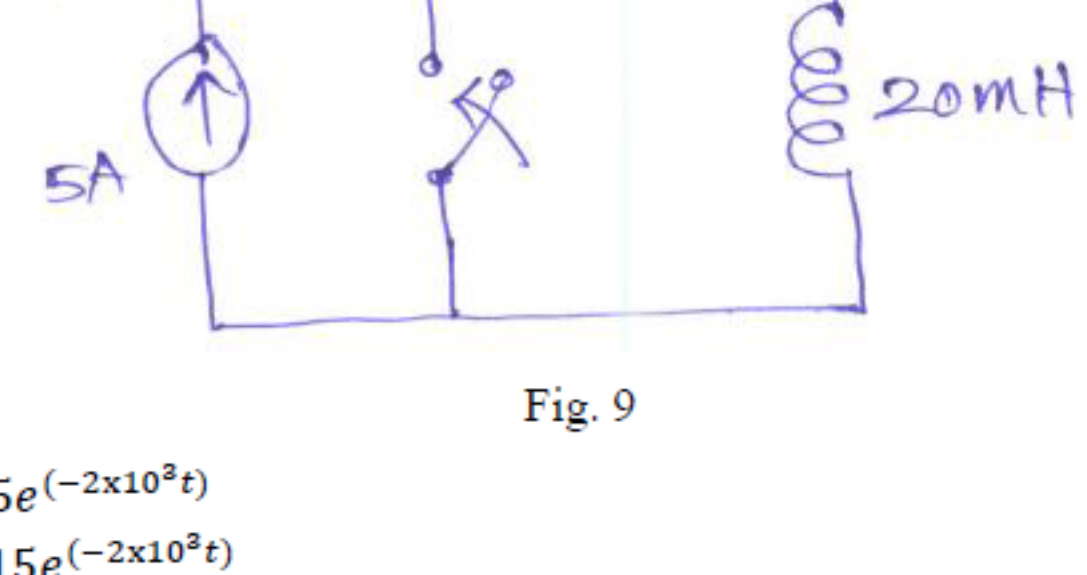10) At instant $t = 0$ the switch is closed in the circuit shown in Fig. 9. The current flowing (in Amp) in the inductor after switching is?



- a. $i(t) = 5e^{-2 \times 10^2 t}$
- b. $i(t) = 15e^{-2 \times 10^2 t}$
- c. $i(t) = 15e^{2 \times 10^2 t}$
- d. $i(t) = 5e^{2 \times 10^2 t}$

- a.
- b.
- c.
- d.

No, the answer is incorrect. Score: 0

Accepted Answers: a.

11) Consider a DC voltage source connected to a series R-C circuit. When the steady state reaches, the ratio of the energy stored in the capacitor to the total energy supplied by the voltage source, is equal to

- a. 0.362
- b. 0.770
- c. 1
- d. 0.5

- a.
- b.
- c.
- d.

No, the answer is incorrect. Score: 0

Accepted Answers: d.

12) At $t = 0$, suddenly a dc voltage of 30V, is applied to an initially relaxed series RL circuit having $R = 12 \Omega$ and $L = 18H$. The energy stored (in Joules) in the magnetic field at $t = 3$ sec is

- a. 48.2 - 50.2
- b. 12.8 - 14.8
- c. 41.1 - 43.1
- d. 52.2 - 54.2

- a.
- b.
- c.
- d.

No, the answer is incorrect. Score: 0

Accepted Answers: c.