

Unit 10 - Week 8

Course outline	
How to access the portal	
Week 0 Assignment 0	
Week 1	
Week 2	
Week 3	
Week 4	
Week 5	
Week 6	
Week 7	
Week 8	<ul style="list-style-type: none"> Lecture 37 : Single phase AC circuits Lecture 38 : Single phase AC circuits (Contd.) Lecture 39 : Single phase AC circuits (Contd.) Lecture 40 : Single phase AC circuits (Contd.) Lecture 41 : Single phase AC circuits (Contd.) Lecture 42 : Single phase AC circuits (Contd.) Lecture Materials Feedback for Week 8 Quiz : Week 8 Assignment 8
Week 9	
Week 10	
Week 11	
Week 12	
Download Videos	
Detail Solution	

Week 8 Assignment 8

The due date for submitting this assignment has passed. As per our records you have not submitted this assignment.

Due on 2019-09-25, 23:59 IST.

1) The parameters of a series RLC circuit are as follows:
 $R=5 \Omega$, $C=3.28 \mu\text{F}$ and $L=48.3925 \text{ mH}$.

The circuit is excited by a voltage source $V_s(t)=10 \sin(2510t)$ volts. Find $i(t)$ (in A) in the circuit.

- $2 \cos(2510t)$
- $-2 \cos(2510t)$
- $2 \sin(2510t)$
- $-2 \sin(2510t)$

- a.
 b.
 c.
 d.

No, the answer is incorrect.
 Score: 0
 Accepted Answers:
 c.

2) The crest factor (or peak factor) of a sinusoidal wave is:

- 1.414
- 1.11
- 2.0
- 1.5

- a.
 b.
 c.
 d.

No, the answer is incorrect.
 Score: 0
 Accepted Answers:
 a.

3) The r.m.s value of the resultant current (in A) in a wire which carries a DC current of 8 A and a sinusoidal alternating current of peak value 8.485A is approximately

- 8.25
- 9.50
- 10.4
- 10.0

- a.
 b.
 c.
 d.

No, the answer is incorrect.
 Score: 0
 Accepted Answers:
 c.

4) In a series RLC circuit, $R=5 \text{ ohms}$, $X_L=20 \text{ ohms}$, $X_C=25 \text{ ohms}$ at 50Hz frequency. If the circuit is connected to a voltage source $V(t) = 100 \sin(314t + 30^\circ)$ Volts, the rms value of the current (in A) will be approximately equal to

- 3.33
- 5
- 10
- 14.14

- a.
 b.
 c.
 d.

No, the answer is incorrect.
 Score: 0
 Accepted Answers:
 c.

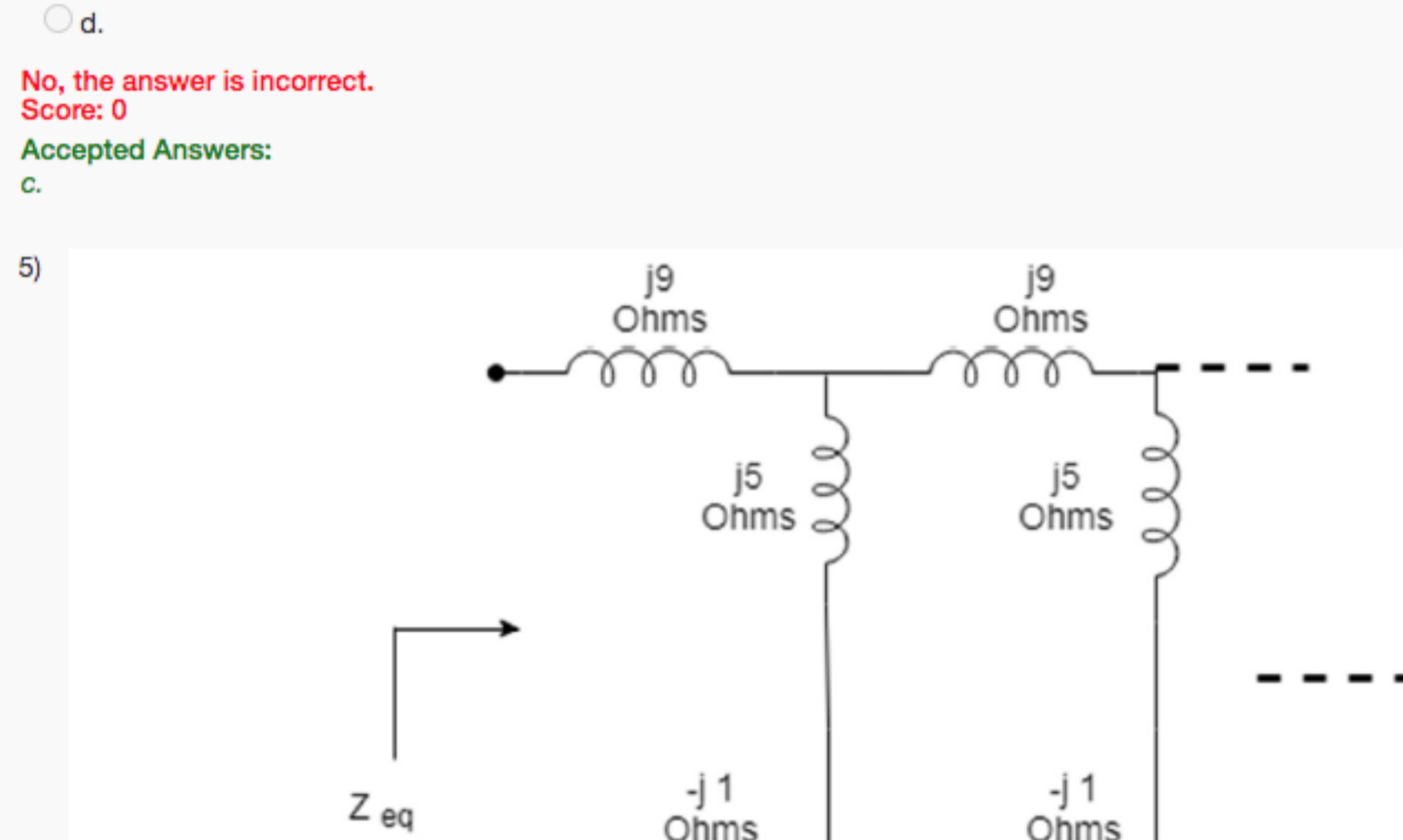


Fig.5

The equivalent impedance Z_{eq} (in Ω) of the infinite ladder circuit shown in Fig.5 is:

- $-j12$
- $j12$
- $j13$
- $-j13$

- a.
 b.
 c.
 d.

No, the answer is incorrect.
 Score: 0
 Accepted Answers:
 b.

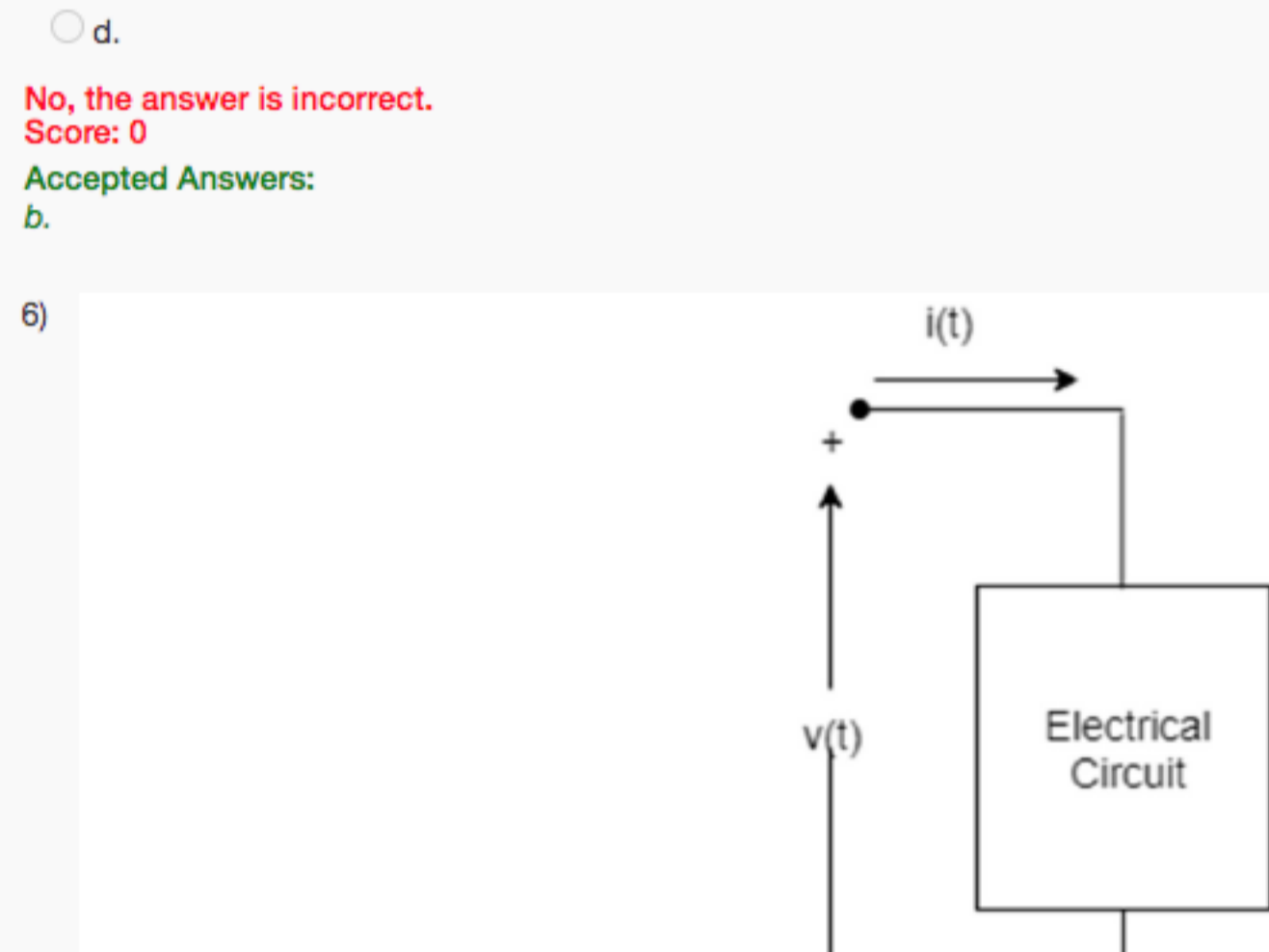


Fig.6

The voltage across an electrical network shown in Fig.6 $v(t)$, and the current $i(t)$ through it are expressed as follows:

$$V(t) = [5 - 10 \cos(\omega t + 60^\circ)] V ; \quad i(t) = [5 + X \cos(\omega t)] A$$

Where $\omega = 150\pi \text{ rad/s}$. If the average power delivered to the circuit is zero, find the value of X (in A)

- 0
- 5
- 5.77
- 10

- a.
 b.
 c.
 d.

No, the answer is incorrect.
 Score: 0
 Accepted Answers:
 d.

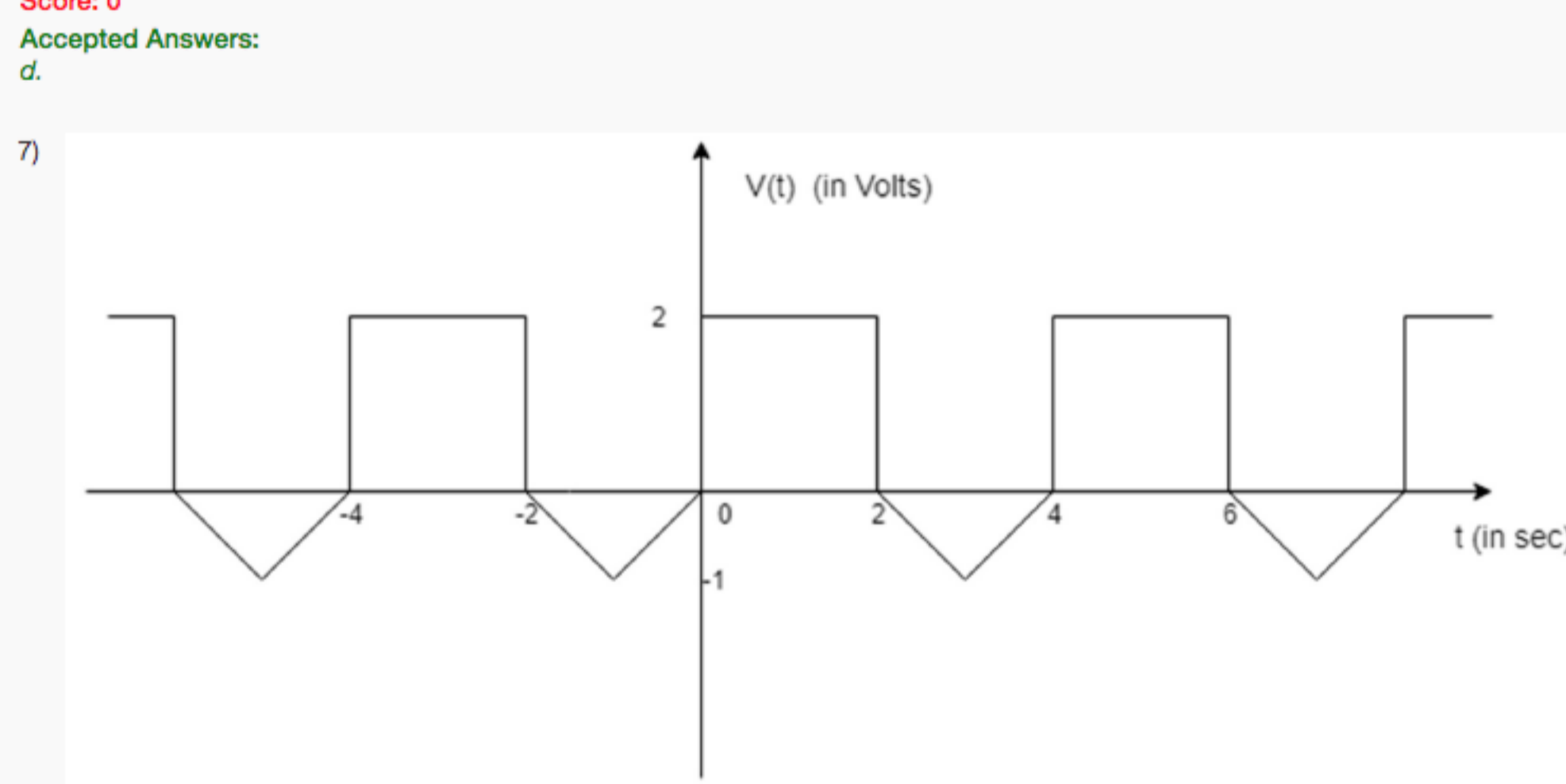


Fig.7

Determine the full cycle average value (in Volts) of the voltage waveform shown in Fig.7

- 0.75
- 1.25
- 3.00
- None of the above

- a.
 b.
 c.
 d.

No, the answer is incorrect.
 Score: 0
 Accepted Answers:
 a.

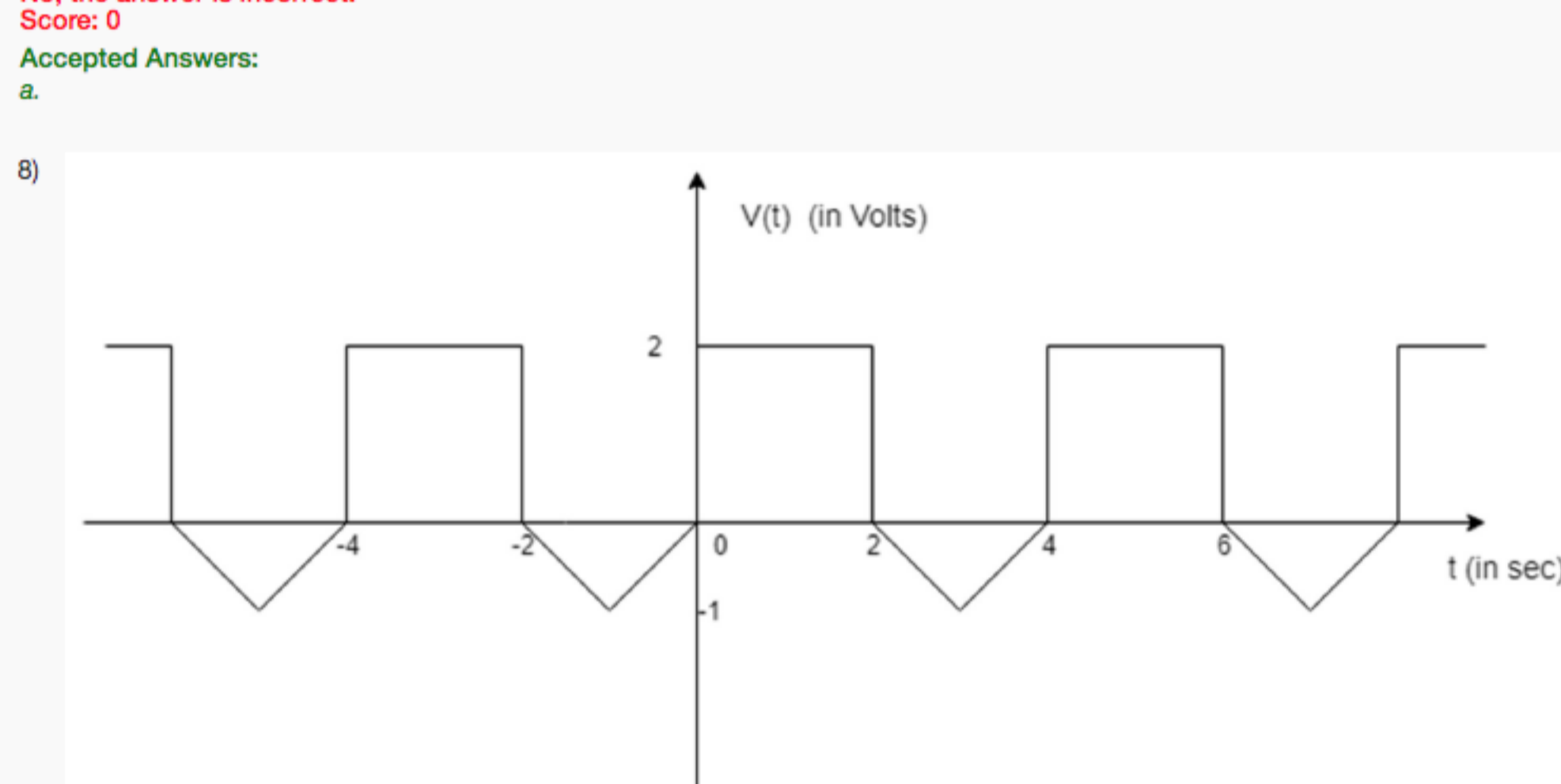


Fig.8

Determine the rms value (in Volts) of the voltage waveform shown in Fig.8

- $\sqrt{\frac{26}{3}}$
- $\sqrt{\frac{13}{6}}$
- $\sqrt{\frac{5}{4}}$
- None of the above

- a.
 b.
 c.
 d.

No, the answer is incorrect.
 Score: 0
 Accepted Answers:
 b.

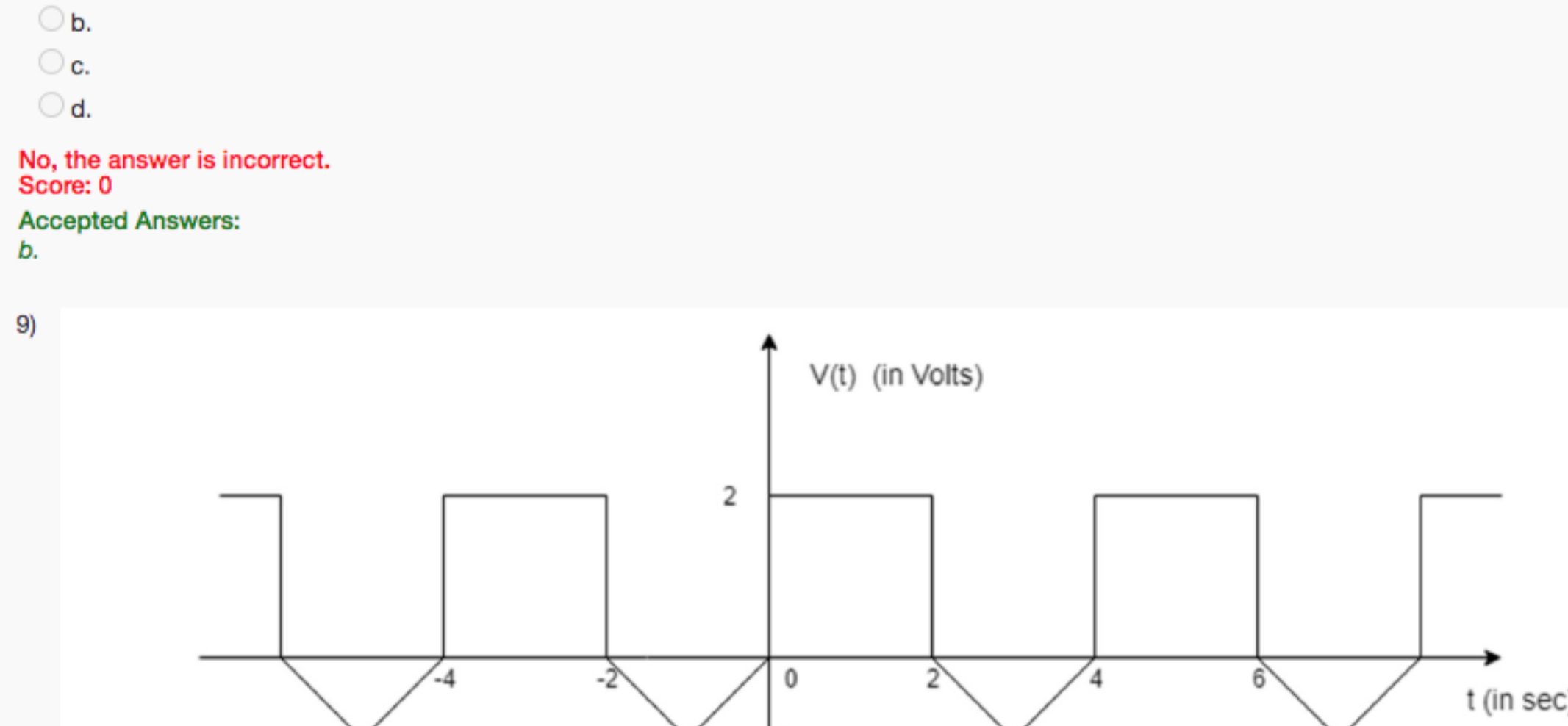


Fig.9

The voltage waveform shown in Fig.9 is passed through a 1.3Ω resistor. Find out the average power (in W) dissipated in the resistor.

- 1.65 - 1.67
- 1.72 - 1.74
- 6.65 - 6.67
- 2.80 - 2.82

- a.
 b.
 c.
 d.

No, the answer is incorrect.
 Score: 0
 Accepted Answers:
 a.

10) An LCR series circuit with $R=100 \Omega$ is connected to a 200 V, 50 Hz a.c source. When only the capacitor is removed, the voltage leads the current by 60° . When only the inductor is removed, the current leads the voltage by 60° . The current (in A) in the circuit when all three elements are connected in series is:

- $\frac{2}{\sqrt{3}}$
- $\frac{\sqrt{3}}{2}$
- 1.0
- 2.0

- a.
 b.
 c.
 d.

No, the answer is incorrect.
 Score: 0
 Accepted Answers:
 d.

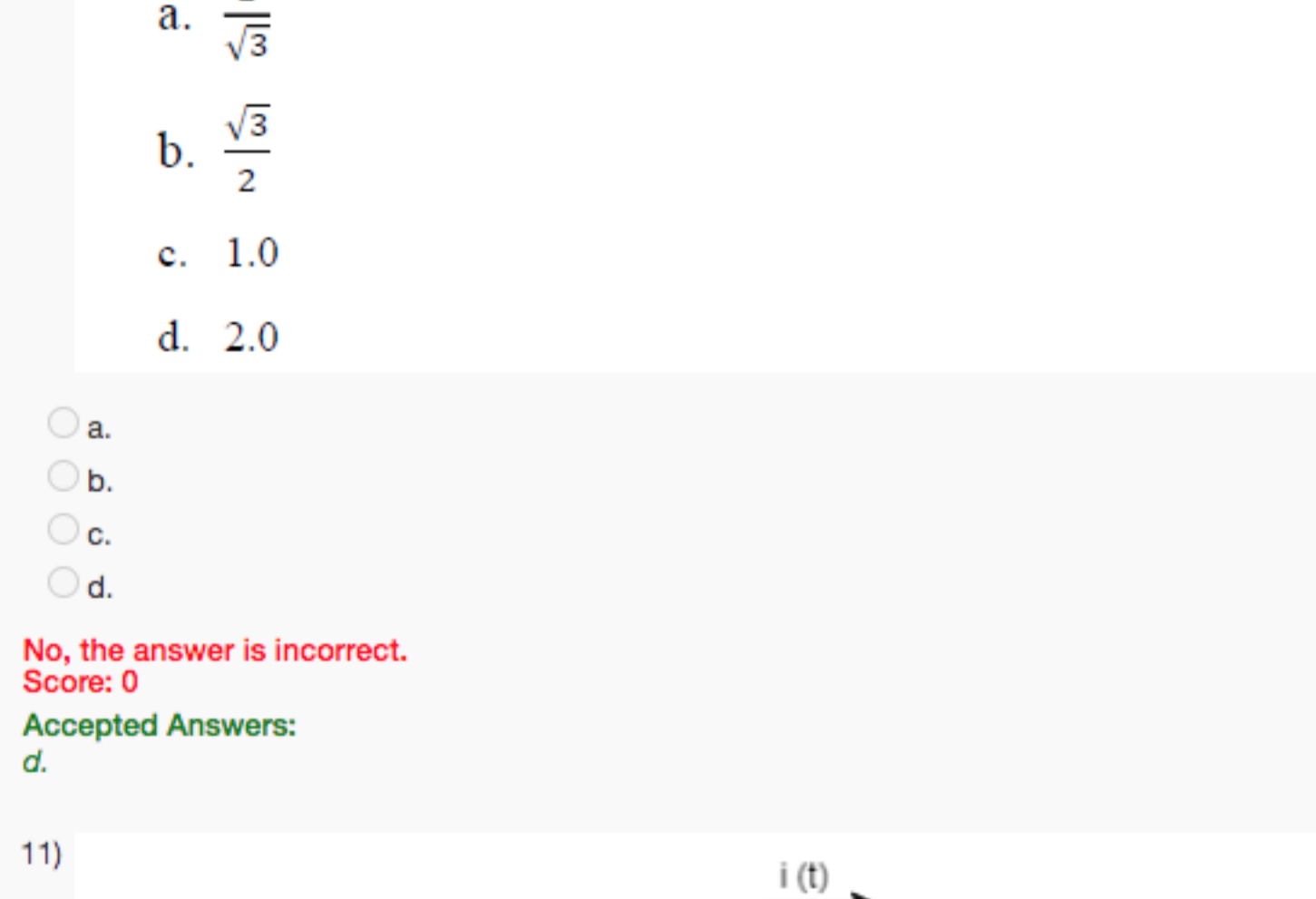


Fig.11

In the circuit shown in Fig.11, $V_s(t) = \cos(2.5t)$ Volts, $Z = (2+j2)$ ohms, C is so chosen that the current $i(t)$ is in phase with the supply voltage $V_s(t)$. Find the value of the capacitor C (in F).

- 1.00
- 0.10
- 10.0
- None of the above

- a.
 b.
 c.
 d.

No, the answer is incorrect.
 Score: 0
 Accepted Answers:
 b.

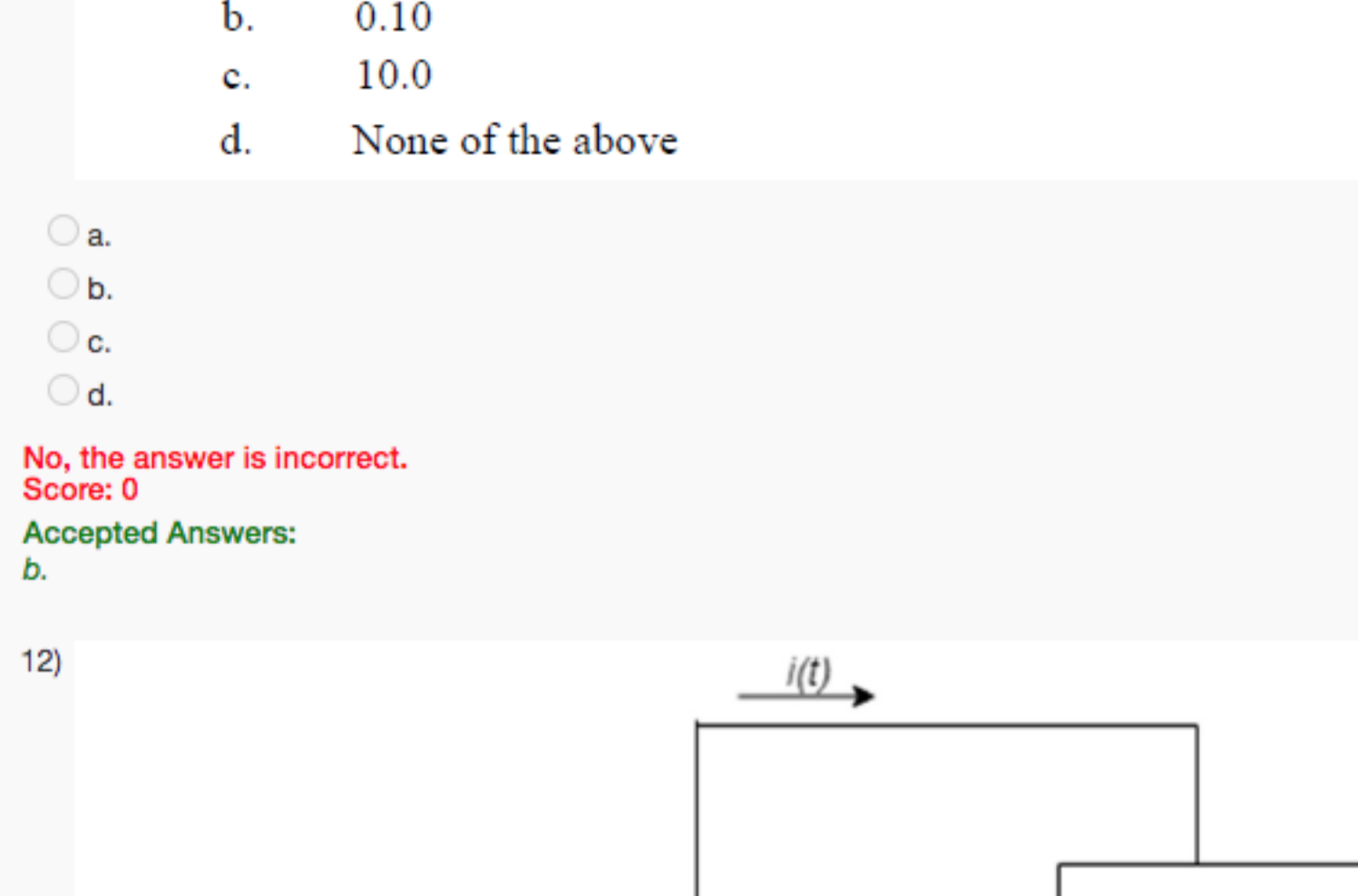


Fig.12

In the linear circuit shown in Fig.12, when $v(t) = 5 \cos(500t)$ Volts, $i(t) = 0.4 \cos(500t - 30^\circ)$ A. Calculate $i(t)$ (in A) when $v(t) = 5 \sin(1000t)$ Volts.

- $0.3024 \cos(1000t - 49.11^\circ)$
- $0.4 \sin(1000t - 30^\circ)$
- $0.3024 \sin(1000t - 49.11^\circ)$
- $0.4 \sin(1000t - 49.11^\circ)$

- a.
 b.
 c.
 d.

No, the answer is incorrect.
 Score: 0
 Accepted Answers:
 c.