

X

<https://swayam.gov.in>[https://swayam.gov.in/nc\\_details/NPTEL](https://swayam.gov.in/nc_details/NPTEL)

reviewer4@nptel.iitm.ac.in ▾

**NPTEL (<https://swayam.gov.in/explorer?ncCode=NPTEL>) » Architectural Design of Digital Integrated Circuits (course)**

Announcements (announcements)

**About the Course ([https://swayam.gov.in/nd1\\_noc20\\_ee37/preview](https://swayam.gov.in/nd1_noc20_ee37/preview))** Ask a Question (forum)

Progress (student/home) Mentor (student/mentor)

---

**Due on 2020-02-28, 23:59 IST**

1. Draw the architecture (serial and parallel) of a circuit which can compute the minimum number amongst 4 different numbers.
2. Draw the architecture (serial and parallel) of a circuit which can compute the maximum number amongst 4 different numbers.
3. Derive the logical expression for one 5-bit incrementer circuits which can increment at every step by a factor of 2. Draw the architecture of the particular circuit.
4. Derive the logical expression for one 5-bit decremter circuits which can increment at every step by a factor of 2. Draw the architecture of the particular circuit.
5. Draw the architecture of one controlled 1's complement and 2's complement circuit.

## Your Submission:

The due date for submitting this assignment has passed.  
As per our records you have not submitted this assignment.

