

Unit 4 - WEEK 2

Course outline

How does an NPTEL online course work?

Week 0 Assignment 0

WEEK 1

WEEK 2

- Lecture 07 : Revisiting BJT Characteristic
- Lecture 08 : Revisiting BJT Characteristic (Contd.)
- Lecture 09 : Revisiting BJT Characteristic (Contd.)
- Lecture 10 : Revisiting MOSFET
- Lecture 11 : Revisiting MOSFET (Contd.)
- Lecture 12 : Revisiting MOSFET (Contd.)
- Lecture 13 : Revisiting MOSFET (Contd.)
- Quiz : Week 2 Assignment 2
- Week 2 Lecture material
- Week 2 Feedback Form

WEEK 3

WEEK 4

WEEK 5

WEEK 6

WEEK 7

WEEK 8

WEEK 9

WEEK 10

WEEK 11

WEEK 12

Supplementary material

Download Videos

Detail solution

Live Interactive Session

Text Transcripts

Week 2 Assignment 2

The due date for submitting this assignment has passed. **Due on 2020-02-12, 23:59 IST.**
As per our records you have not submitted this assignment.

1) For the circuit shown in Fig 2.1, find the closest value of V_B by considering $V_{EB(om)} \approx 0.6$ V and $\beta = 99$. Select the correct option from the following:

Fig 2.1

a) 11.4 V
b) -9.87 V
c) 2.127 V
d) 1.036 V
e) 5.7 V

a)
 b)
 c)
 d)
 e)

No, the answer is incorrect.
Score: 0
Accepted Answers: d)

2) For the circuit shown in Fig 2.1, find the value of V_C . Select the correct option from the following:

a) -1.74 V b) 10.26 V c) 0.3 V d) 0 V e) -1.23 V

a)
 b)
 c)
 d)
 e)

No, the answer is incorrect.
Score: 0
Accepted Answers: a)

3) The V-I characteristics of an NPN transistor in active region of operation is given in Table 2.1.

$V_{BE}(V)$	0.50	0.51	0.52	0.53	0.54	0.55	0.56	0.57	0.58	0.59
$I_B(\mu A)$	0.48	0.72	1.08	1.61	2.40	3.58	5.35	7.98	11.90	17.76
$I_C(mA)$	0.096	0.144	0.22	0.322	0.48	0.716	1.07	1.596	2.38	3.552

Table 2.1

Then, find the closest input resistance (in $K\Omega$) value of the transistor for $V_{BE} = 0.535$ V. Select the correct option from the following:

a) 3.80 b) 2.55 c) 26.32 d) 1.887 e) 12.66

a)
 b)
 c)
 d)
 e)

No, the answer is incorrect.
Score: 0
Accepted Answers: e)

4) From the V-I characteristics of Table 2.1, find the value of transconductance, g_m for $V_{BE} = 0.515$ V. Select the correct option from the following:

a) 23.6 mS d) 10.2 mS
b) 35.4 mS e) 4.8 mS
c) 7.9 mS f) 7.6 mS

a)
 b)
 c)
 d)
 e)
 f)

No, the answer is incorrect.
Score: 0
Accepted Answers: f)

5) For the circuit shown in the Fig 2.2, identify the correct I - V characteristics from given options:

Fig 2.2

a) b)
c) d)
e)

a)
 b)
 c)
 d)
 e)

No, the answer is incorrect.
Score: 0
Accepted Answers: b)
c)

6) For the circuit shown in Fig 2.3, consider $\mu_n \frac{\epsilon_{ox} W}{t_{ox} L} = K_n = 0.5 \text{ mA/V}^2$, $V_{thn} = -0.5$ V, $\lambda \approx 0 \text{ V}^{-1}$, $R_1 = R_2 = 10 \text{ k}\Omega$. Find the maximum value of resistor, R (in $k\Omega$) such that the p-channel remains in pinched off condition. (i.e., the device remains in saturation region of operation). Select the correct option from the following:

Fig 2.3

a) 12 d) 10
b) 24 e) 3.4
c) 5.6

a)
 b)
 c)
 d)
 e)

No, the answer is incorrect.
Score: 0
Accepted Answers: b)

7) For the circuit shown in Fig 2.4, consider the values of device parameters: $\mu_n \frac{\epsilon_{ox} W}{t_{ox} L} = K_n = 1 \text{ mA/V}^2$, $V_{thn} = 0.5$ V, $\lambda \approx 0 \text{ V}^{-1}$. Find the value of resistor R_2 (in $k\Omega$) to get $I_{DS} = 100 \mu A$. Select the correct option from the following:

Fig 2.4

a) 12 d) 11
b) 9 e) 18
c) 6

a)
 b)
 c)
 d)
 e)

No, the answer is incorrect.
Score: 0
Accepted Answers: d)

8) Find the "output resistance, r_o " looking into collector terminal of the transistor given in Fig 2.5. Considering $V_{BE(on)} \approx 0.7$ V, $\beta = 120$ and the early voltage $V_A = 48$ V. Select the correct option from the following:

Fig 2.5

a) 100 $k\Omega$ d) 6.48 $k\Omega$
b) 75 $k\Omega$ e) 54 $k\Omega$
c) 50 $k\Omega$

a)
 b)
 c)
 d)
 e)

No, the answer is incorrect.
Score: 0
Accepted Answers: a)

9) Calculate the closest value of V_{EB} for $I_C = 0.5$ mA. Given, the reverse saturation current of PNP transistor $I_S^{(C)} = 10^{-12}$ mA, $\beta = 80$, thermal equivalent voltage $V_T = 25$ mV and early voltage is very high. Select the correct option from the following:

a) 633.53 mV d) 668.97 mV
b) 643.65 mV e) 673.44 mV
c) 656.72 mV f) 688.34 mV

a)
 b)
 c)
 d)
 e)
 f)

No, the answer is incorrect.
Score: 0
Accepted Answers: e)

10) For the circuit shown in Fig 2.6, consider $K = \mu_n C_{ox} = 120 \mu A/V^2$, $W = 8 \mu m$, $L = 1 \mu m$, $V_{thn} = 0.5$ V, $\lambda \approx 0 \text{ V}^{-1}$. Find the required value of R to get $I_{DS} = 120 \mu A$? Select the correct option from the following:

Fig 2.6

a) 33.33 $k\Omega$ d) 25 $k\Omega$
b) 15 $k\Omega$ e) 50 $k\Omega$
c) 16.66 $k\Omega$ f) 20.83 $k\Omega$

a)
 b)
 c)
 d)
 e)
 f)

No, the answer is incorrect.
Score: 0
Accepted Answers: d)

11) For the circuit shown in Fig 2.7, consider $V_{thn} = 0.4$ V and $V_{thp} = -0.5$ V. Find the range of V_{DDC} such that both NMOS and PMOS transistors are in saturation region. Select the correct option from the following:

Fig 2.7

a) 0.4 V to 1.3 V
b) 0.4 V to 1.4 V
c) 0.5 V to 1.4 V
d) 0.4 V to 1.5 V
e) 0.5 V to 1.3 V

a)
 b)
 c)
 d)
 e)

No, the answer is incorrect.
Score: 0
Accepted Answers: c)

12) Find the minimum base current (I_B) required to drive the transistor in saturation as shown in Fig 2.8. Given, $V_{CE(sat)} = 0.2$ V and $\beta = 100$. Select the correct option from the following:

Fig 2.8

a) 14 μA d) 15 μA
b) 20 μA e) 30 μA
c) 28 μA

a)
 b)
 c)
 d)
 e)

No, the answer is incorrect.
Score: 0
Accepted Answers: a)

13) For the circuit shown in Fig 2.9, consider $\alpha = 0.99$ and $V_{BE} = 0.7$ V. Find the value of collector current? Select the correct option from the following:

Fig 2.9

a) 1.55 mA d) 31.31 μA
b) 3.1 mA e) 9.3 mA
c) 93.93 μA

a.
 b.
 c.
 d.
 e.

No, the answer is incorrect.
Score: 0
Accepted Answers: b.