

Unit 3 - Week 1

Course outline

How does an NPTEL online course work?

Week 0

Week 1

- Introduction to PMIC - Part 1
- Introduction to PMIC - Part 2
- Linear versus Switching Regulators
- Performance Parameters of Regulators
- Local versus Remote Feedback, Point-of-Load Regulators
- Kelvin Sensing, Droop Compensation
- Current Regulator Applications, Introduction to Bandgap Voltage References, PTAT and CTAT Voltages
- Adding PTAT and CTAT Voltages
- Bandgap Voltage Reference Circuit, Brokaw Bandgap Circuit

○ Quiz : Assignment 1

○ Week 1 Feedback

● Supplementary material

Week 2

Week 3

Week 4

Week 5

Week 6

Week 7

Week 8

Week 9

Week 10

Week 11

Week 12

Download Videos

Assignment solutions

Assignment 1

The due date for submitting this assignment has passed.
As per our records you have not submitted this assignment.

Due on 2020-02-12, 23:59 IST.

1) State whether the following statement is true or false. "The efficiency of a switching regulator can be lower than that of a linear regulator." 1 point

- True
 False

No, the answer is incorrect.
Score: 0

Accepted Answers:
True

2) State whether the following statement is true or false. "The temperature coefficient of the resistors used in a bandgap circuit must be zero so as to achieve a temperature-independent voltage reference." 1 point

- True
 False

No, the answer is incorrect.
Score: 0

Accepted Answers:
False

3) State whether the following statement is true or false. "The curvature in the output voltage of a bandgap reference circuit occurs mainly due to the non-linearity in the PTAT current." 1 point

- True
 False

No, the answer is incorrect.
Score: 0

Accepted Answers:
False

4) State whether the following statement is true or false. "Droop compensation cannot be used to improve the DC accuracy of a regulator." 1 point

- True
 False

No, the answer is incorrect.
Score: 0

Accepted Answers:
True

5) State whether the following statement is true or false. "Switching regulators offer high efficiency over a wide range of the conversion ratio V_O/V_{IN} because conduction losses depend on $(V_{IN} - V_O)$." 1 point

- True
 False

No, the answer is incorrect.
Score: 0

Accepted Answers:
False

6) State whether the following statement is true or false. "Linear regulators with a high dropout voltage are efficient when the load current is small." 1 point

- True
 False

No, the answer is incorrect.
Score: 0

Accepted Answers:
False

7) State whether the following statement is true or false. "Switching regulators are preferred in noise-sensitive applications." 1 point

- True
 False

No, the answer is incorrect.
Score: 0

Accepted Answers:
False

8) State whether the following statement is true or false. "The total power loss in a switching regulator operating at an efficiency of 93% with $V_{IN} = 1.8$ V, $V_O = 1.5$ V and delivering a load current of 1 A is 300 mW." 1 point

- True
 False

No, the answer is incorrect.
Score: 0

Accepted Answers:
False

9) State whether the following statement is true or false. "Droop compensation calls for the output to be regulated slightly above the required value at full load." 1 point

- True
 False

No, the answer is incorrect.
Score: 0

Accepted Answers:
False

10) A power management module comprises two regulators with the following specifications. Both regulators operate from a common supply voltage of 1.8 V.
Regulator 1: Linear, $V_O = 1.5$ V, $I_{LOAD} = 500$ mA, $\eta = 83.3\%$
Regulator 2: Switching, $V_O = 1.5$ V, $I_{LOAD} = 1$ A, $\eta = 90\%$
Fill in the blank with a numerical answer: The total efficiency of the above power management module is $\eta =$ _____ % (up to 2 decimal places).

No, the answer is incorrect.
Score: 0

Accepted Answers:
(Type: Range) 86.78,88.54

2 points

Consider the circuit shown in Figure 1 for questions 11 and 12. Assume that M_{P1} , M_{P2} and M_{P3} are identical MOSFETs with $r_{ds} \rightarrow \infty$. Assume also, that Q_1 , Q_2 are BJTs with $\beta \rightarrow \infty$ and an emitter area ratio of 1: m.

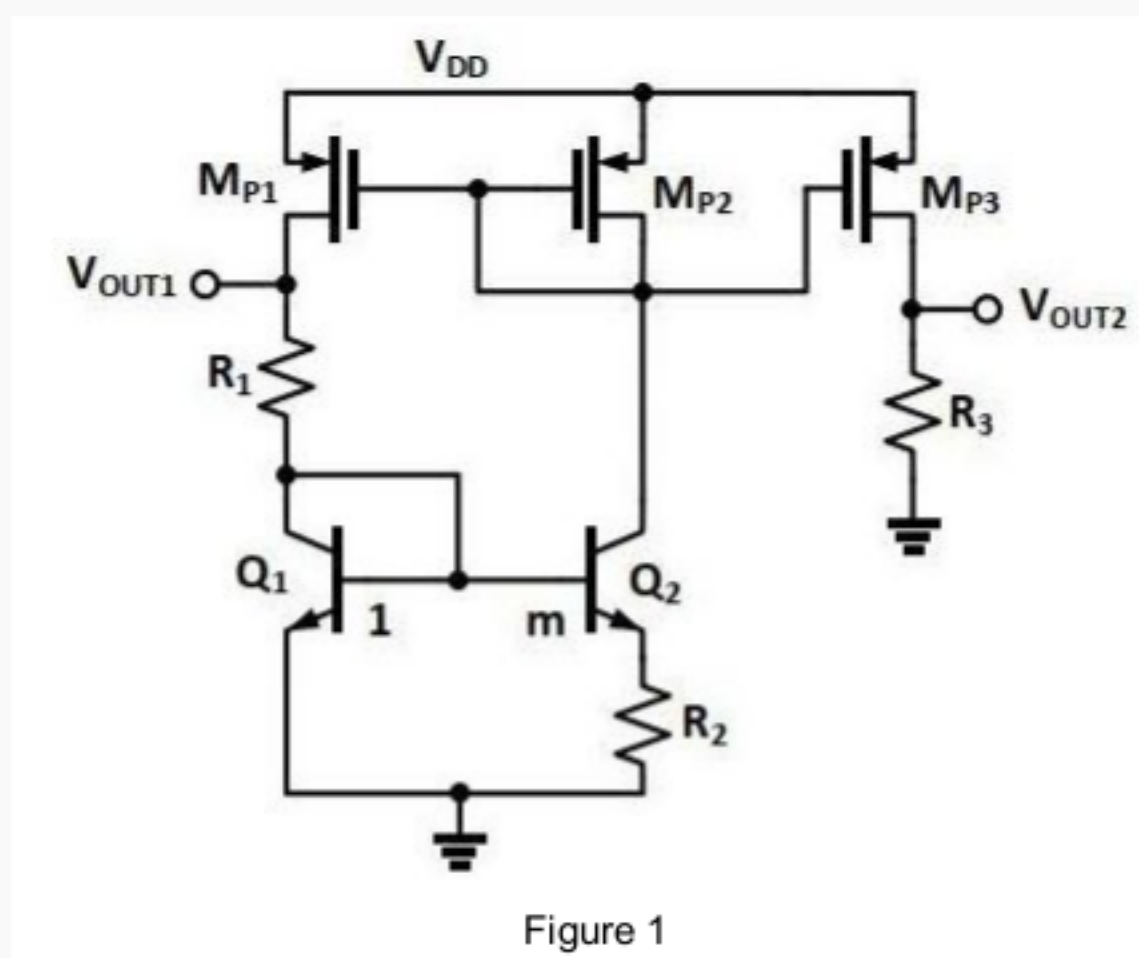


Figure 1

11) What is the expression for V_{OUT1} (in respect of the circuit shown in Figure 1)? 1 point

- $V_{OUT1} = V_{BE2} + (R_2/R_1) V_T \ln(1/m)$
 $V_{OUT1} = V_{BE1} + (R_2/R_1) V_T \ln(m)$
 $V_{OUT1} = V_{BE1} + (R_1/R_2) V_T \ln(m)$
 $V_{OUT1} = V_{BE2} + (R_2/R_1) V_T \ln(m)$

No, the answer is incorrect.
Score: 0

Accepted Answers:
 $V_{OUT1} = V_{BE1} + (R_1/R_2) V_T \ln(m)$

12) What is the expression for V_{OUT2} (in respect of the circuit shown in Figure 1)? 1 point

- $V_{OUT2} = (R_3/R_1) V_T \ln(1/m)$
 $V_{OUT2} = (R_3/R_2) V_T \ln(m)$
 $V_{OUT2} = (R_2/R_3) V_T \ln(m)$
 $V_{OUT2} = (R_2/R_1) V_T \ln(1/m)$

No, the answer is incorrect.
Score: 0

Accepted Answers:
 $V_{OUT2} = (R_3/R_2) V_T \ln(m)$

Consider the circuit shown in Figure 2 for questions 13 and 14. It was designed to get a constant V_{OUT} across temperature with the following parameters.

$V_{DD} = 1.8$ V, $R_1 = 6$ k Ω , $r_{ds} \rightarrow \infty$ for M_{P1} and M_{P2} , $V_{EB1} = 0.7$ V, $dV_T/dT = 0.1$ mV/K, $V_T = 26$ mV and $dV_{EB}/dT = -2$ mV/K.

Assume that M_{P1} and M_{P2} are perfectly matched and that the area of Q_2 is 20 times that of Q_1 . Adhere to the units mentioned in the question while filling in numerical answers.

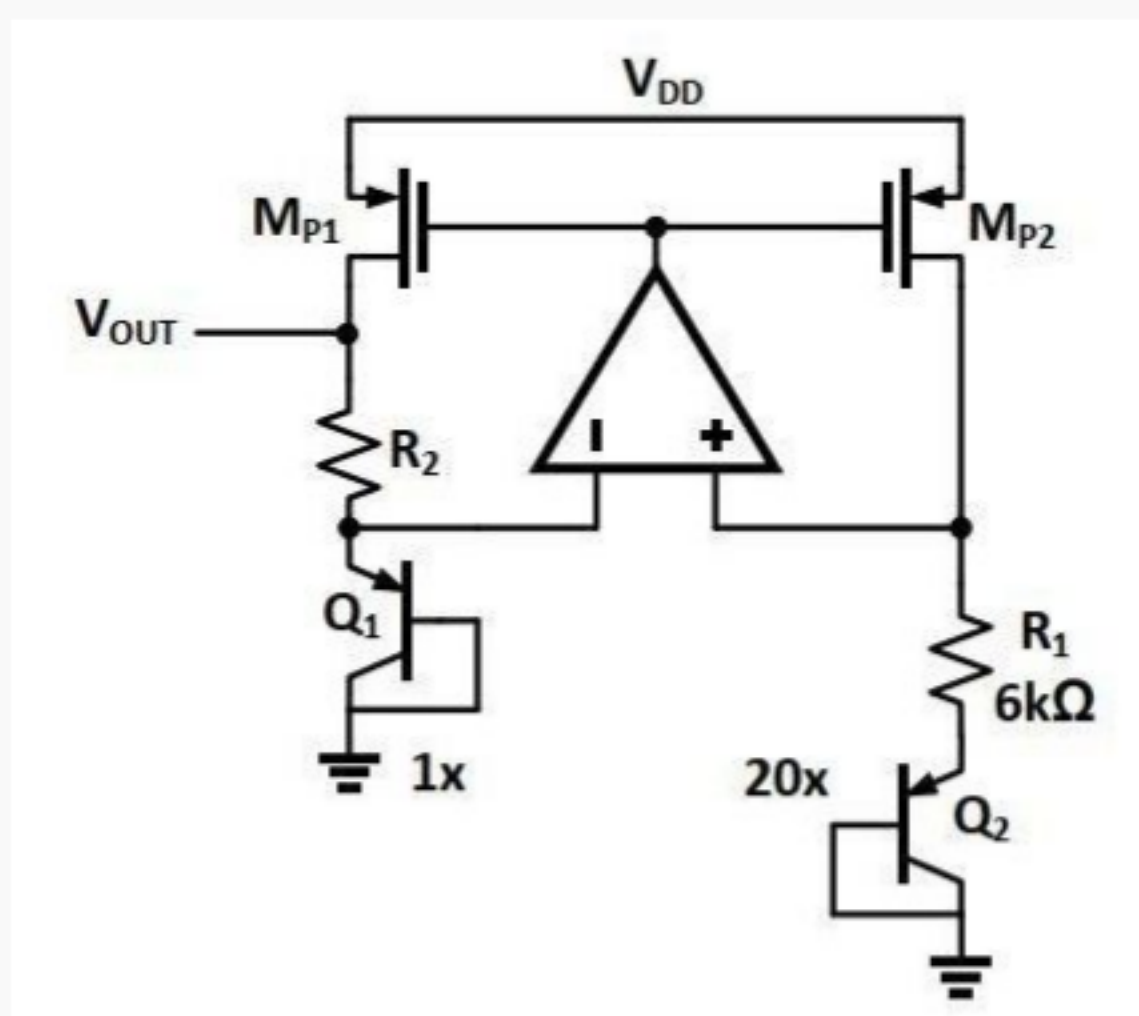


Figure 2

13) Fill in the blank with a numerical answer: The value of R_2 (in respect of the circuit shown in Figure 2) that is required to obtain a constant and temperature-independent V_{OUT} is _____ k Ω (up to 1 decimal place).

No, the answer is incorrect.
Score: 0

Accepted Answers:
(Type: Range) 39.5,40.5

2 points

14) Fill in the blank with a numerical answer: The value of R_2 (that was obtained in question 13) gives the value of V_{OUT} to be _____ volt (up to 2 decimal places).

No, the answer is incorrect.
Score: 0

Accepted Answers:
(Type: Range) 1.2,1.24

1 point