

# Unit 10 - Week 8

**Course outline**

How does an NPTEL online course work?

**Week 0**

**Week 1**

**Week 2**

**Week 3**

**Week 4**

**Week 5**

**Week 6**

**Week 7**

**Week 8**

- Gate Buffer and Non-Overlap Clock Generator in Gate- Driver Circuit
- Pulse-Width Modulator- Trailing Edge, Leading Edge and Dual Edge; Triangle Wave Generator
- Average Ramp Voltage of Single-Edge PW Modulator, Design Considerations of EA
- Delays Associated with PW Modulator, PFM and PSM Operation, DCM Operation using NMOS
- Designing a Zero-Cross Comparator, Inverter-Based Auto-Zeroed Comparator, Simulation Demo
- Current Mode Control- Peak, Valley, Emulated; VMC versus CMC; Sub-Harmonic Oscillation
- Ramp-Adaptive Slope Compensation to Avoid Current Loop Instability

**Quiz : Assignment 8**

Week 8 Feedback

**Week 9**

**Week 10**

**Week 11**

**Week 12**

**Download Videos**

**Assignment solutions**

## Assignment 8

The due date for submitting this assignment has passed. **Due on 2020-03-25, 23:59 IST.**  
 As per our records you have not submitted this assignment.

- 1) State whether the following statement is true or false. "Valley current-mode control offers a better line transient response compared to peak current-mode control." **1 point**
  - True
  - False

No, the answer is incorrect.  
 Score: 0  
 Accepted Answers: False
- 2) Which of the following statements is true (ignoring all losses) for a current-mode DC-DC converter with  $V_{in} = 2.5\text{ V}$  and  $V_{out} = 1.2\text{ V}$ ? **1 point**
  - Peak current-mode control is most suitable
  - Valley current-mode control is most suitable
  - Both peak and valley current-mode control are suitable
  - Current mode control cannot be used

No, the answer is incorrect.  
 Score: 0  
 Accepted Answers: Peak current-mode control is most suitable

- 3) State whether the following statement is true or false. "Operating a switching DC-DC converter in DCM is more power-efficient than operating it in CCM, for light loads." **1 point**
  - True
  - False

No, the answer is incorrect.  
 Score: 0  
 Accepted Answers: True

Consider the gate driver buffers shown in Figure 1, for questions 4 to 7. Assume that the transistors in the gate driver buffers operate in the linear/triode region. All of the gate driver circuitry operates from a common supply voltage of 1.8 V. Adhere to the units mentioned in the question while filling in numerical answers. Use information provided / obtained in a previous question to answer subsequent questions.

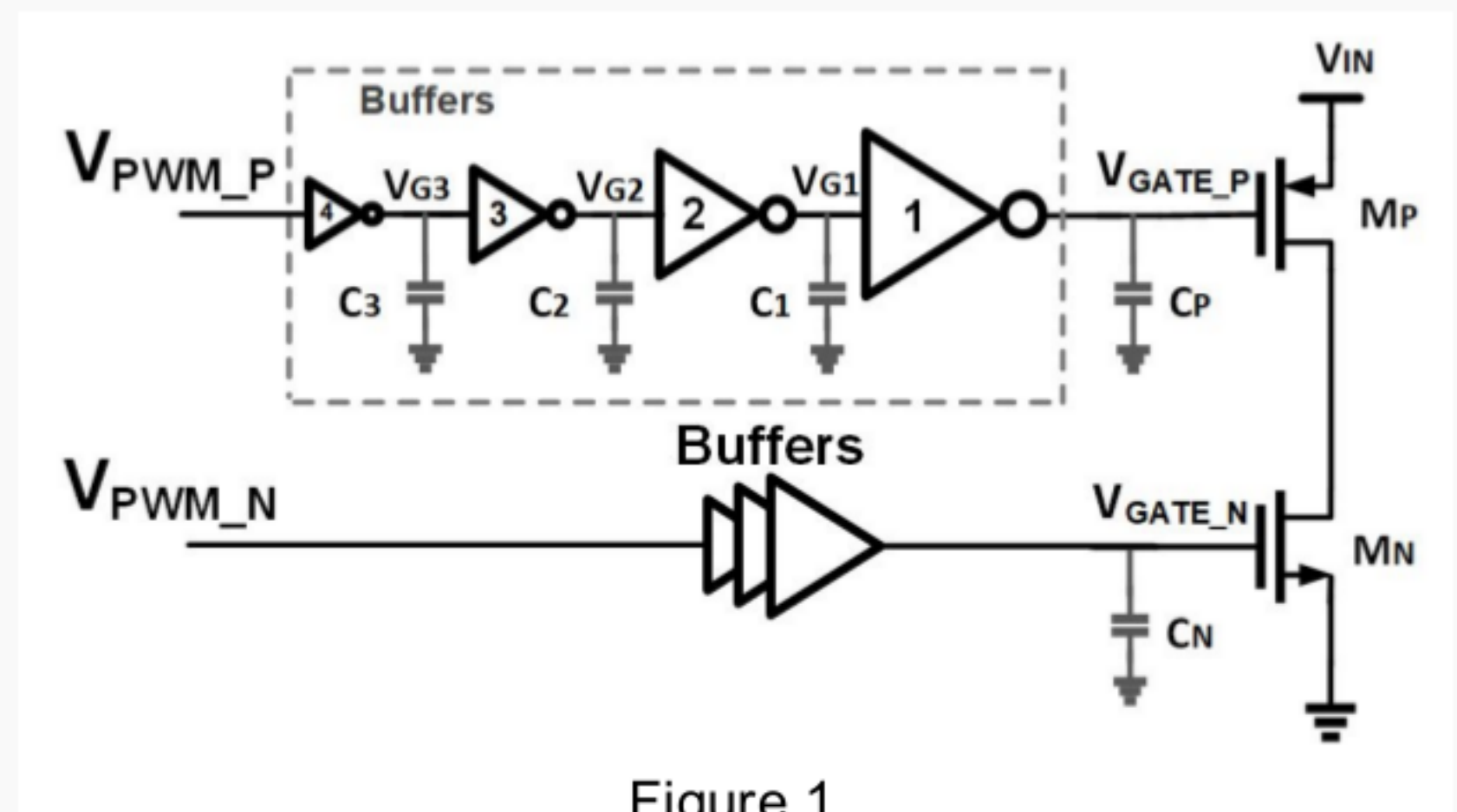


Figure 1

- 4) Fill in the blank with a numerical answer: Given  $C_p = 20\text{ pF}$ , the  $R_{DS,ON}$  of the PMOS and NMOS transistors used in inverter-1, that gives equal rise and fall times respectively (10% to 90% of  $V_{DD}$  and vice versa) of 100 ps, is  $\_\_\_\_\_\_ \Omega$  (up to 2 decimal places).
 

No, the answer is incorrect.  
 Score: 0  
 Accepted Answers: (Type: Range) 2,2.5 **1 point**
- 5) Fill in the blank with a numerical answer: Given  $\mu_p C_{ox} = 50\text{ }\mu\text{A/V}^2$  and  $|V_{T,p}| = 0.5\text{ V}$ , the W/L ratio of the PMOS transistor used in inverter-1, that is required to achieve a rise time (10% to 90% of  $V_{DD}$ ) of 100 ps, is  $\_\_\_\_\_\_ \times 10^3$  (up to 2 decimal places).
 

No, the answer is incorrect.  
 Score: 0  
 Accepted Answers: (Type: Range) 6.15,7,7 **1 point**
- 6) Fill in the blank with a numerical answer: Given  $\mu_n C_{ox} = 150\text{ }\mu\text{A/V}^2$  and  $V_{T,n} = 0.5\text{ V}$ , the W/L ratio of the NMOS transistor used in inverter-1, that is required to achieve a fall time (90% to 10% of  $V_{DD}$ ) of 100 ps, is  $\_\_\_\_\_\_ \times 10^3$  (up to 2 decimal places).
 

No, the answer is incorrect.  
 Score: 0  
 Accepted Answers: (Type: Range) 2,2.6 **1 point**
- 7) Fill in the blank with a numerical answer: The ratio of the load capacitance at the output of an inverter to its input capacitance is defined as the fanout of the inverter. Assuming, (i) that the fanout scales linearly with the W/L ratio of the inverter's transistors, and (ii) that every inverter has a fanout of 10, the W/L ratio of the PMOS transistor used in inverter-4, that gives equal rise times (10% to 90% of  $V_{DD}$ ) of 100 ps at the output of every inverter, is  $\_\_\_\_\_\_$  (up to 2 decimal places).
 

No, the answer is incorrect.  
 Score: 0  
 Accepted Answers: (Type: Range) 6.15,7,7 **1 point**

- 8) Consider the ramp generator circuit shown in Figure 2, for question 8. Adhere to the units mentioned in the question while filling in numerical answers.

 


Figure 2

- Fill in the blank with a numerical answer: Given that  $I_{BIAS} = 5\text{ }\mu\text{A}$  and assuming that the NMOS reset switch resets  $V_{OUT}$  instantaneously, the capacitance of the capacitor C that is required to generate a ramp for trailing-edge PW modulation at  $F_{SW} = 1\text{ MHz}$ , with a peak voltage  $V_m = 1\text{ V}$ , is  $\_\_\_\_\_\_ \text{ pF}$  (no decimal places).
 

No, the answer is incorrect.  
 Score: 0  
 Accepted Answers: (Type: Range) 4.99,5 **1 point**

Consider the zero-cross comparator shown in Figure 3, for questions 9 to 13. Adhere to the units mentioned in the question while filling in numerical answers. Use information provided / obtained in a previous question to answer subsequent questions.

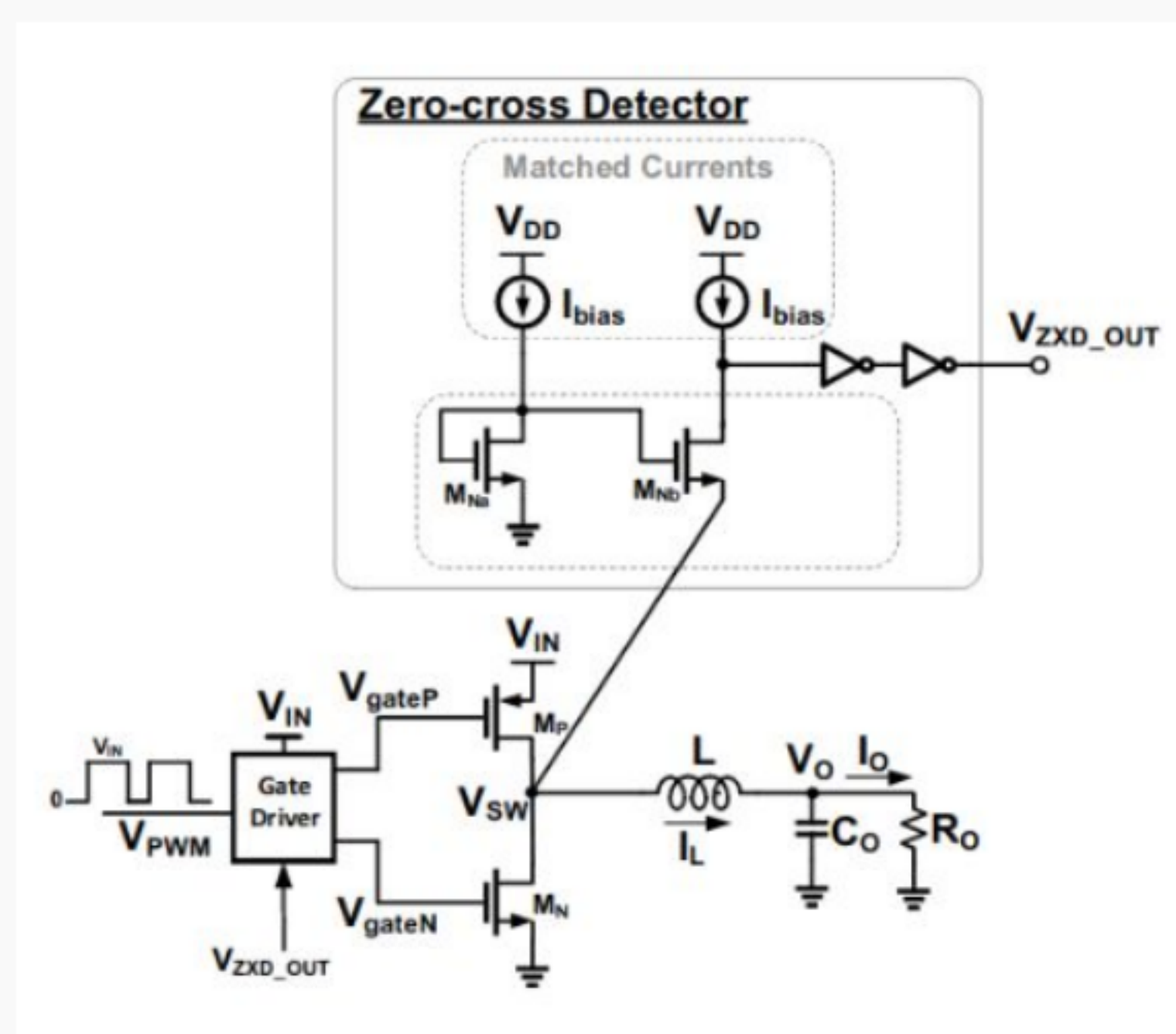


Figure 3

- 9) Fill in the blank with a numerical answer: Given that transistors  $M_{Na}$  and  $M_{Nb}$  operate in the saturation region,  $\mu_n C_{ox} = 150\text{ }\mu\text{A/V}^2$ ,  $V_{T,n} = 0.5\text{ V}$ ,  $I_{BIAS} = 1.5\text{ }\mu\text{A}$  and  $(W/L)_{M,Na} = (W/L)_{M,Nb} = 2$  (when transistors  $M_{Na}$  and  $M_{Nb}$  are perfectly matched), then ignoring the effect of channel length modulation, the gate-to-source voltage  $V_{GS}$  of transistor  $M_{Nb}$ , at which the zero-crossing of the switching node  $V_{SW}$  is detected, is  $\_\_\_\_\_\_ \text{ mV}$  (no decimal places).
 

No, the answer is incorrect.  
 Score: 0  
 Accepted Answers: (Type: Numeric) 600 **1 point**
- 10) Fill in the blank with a numerical answer (include the sign as well): Supposing that transistor  $M_{Nb}$  is not perfectly matched with transistor  $M_{Na}$ , in that  $M_{Nb}$  has a current factor that is greater than that of  $M_{Na}$  by 5% (while  $M_{Na}$  has the value mentioned in question 9), the zero-crossing of the switching node  $V_{SW}$  is detected with an offset of  $\_\_\_\_\_\_ \text{ mV}$  (up to 1 decimal place).
 

No, the answer is incorrect.  
 Score: 0  
 Accepted Answers: (Type: Range) 2,2,2,2.6 **1 point**
- 11) Fill in the blank with a numerical answer (include the sign as well): Given  $V_{IN} = 1.8\text{ V}$ ,  $V_O = 1\text{ V}$ ,  $L = 1\text{ }\mu\text{H}$ , switching frequency ( $F_{SW}$ ) = 5 MHz and  $R_{DS,ON,MP} = R_{DS,ON,MN} = 100\text{ m}\Omega$ , the value of the inductor current at which the zero-crossing of the switching node  $V_{SW}$  is detected (in respect of question 10) is  $\_\_\_\_\_\_ \text{ mA}$  (up to 1 decimal place).
 

Additional exercise (not evaluated): Find the duration over which  $M_N$  remains ON, during  $T_{OFF}$ , in terms of the load current. Hint: Use the expression for the voltage conversion ratio in DCM.

No, the answer is incorrect.  
 Score: 0  
 Accepted Answers: (Type: Range) -26,-22 **1 point**
- 12) Fill in the blank with a numerical answer (include the sign as well): Supposing that transistor  $M_{Nb}$  is not perfectly matched with transistor  $M_{Na}$ , in that  $M_{Nb}$  has a threshold voltage that is greater than that of  $M_{Na}$  by 2% (while  $M_{Na}$  has the value mentioned in question 9), the zero-crossing of the switching node  $V_{SW}$  is detected with an offset of  $\_\_\_\_\_\_ \text{ mV}$  (up to 1 decimal place).
 

No, the answer is incorrect.  
 Score: 0  
 Accepted Answers: (Type: Range) -11,-9 **1 point**
- 13) Fill in the blank with a numerical answer (include the sign as well): Given  $V_{IN} = 1.8\text{ V}$ ,  $V_O = 1\text{ V}$ ,  $L = 1\text{ }\mu\text{H}$ , switching frequency ( $F_{SW}$ ) = 5 MHz and  $R_{DS,ON,MP} = R_{DS,ON,MN} = 100\text{ m}\Omega$ , the value of the inductor current at which the zero-crossing of the switching node  $V_{SW}$  is detected (in respect of question 12) is  $\_\_\_\_\_\_ \text{ mA}$  (up to 1 decimal place).
 

Additional exercise (not evaluated): Find the duration over which  $M_N$  remains ON, during  $T_{OFF}$ , in terms of the load current. Hint: Use the expression for the voltage conversion ratio in DCM.

No, the answer is incorrect.  
 Score: 0  
 Accepted Answers: (Type: Range) 90,110 **1 point**
- 14) Fill in the blank with a numerical answer (specify only the absolute value): The inductor current in a peak-current-mode controlled switching converter rises (during  $T_{ON}$ ) with a slope of 800 kA/s and falls (during  $T_{OFF}$ ) with a slope of -1000 kA/s. The minimum possible slope of the compensating ramp that will stabilise the current loop of the converter is  $\_\_\_\_\_\_ \text{ kA/s}$  (no decimal places).
 

No, the answer is incorrect.  
 Score: 0  
 Accepted Answers: (Type: Numeric) 100 **1 point**