

Unit 5 - Week 4

Course outline

How to access the portal

Week 1

Week 2

Week 3

Week 4

Modelling of Three-Phase Transformers – Part III

Modelling of Three-Phase Transformers – Part IV

Modelling of Step Voltage Regulators - Part I

Modelling of Step Voltage Regulators – Part II

Modelling of Step Voltage Regulators – Part III

Quiz : Assignment 4

Solution for Assignment 4

Week 5

Week 6

Week 7

Week 8

WEEKLY FEEDBACK

DOWNLOAD VIDEOS

Assignment 4

The due date for submitting this assignment has passed. As per our records you have not submitted this assignment.

Due on 2019-08-28, 23:59 IST.

1) To convert line-to-line voltages to line-to-neutral voltages, $[W]$ matrix is used. 2 points

Then, the $[W]$ matrix in the following equation is given by

$$[VLN_{ABC}] = [W][VLL_{ABC}]$$

where, $[VLN_{ABC}] = [V_{AN} \ V_{BN} \ V_{CN}]^T$ and $[VLL_{ABC}] = [V_{AB} \ V_{BC} \ V_{CA}]^T$

$[W] = \begin{bmatrix} 1 & -1 & 0 \\ 0 & 1 & -1 \\ -1 & 0 & 1 \end{bmatrix}$

$[W] = \begin{bmatrix} 1 & 0 & -1 \\ -1 & 1 & 0 \\ 0 & -1 & 1 \end{bmatrix}$

$[W] = \frac{1}{3} \begin{bmatrix} 2 & 1 & 0 \\ 0 & 2 & 1 \\ 1 & 0 & 2 \end{bmatrix}$

$[W] = \frac{1}{3} \begin{bmatrix} 1 & -1 & 0 \\ 1 & 2 & 0 \\ -2 & -1 & 0 \end{bmatrix}$


No, the answer is incorrect. Score: 0

Accepted Answers:

$$[W] = \frac{1}{3} \begin{bmatrix} 2 & 1 & 0 \\ 0 & 2 & 1 \\ 1 & 0 & 2 \end{bmatrix}$$

Data for the Q. 2, Q.3 and Q.4: A delta/delta (Dd0) connected transformer with the turns ratio of $n_t = 20$ is shown in the following figure. The secondary-side delta currents are
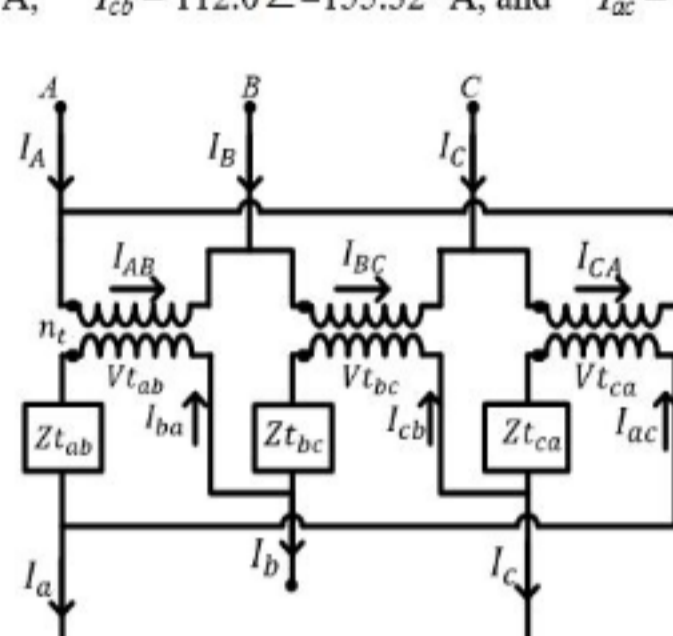
$$I_{ba} = 210.0 \angle -24.84^\circ \text{ A}, \quad I_{cb} = 112.0 \angle -155.32^\circ \text{ A}, \quad \text{and} \quad I_{ac} = 112.0 \angle 84.12^\circ \text{ A},$$



2) The secondary side line currents (A) I_a , I_b , and I_c respectively are 4 points

- 268.19∠-48.10, 295.26∠171.93, 194.53∠54.4
- 295.26∠171.93, 194.53∠54.4, 268.19∠-48.10
- 194.53∠54.4, 268.19∠-48.10, 295.26∠171.93
- 268.19∠-48.10, 238.83∠176.87, 220.78∠74.4

No, the answer is incorrect. Score: 0

Accepted Answers:

$$268.19 \angle -48.10, \quad 295.26 \angle 171.93, \quad 194.53 \angle 54.4$$

3) The primary side delta currents (A) I_{AB} , I_{BC} , and I_{CA} respectively are 2 points

- 5.6∠-155.32, 10.5∠-24.84, 5.6∠84.12
- 10.5∠-24.84, 5.6∠-155.32, 5.6∠84.12
- 10.5∠155.16, 5.6∠24.68, 5.6∠-95.88
- 5.6∠24.68, 10.5∠155.16, 5.6∠-95.88

No, the answer is incorrect. Score: 0

Accepted Answers:

$$10.5 \angle -24.84, \quad 5.6 \angle -155.32, \quad 5.6 \angle 84.12$$

4) The primary side line currents (A) I_A , I_B , and I_C respectively are 4 points

- 4.92∠171.93, 3.24∠54.40, 4.47∠-48.10
- 4.47∠-48.10, 4.92∠171.93, 3.24∠54.40
- 14.76∠171.93, 9.73∠54.40, 13.41∠-48.10
- 13.41∠-48.10, 14.76∠171.93, 9.73∠54.40

No, the answer is incorrect. Score: 0

Accepted Answers:

$$13.41 \angle -48.10, \quad 14.76 \angle 171.93, \quad 9.73 \angle 54.40$$

5) The relation between voltage transformation ratio a_t (HV to LV) and actual winding turn-ratio (n_t) of a grounded- Δ / Δ step-down transformer connection is 2 points

- $n_t = 3a_t$
- $n_t = \sqrt{3} a_t$
- $n_t = a_t$
- $n_t = a_t / \sqrt{3}$


No, the answer is incorrect. Score: 0

Accepted Answers:

$$n_t = a_t / \sqrt{3}$$

Data for the Q.6, Q.7 and Q.8: The 7200/415 V grounded wye / grounded wye transformer is shown in the following figure. The primary side line-to-line voltages are
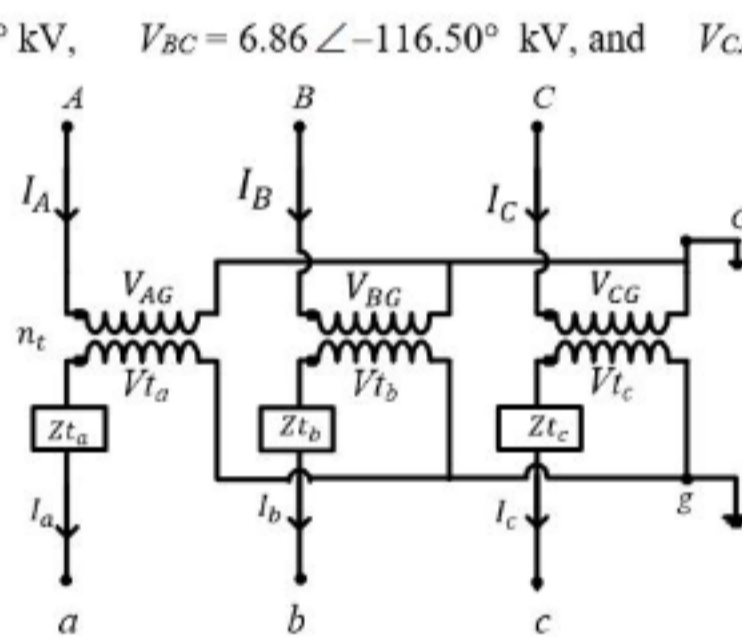
$$V_{AB} = 6.67 \angle -2.50^\circ \text{ kV}, \quad V_{BC} = 6.86 \angle -116.50^\circ \text{ kV}, \quad \text{and} \quad V_{CA} = 7.37 \angle 119.26^\circ \text{ kV}.$$



6) The primary side phase voltages (kV) V_{AG} , V_{BG} , and V_{CG} respectively are 4 points

- 2.36∠-34.48, 3.63∠-147.67, 3.68∠93.21
- 3.08∠-33.21, 3.89∠-148.97, 4.03∠92.46
- 4.09∠-33.21, 3.78∠-148.97, 4.19∠92.46
- 5.44∠-34.48, 3.37∠-147.67, 3.47∠93.21

No, the answer is incorrect. Score: 0

Accepted Answers:

$$4.09 \angle -33.21, \quad 3.78 \angle -148.97, \quad 4.19 \angle 92.46$$

7) The secondary side phase voltages (kV) V_{t_a} , V_{t_b} , and V_{t_c} respectively are 2 points

- 0.236∠-33.21, 0.218∠-148.97, 0.241∠92.46
- 0.321∠-33.21, 0.268∠-148.97, 0.299∠92.46
- 0.344∠-34.48, 0.256∠-147.67, 0.278∠93.21
- 0.356∠-34.48, 0.219∠-147.67, 0.225∠93.21

No, the answer is incorrect. Score: 0

Accepted Answers:

$$0.236 \angle -33.21, \quad 0.218 \angle -148.97, \quad 0.241 \angle 92.46$$

8) The secondary side no load line voltages (kV) V_{ab} , V_{bc} , and V_{ca} respectively are 2 points

- 0.445∠-2.50, 0.301∠-116.50, 0.482∠119.26
- 0.234∠-2.50, 0.325∠-116.50, 0.495∠119.26
- 0.518∠-2.50, 0.345∠-116.50, 0.301∠119.26
- 0.385∠-2.50, 0.395∠-116.50, 0.425∠119.26

No, the answer is incorrect. Score: 0

Accepted Answers:

$$0.385 \angle -2.50, \quad 0.395 \angle -116.50, \quad 0.425 \angle 119.26$$

9) The three single-phase transformers of the following ratings are connected as ungrounded- Δ / Δ . Transformer rating: 100 kVA, 11 kV/415 V. The a_t parameter matrix of the connection is 4 points

$a_t = \begin{bmatrix} 30 & -30 & 0 \\ 0 & 30 & -30 \\ -30 & 0 & 30 \end{bmatrix}$

$a_t = \begin{bmatrix} 11.54 & 5.77 & 0 \\ 0 & 11.54 & 5.77 \\ 5.77 & 0 & 11.54 \end{bmatrix}$

$a_t = \begin{bmatrix} 20 & 10 & 0 \\ 0 & 20 & 10 \\ 10 & 0 & 20 \end{bmatrix}$

$a_t = \begin{bmatrix} 15.3 & -15.3 & 0 \\ 0 & 15.3 & -15.3 \\ -15.3 & 0 & 15.3 \end{bmatrix}$

No, the answer is incorrect. Score: 0

Accepted Answers:

$$a_t = \begin{bmatrix} 15.3 & -15.3 & 0 \\ 0 & 15.3 & -15.3 \\ -15.3 & 0 & 15.3 \end{bmatrix}$$

10) The equivalent line impedance from the regulator to the load center is $(0.25 + j 0.75) \Omega$. The R and X setting of the compensator are $(0.50 + j 1.5) \Omega$. If the rating of the CT is 600/5 A, the rating of PT is 2 points

- 6400/120 V
- 4200/120 V
- 7200/120 V
- 3900/120 V

No, the answer is incorrect. Score: 0

Accepted Answers:

$$7200/120 \text{ V}$$

11) If the tap position of the standard single-phase B-Type regulator is at +13, the a , b , c , and d parameters of the regulator are 2 points

- $a = 1.04, b = 0, c = 0, d = 0.97$
- $a = 0.92, b = 0, c = 0, d = 1.08$
- $a = 0.97, b = 0, c = 0, d = 1.04$
- $a = 1.08, b = 0, c = 0, d = 0.92$

No, the answer is incorrect. Score: 0

Accepted Answers:

$$a = 0.92, b = 0, c = 0, d = 1.08$$