

Unit – III

Small Signal Amplified

3.1 A transistor is said to be in a quiescent stage when

- (a) Emitter junction bias is just equal to collector junction bias.
- (b) no currents are flowing
- (c) no signal is applied to the input
- (d) it is unbiased

3.2 A transistor in amplifier circuit is biased such that

- (a) emitter junction is reverse biased and collector junction is forward biased
- (b) emitter junction is forward biased and collector junction is reverse biased
- (c) both junctions are forward biased
- (d) Both junctions are reverse biased.


3.3 The CB amplifier has fewer applications because

- (a) It exhibits poor current gain
- (b) It exhibits very low input impedance.
- (c) It exhibits high output impedance
- (d) It exhibits poor power gain

3.4 Which of the following statements is not correct for emitter follower circuit?

- (a) It raises power level.
- (b) It exhibits high input impedance and low output impedance
- (c) It has high current gain.
- (d) It has high voltage gain

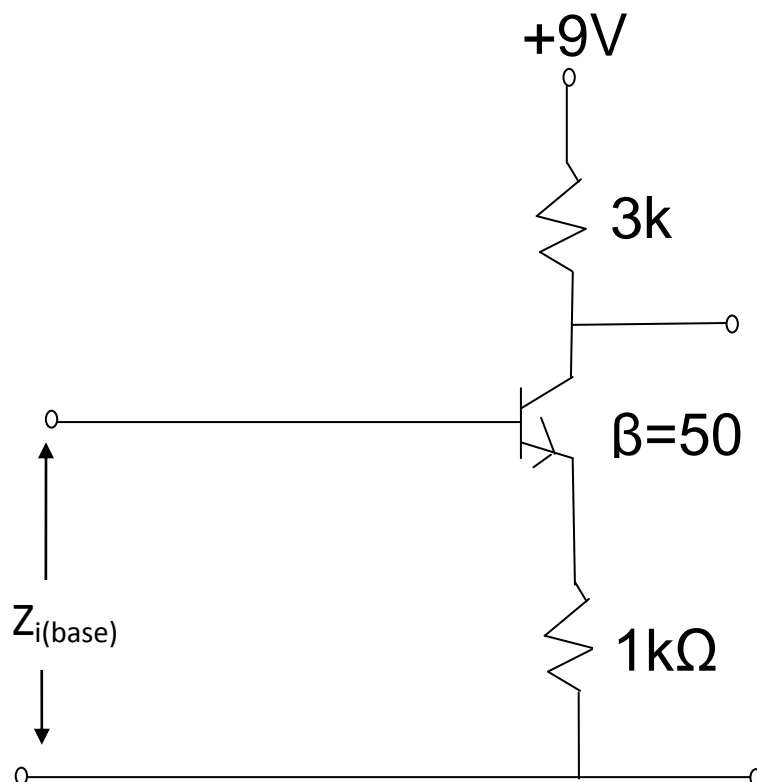3.5 In the section of CE amplifier shown in the fig., the input impedance $Z_{i(\text{base})}$ is



- (a) 50 k Ω
- (b) 1 k Ω
- (c) 50 Ω
- (d) 20 Ω


3.6 The most striking feature of CE amplifier responsible for its wide use is,

- (a) It has high current gain
- (b) It has high voltage gain
- (c) It has a phase difference of 180° between input and output.
- (d) It shows input and output impedances of the same order.

3.7 Assuming $V_{BE} = 0.7V$ and $\beta = 50$ for the transistor in the circuit shown in figure, the value of R_B for $V_{CE} = 2V$ is

- (a) 200 k Ω
- (b) 243 k Ω
- (c) 283 k Ω
- (d) 300 k Ω

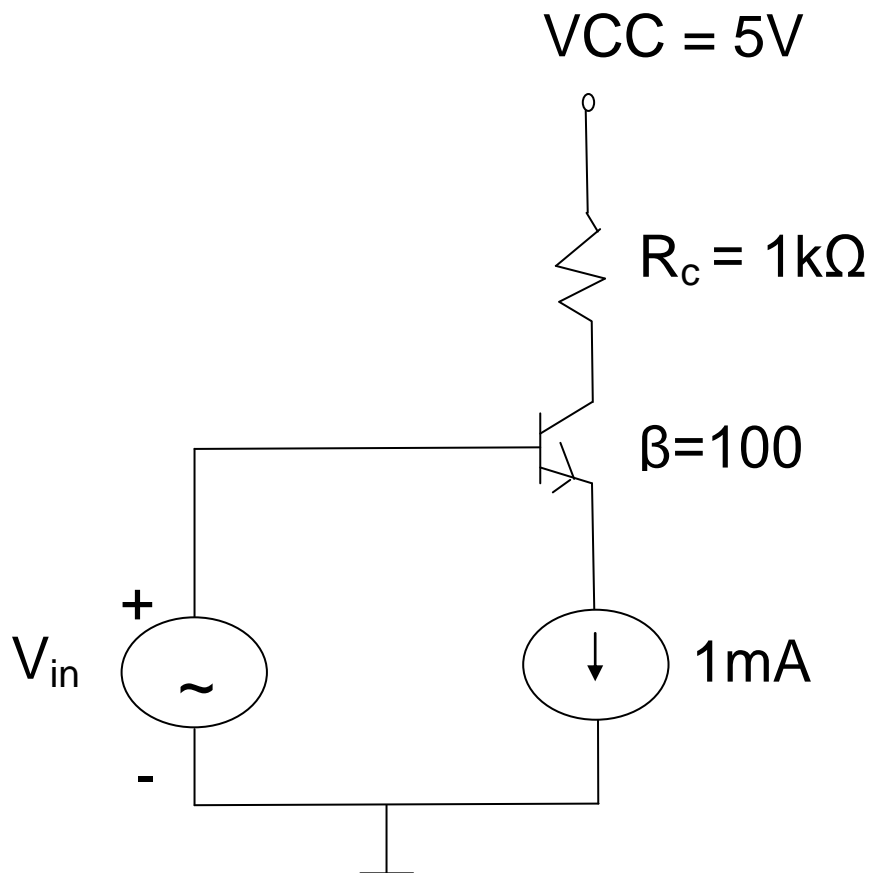3.8 The common emitter amplifier shown in figure is biased using a 1mA ideal current source. The approximate base current value is,



- (a) 0 μA
- (b) 10 μA
- (c) 100 μA
- (d) 1000 μA

Answer:

- 3.1 (c) 3.2 (b) 3.3 (b) 3.4 (d) 3.5 (a) 3.6 (d)
3.7 (c) 3.8 (b)